

## SECTION D: ELECTROSTATICS, CAPACITORS AND ELECTRICITY

Electrostatics (static electricity) is the study of electric charges at rest, the forces between them, and the electric fields associated with them.

Static electricity occurs when positive (+) or negative (-) electrical charges collect on an object's surface. There are several methods through which this condition can be caused.

One way is by rubbing certain materials together or pulling them apart. Another way is by bringing a charged material near to a neutral material, and also by sharing the charge on a body with another neutral insulated body when they come into contact with each other.

### Electrification by friction / charging by rubbing or friction

- When two dissimilar bodies are rubbed together, heat is generated due to friction
- The heat is sufficient to make the material of lower work function to release some electron, which are taken up by other material.
- The one which lost electrons become positively charged while the one which gained electrons becomes negatively charged
- The number of electrons lost is equal to the number of electrons acquire therefore two insulating bodies rubbed together acquire equal and opposite charges.

### Examples of charging by friction

- When a polythene rod (ebonite rod) is rubbed with fur (woolen duster), the ebonite rod becomes negatively charged while the duster becomes positively charged.
- If a glass rod (cellulose acetate) is rubbed with silk, a glass rod becomes positively charged while the silk becomes negatively charged.

### Insulators, semiconductors and conductors

#### Conductor

This is a material with free electrons and it can allow electricity and heat to pass through it.

**Examples:** Copper, bronze

#### Insulator

This is a material without free electrons and it cannot allow electricity and heat to pass through it.

**Examples:** Dry wood, plastic

#### Semiconductors

These are materials which allow electric charges to pass through them with difficulty.

**Examples:** Moist air, paper

### Law of electrostatics

Like charges repel each other and unlike charges attract each other.


### Precautions taken when carrying experiments in electrostatics

- (i) Apparatus must be insulated
- (ii) The surrounding must be free from dust and moisture

### Attraction of neutral body by charged body

Consider the uncharged conductor being brought near a negatively charged ebonite rod. Negative charges on the ebonite rod repel the free electrons on the conductor to the remote end and positive charge is thus left near the end of the metal adjacent to the ebonite rod. So the conductor is now attracted by the ebonite rod.

## GOLD LEAF ELECTROSCOPE (GLE)

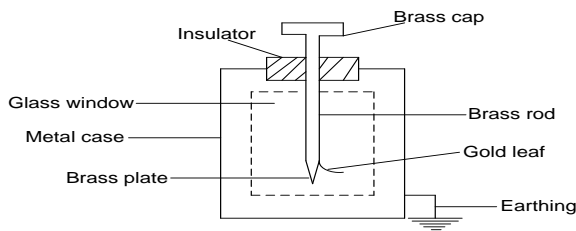

### Uses of GLE

- (i) Test for the presence of charge
- (ii) Test the sign of the charge
- (iii) To test the magnitude of charge
- (iv) Measure  $p. d$


### Electrostatic induction

It's a phenomenon that describes the formation of charges on a conductor when a charged body is brought near it.

The charge acquired is opposite to that of inducing body.

### Charging a gold leaf electroscope by induction


#### (a) Charging G.L.E negatively

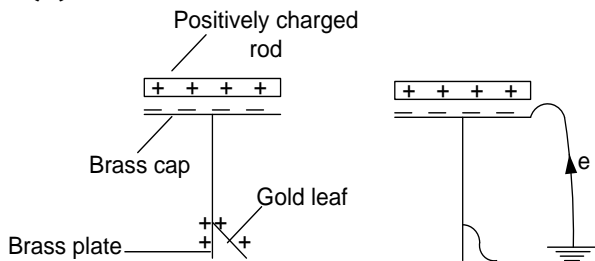

- ❖ A positively charged glass rod is brought near the cap of the G.L.E, negative charges are

- induced on the brass cap and positive charges on G.L and brass plate. The gold leaf diverges.
- ❖ With glass rod still in position, the G.L.E is earthed. Free electrons flow from the earth to the brass plate and gold leaf thus collapses.
- ❖ With the rod still in position, the earthing wire is removed.
- ❖ Glass rod is removed, the negative charges then redistribute themselves to the brass cap, plate and gold leaf thus causing the leaf to diverge. The electroscope is now negatively charged.

#### (b) Charging G.L.E positively

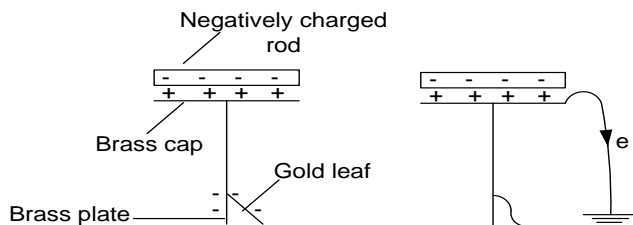

- ❖ A negatively charged rod is brought near the cap of the G.L.E, positive charges are induced

- on the brass cap and negative charges on G.L and brass plate. The gold leaf diverges.
- ❖ With glass rod still in position, the G.L.E is earthed. Free electrons flow from the plate and leaf to the earth thus the leaf collapses.
- ❖ With the rod still in position, the earthing wire is removed.
- ❖ The rod is removed, the positive charges then redistribute themselves to the brass cap, plate and gold leaf thus causing the leaf to diverge. The electroscope is now positively charged

### Testing for the sign of charge on a body

- ❖ Charge an electroscope negatively and the divergence noted. Bring the body under test near the cap of *GLE*. If the leaf divergence increases then that body is negatively charged, but if the divergence of the leaf decreases, then that body has either **positive** charge or it is **neutral body**
- ❖ To differentiate between the two alternatives, discharge the *GLE* and now charge it positively
- ❖ Bring the same body under test near the cap of oppositely charged *GLE*. If the leaf divergence increases again, then that body has positive charges but if the leaf divergence decreases then that body is neutral.


**Note:** Repulsion is the only confirmatory test for the sign of the charge

**Summary**

| Charge on GLE | Charge brought near cap | Effect on leaf divergence |
|---------------|-------------------------|---------------------------|
| +             | +                       | Increase (repulsion)      |
| -             | -                       | Increase (repulsion)      |
| +             | -                       | Decrease (attraction)     |
| -             | +                       | Decrease (attraction)     |
| + or -        | Uncharged body          | Decrease (attraction)     |

**Charging a conductor by induction**


**a) Positively**

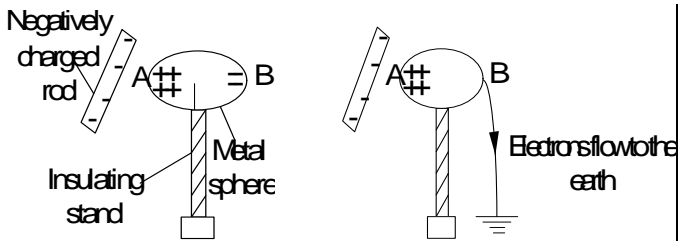

- ❖ Metal sphere on an insulating stand is placed near the negatively charged body. Free

- electrons in the metal sphere are repelled to the far end of the sphere.
- ❖ The sphere is earthed while the charged body is still in position. Free electrons move from the sphere to the earth.
- ❖ The earthing wire is removed while the charged rod is still in position
- ❖ The charged body is removed and charges distributes themselves all over the sphere. Hence the metal sphere is now positively charged.

**b) Negatively**

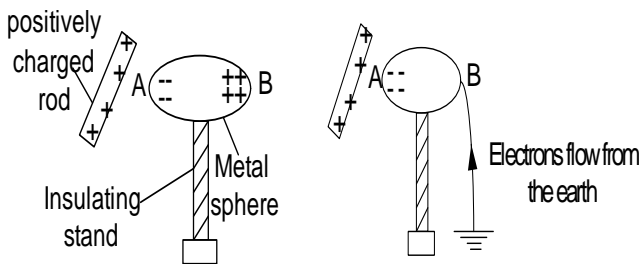


- ❖ Metal sphere on an insulating stand is placed near the positively charged body. Free

- electrons in the metal sphere are attracted to the near end of the sphere.
- ❖ The sphere is earthed while the charged body is still in position. Free electrons move from the earth to the sphere.
- ❖ The earthing wire is removed while the charged rod is still in position
- ❖ The charged body is removed and charges distributes themselves all over the sphere. Hence the metal sphere is now negatively charged.


**Separation of conductors**

i)

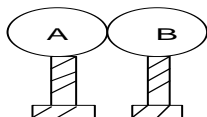


ii)

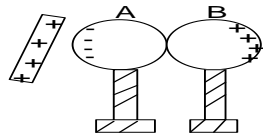Two identical brass spheres A and B are placed together so that they touch one another.




A positively charged rod is now brought near end A and as a result negative charge is induced at A and positive charges repelled to B.

iii)

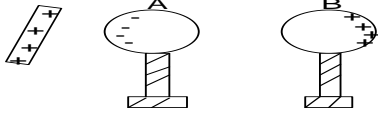

Keeping the positive rod in position, sphere B is moved a short distance away from B

iv)

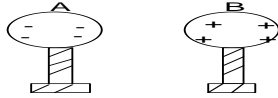

The charged rod is now removed and charges redistribute

Explain how two spherical conductors made of brass can be charged oppositely and simultaneously by induction.

### How to distinguish a conductor and an insulator using an electroscope

- ❖ An electroscope is given charge and the divergence noted. The material is brought near the cap of the electroscope
- ❖ If there is no change in divergence, the material is an insulator. If the leaf divergences material is a conductor

### Charging a body negatively at zero potential

- ❖ A positively charged glass rod is brought near end A of the conductor. Negative charges are induced at the near end and positive charges at the far end of the neutral body.
- ❖ With the glass rod still in position, body is earthed. Body is now negatively charged at zero potential

### Electrophorus


This an instrument for produce unlimited supply of charge but it is not source of energy though converts mechanical energy to electrical energy

### Distribution of charge over the surface of a conductor.


#### Surface charge density:

This is the quantity of charge per unit area over the surface of the conductor. Charge is mostly concentrated at sharp points.


Spherical conductor

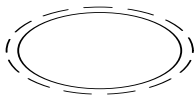

Rectangular conductor

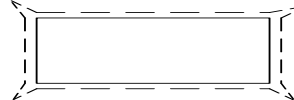

Triangular conductor

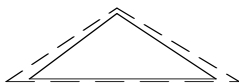


#### Note:

Charge only resides on the outside of a hollow conductor
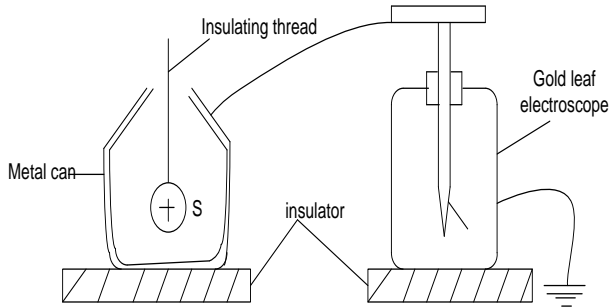
### Investigating charge distribution on a pear shaped conductor

- ❖ A proof plane is placed on the surface of the conductor. A sample of charge acquired by the proof plane is then transferred to a hollow metal can placed on the cap neutral electroscopes and the deflection of the electroscopes is noted
- ❖ The proof plane is then used to pick samples charges from different parts of the conductor and each time the deflection of the electroscopes is noted
- ❖ The greatest deflection is obtained when the sample of charge are picked from the pointed end of the conductor. Therefore the surface charge density of charges is greatest where the curvature is greatest

**Experiment to show distribution of charge in a hollow conductor.  
(Faraday's ice pail experiment)**



- ❖ A positively charged metal sphere, S is lowered into a metal can ( without touching it) connected to a gold leaf electroscope. The leaf of the electroscopes diverges

- ❖ S is withdrawn, the leaf of the electroscopes collapses
- ❖ S is again lowered inside the metal ( without touching it), the leaf of the electroscopes diverges to the same extent as before.
- ❖ S is then allowed to touch the can. The divergence of the leaf remains unchanged
- ❖ S is withdrawn and on testing , it is found to have no charge
- ❖ There must have been charge inside the can equal and opposite to the charge on S. since the leaf remains diverged, the charge on the can must be residing on the out side of it. This charge is equal to that which was originally on S


**Action at sharp points: [Corona discharge]**

The high electric field intensity at the sharp points of a charged conductor, ionizes the air molecules around the sharp points. The ions of opposite charge are attracted to the sharp point and neutralize the charge there. This way the conductor loses charge and the process is called **corona discharge**.

**Applications of action at sharp points:**

**(a) Lightning Conductor**

**Action of a lightning conductor**

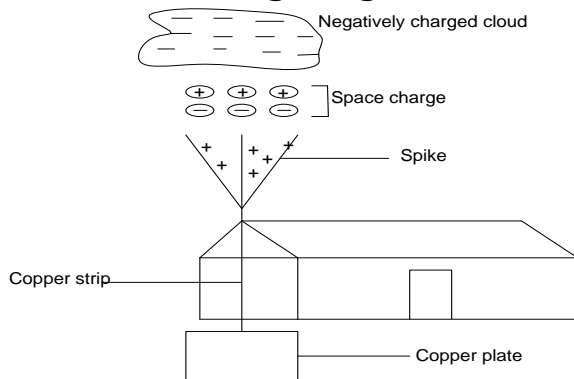


- When a charged cloud passes over a lightning conductor, it induces opposite charge on the spikes of the conductor which results to high electric field intensity
- The high electric field intensity on the spikes ionizes the air around it. Charge similar to those on the spikes is repelled to the clouds and neutralize charge on the cloud, while those opposite are attracted and discharged at the spikes
- This way charge from the cloud is safely conducted to the ground

**Effect of Lightning**

Clouds in relative motion become charged due to friction. The resulting charge builds up leading to a high p.d between the clouds and the earth. Large discharge currents through the building can cause them to burn

### (b) Vander graaf generator

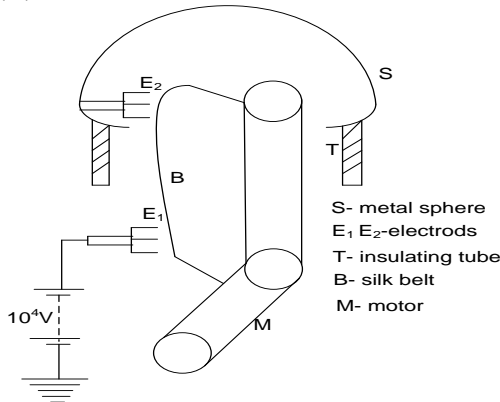

- ❖ The electrode  $E_1$  is made  $10^4V$  positive relative to the earth. The high electric field intensity at the sharp points of  $E_1$  ionizes air

around it repelling positive charges on to the belt.

- ❖ The belt driven by a motor carries this charge into the sphere. As it approaches  $E_2$ , it induces negative charge at the spikes of  $E_2$  and positive charge on the sphere
- ❖ The high electric field intensity around  $E_2$  ionizes air there, repelling negative charge onto the belt. The negative charge neutralizes positive charge on the belt before it goes over the upper pulley.
- ❖ The process is repeated many times until the potential of the sphere is about  $10^6V$  relative to the earth

### COULOMBS LAW OF ELECTROSTATIC

It states that the force between any two point charges is directly proportional to the product of the magnitude of the charges and inversely proportional to the square of the distance of separation of the charges.

$$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$$

For vacuum or air

$$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$$

$$\frac{1}{4\pi\epsilon_0} = 9 \times 10^9$$

$$F = \frac{9 \times 10^9 Q_1 Q_2}{r^2}$$

This law holds for all sign of charges. If  $Q_1$  and  $Q_2$  are unlike then the force is attractive but if they are like then the force is repulsive

#### Illustration




#### Example

1. Find the force between two point charges  $+4\mu C$  and  $-3\mu C$  placed 10cm apart

#### Solution

$$F = \frac{9 \times 10^9 Q_1 Q_2}{r^2} \quad \left| \quad F = \frac{9 \times 10^9 \times 4 \times 10^{-6} \times 3 \times 10^{-6}}{0.1^2} \quad \right| \quad F = 10.8N \text{ attractive}$$

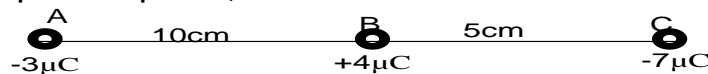2. Three point charges are placed at point A, B and C as shown below



Find the resultant force on the charge at B


#### Solution

$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$   
 $F_A = \frac{9 \times 10^9 \times 4 \times 10^{-6} \times 3 \times 10^{-6}}{0.1^2}$   
 $F_A = 10.8 \text{ N attracted towards A}$

$$F_C = \frac{9 \times 10^9 \times 4 \times 10^{-6} \times 7 \times 10^{-6}}{0.05^2}$$

$F_C = 100.8 \text{ N attracted towards C}$   
 $F_B = 100.8 - 10.8$   
 $F_B = 90 \text{ N attracted towards C}$

3.

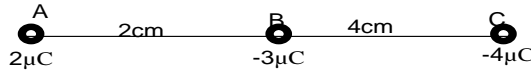

Calculate the force on  $-3\mu\text{C}$


**Solution**

$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$   
 $F_A = \frac{9 \times 10^9 \times 2 \times 10^{-6} \times 3 \times 10^{-6}}{0.02^2}$   
 $F_A = 135 \text{ N towards left}$

$$F_C = \frac{9 \times 10^9 \times 4 \times 10^{-6} \times 3 \times 10^{-6}}{0.04^2}$$

$F_C = 67.5 \text{ N towards left}$   
 $F_B = 135 + 67.5$   
 $F_B = 202.5 \text{ N towards left}$

4.

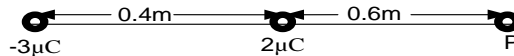

Find the resultant force acting at point P if a charge of  $1\mu\text{C}$  is placed at point P.


**Solution**

$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$   
 $F_3 = \frac{9 \times 10^9 \times 1 \times 10^{-6} \times 3 \times 10^{-6}}{1^2}$   
 $F_3 = 0.027 \text{ N towards left}$

$$F_2 = \frac{9 \times 10^9 \times 2 \times 10^{-6} \times 1 \times 10^{-6}}{0.6^2}$$

$F_2 = 0.05 \text{ N towards right}$   
 $F_P = 0.05 - 0.027$   
 $F_P = 0.023 \text{ N towards right}$

5.

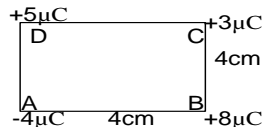


Find the resultant force at C

**Solution**

$x^2 = 4^2 + 4^2$   
 $x = \sqrt{32} = 5.66 \text{ cm}$   
 $\tan\theta = \frac{4}{4}$   
 $\theta = \tan^{-1}(1) = 45^\circ$   
 $F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$

$$F_A = \frac{9 \times 10^9 \times 4 \times 10^{-6} \times 3 \times 10^{-6}}{0.0566^2}$$

$F_A = 33.75 \text{ N}$   
 $F_B = \frac{9 \times 10^9 \times 8 \times 10^{-6} \times 3 \times 10^{-6}}{0.04^2}$   
 $F_B = 135 \text{ N upwards}$   
 $F_D = \frac{9 \times 10^9 \times 5 \times 10^{-6} \times 3 \times 10^{-6}}{0.04^2}$   
 $F_D = 84.375 \text{ N towards right}$   
 $F = \begin{pmatrix} -33.7 \cos 45 \\ -33.7 \sin 45 \end{pmatrix} + \begin{pmatrix} 0 \\ 135 \end{pmatrix} + \begin{pmatrix} 84.375 \\ 0 \end{pmatrix}$   
 $F = \begin{pmatrix} 60.57 \\ 111.17 \end{pmatrix}$

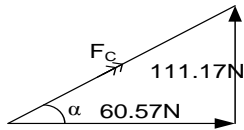

$$F^2 = 60.57^2 + 111.17^2$$


$$F = 126.59N$$

$$\tan \alpha = \frac{111.17}{60.57}$$


$$\alpha = \tan^{-1} \left( \frac{111.17}{60.57} \right) = 61.42^\circ$$

Resultant forces at C is 126.59N at 61.42° to the horizontal

6.

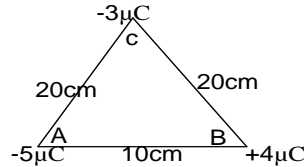

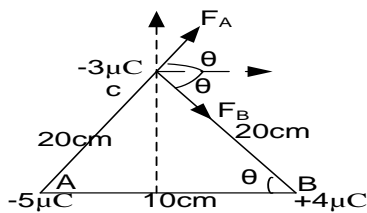Find the resultant force at C  
**Solution**



$$\cos \theta = \frac{5}{20}$$

$$\theta = \cos^{-1} \left( \frac{1}{4} \right) = 75.5^\circ$$

$$F = \frac{Q_1 Q_2}{4\pi \epsilon_0 r^2}$$

$$F_A = \frac{9 \times 10^9 \times 5 \times 10^{-6} \times 3 \times 10^{-6}}{0.2^2}$$


$$F_A = 3.375N$$

$$F_B = \frac{9 \times 10^9 \times 4 \times 10^{-6} \times 3 \times 10^{-6}}{0.2^2}$$

$$F_B = 2.7N$$

$$F = \begin{pmatrix} 3.375 \cos 75.5 \\ 3.375 \sin 75.5 \end{pmatrix} + \begin{pmatrix} 2.7 \cos 75.5 \\ -2.7 \sin 75.5 \end{pmatrix}$$
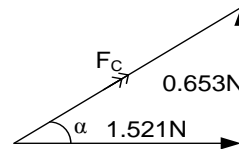
$$F = \begin{pmatrix} 1.521 \\ 0.653 \end{pmatrix}$$



$$F^2 = 1.521^2 + 0.653^2$$


$$F = 1.655N$$

$$\tan \alpha = \frac{0.653}{1.521}$$


$$\alpha = 23.23^\circ$$

Resultant forces at C is 1.655N at 23.23° to the horizontal

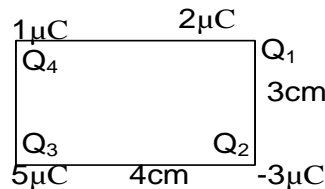7. Four point charges  $Q_1, Q_2, Q_3$  and  $Q_4$  are placed at different corners of rectangle



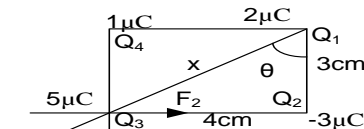Find the resultant force at  $Q_3$   
**Solution**



$$x^2 = 4^2 + 3^2$$

$$x = \sqrt{25} = 5cm$$

$$\tan \theta = \frac{4}{3}$$

$$\theta = 53.13^\circ$$

$$F = \frac{Q_1 Q_2}{4\pi \epsilon_0 r^2}$$

$$F_4 = \frac{9 \times 10^9 \times 1 \times 10^{-6} \times 5 \times 10^{-6}}{0.03^2}$$

$$F_4 = 50N \text{ downwards}$$

$$F_2 = \frac{9 \times 10^9 \times 5 \times 10^{-6} \times 3 \times 10^{-6}}{0.04^2}$$

$$F_2 = 84.4N \text{ towards the right}$$

$$F_1 = \frac{9 \times 10^9 \times 5 \times 10^{-6} \times 2 \times 10^{-6}}{0.05^2}$$

$$F_1 = 36N$$

$$F = \begin{pmatrix} 0 \\ -50 \end{pmatrix} + \begin{pmatrix} 84.4 \\ 0 \end{pmatrix} + \begin{pmatrix} -36\sin 53.13 \\ -36\cos 53.13 \end{pmatrix}$$

$$F = \begin{pmatrix} 55.6 \\ -71.6 \end{pmatrix}$$

$$F^2 = 55.6^2 + 71.6^2$$


$$F = 90.66N$$

$$\tan \alpha = \frac{71.6}{55.6}$$

$$\alpha = 52.2^\circ$$

Resultant forces at  $Q_3$  is  $90.66N$  at  $52.2^\circ$  to the horizontal

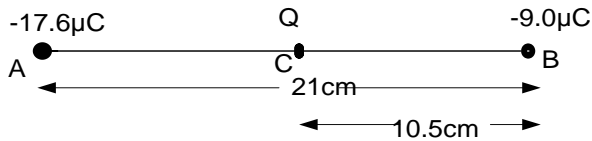8. Two points charges A and B of  $-17.6\mu C$  and  $-9.0\mu C$  respectively are placed in vacuum at a distance of  $21cm$  apart. When a third charge C is placed mid way between A and B, the net force on B is zero
- Determine the charge on C
  - Sketch the electric field lines for the above charge distribution



$$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$$

$$F_A = \frac{9 \times 10^9 \times 17.6 \times 10^{-6} \times 9 \times 10^{-6}}{0.21^2} (\leftarrow)$$

$$F_C = \frac{9 \times 10^9 \times 9 \times 10^{-6} \times Q}{0.105^2} (\rightarrow)$$


$$F_A = F_C$$

$$\frac{9 \times 10^9 \times 17.6 \times 10^{-6} \times 9 \times 10^{-6}}{0.21^2} = \frac{9 \times 10^9 \times 9 \times 10^{-6} \times Q}{0.105^2}$$

$$Q = 4.4 \times 10^{-6} C$$

9. Two pith balls P and Q each of mass  $0.1g$  are separately suspended from the same point by threads  $30cm$  long. When the balls are given equal charges, they repel each other and come to rest  $18cm$  apart. Find the magnitude of each charge.

**Solution**

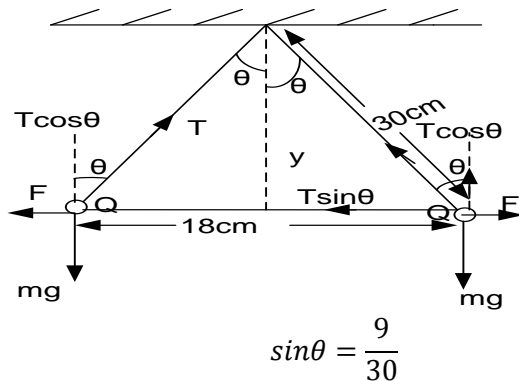

$$\theta = 17.5^\circ$$

$$(\uparrow) T \cos \theta = mg$$

$$T \cos 17.5^\circ = 0.1 \times 10^{-3} \times 9.81$$


$$T = 1.029 \times 10^{-3} N$$

$$(\rightarrow) T \sin \theta = \frac{Q^2}{4\pi\epsilon_0 x (0.18)^2}$$

$$1.029 \times 10^{-3} \times \frac{9}{30} = \frac{9 \times 10^9 \times Q^2}{(0.18)^2}$$

$$Q = 3.33 \times 10^{-8} C$$

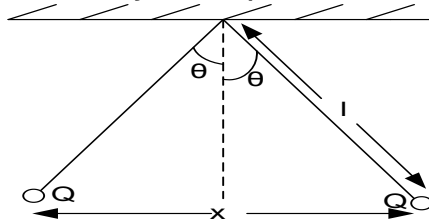
10. Two identical conducting balls of mass  $m$  are each suspended in air from a thick of length  $l$ , When the two balls are each given identical charge  $Q$ , they move apart as shown below



If at equilibrium each thread makes an angle  $\theta$  with vertical and separated  $x$  is given by

$$x = \left( \frac{Q^2 l}{2\pi\epsilon_0 mg} \right)^{1/3}$$

**Solution**

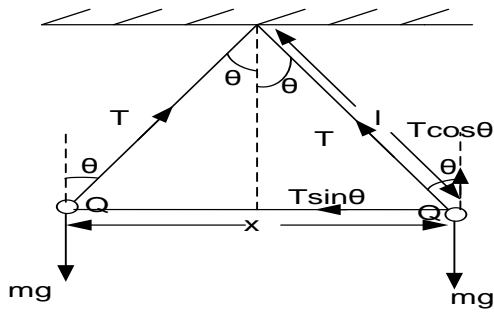

$$T \sin \theta = \frac{Q^2}{4\pi\epsilon_0 x^2} \dots \dots \dots (1)$$

$$T \cos \theta = mg \dots \dots \dots (2)$$

$$\text{eqn1} \div \text{eqn2}$$

$$\frac{T \sin \theta}{T \cos \theta} = \frac{\left(\frac{Q^2}{4\pi\epsilon_0 x^2}\right)}{mg}$$

$$x^2 = \frac{Q^2}{4\pi\epsilon_0 mg \tan \theta}$$

But for small angles in radians  $\tan \theta \approx \sin \theta$

$$\sin \theta = \frac{x}{2l} = \frac{x}{2l}$$

$$x^2 = \left(\frac{Q^2}{4\pi\epsilon_0 mg \frac{x}{2l}}\right)$$


$$x^3 = \left(\frac{Q^2 l}{2\pi\epsilon_0 mg}\right)$$

$$x = \left(\frac{Q^2 l}{2\pi\epsilon_0 mg}\right)^{1/3}$$

**Exercise**


1. Two points charges A and B of  $47.0\mu\text{C}$  and  $24.0\mu\text{C}$  respectively are placed in vacuum at a distance of 30cm apart. When a third charge C of  $-35.0\mu\text{C}$  is placed between A and B at a distance of 20cm from A. find the net force on C **An(-643.2N)**
2. Two point charges of  $5\mu\text{C}$  and  $2\mu\text{C}$  are placed in liquid of relative permittivity 9 at distance 5cm apart. Calculate the force between them. **An(3.998N)**
3. Two insulating metal spheres each of charge  $5 \times 10^{-8}\text{C}$  are separated by distance of 6cm. What is the force of repulsion if;
  - (a) The spheres are in air **An(0.00625N)**
  - (b) The spheres are in air with the charge in each sphere doubled and their distance apart is halved **An(0.1N)**
  - (c) The two sphere are placed in water whose dielectric constant is 81 **An(7.7 x 10<sup>-5</sup> N)**

4.

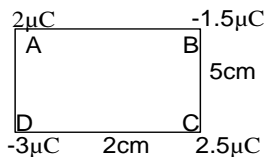

Find the resultant force at charge B. **An(12.58N at 88.5° to the horizontal)**

5.

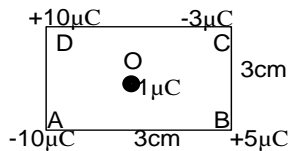

Calculate the resultant force at charge O, where O is the mid- point of the square **An(523.166N at 46.8° to the horizontal)**

## ELECTRIC FIELD


An electric field is a region within which an electric force is experienced.  
Electric fields can be represented by electric field line.

### Definition

An electric field line is the path taken by a small positive charge placed in the field
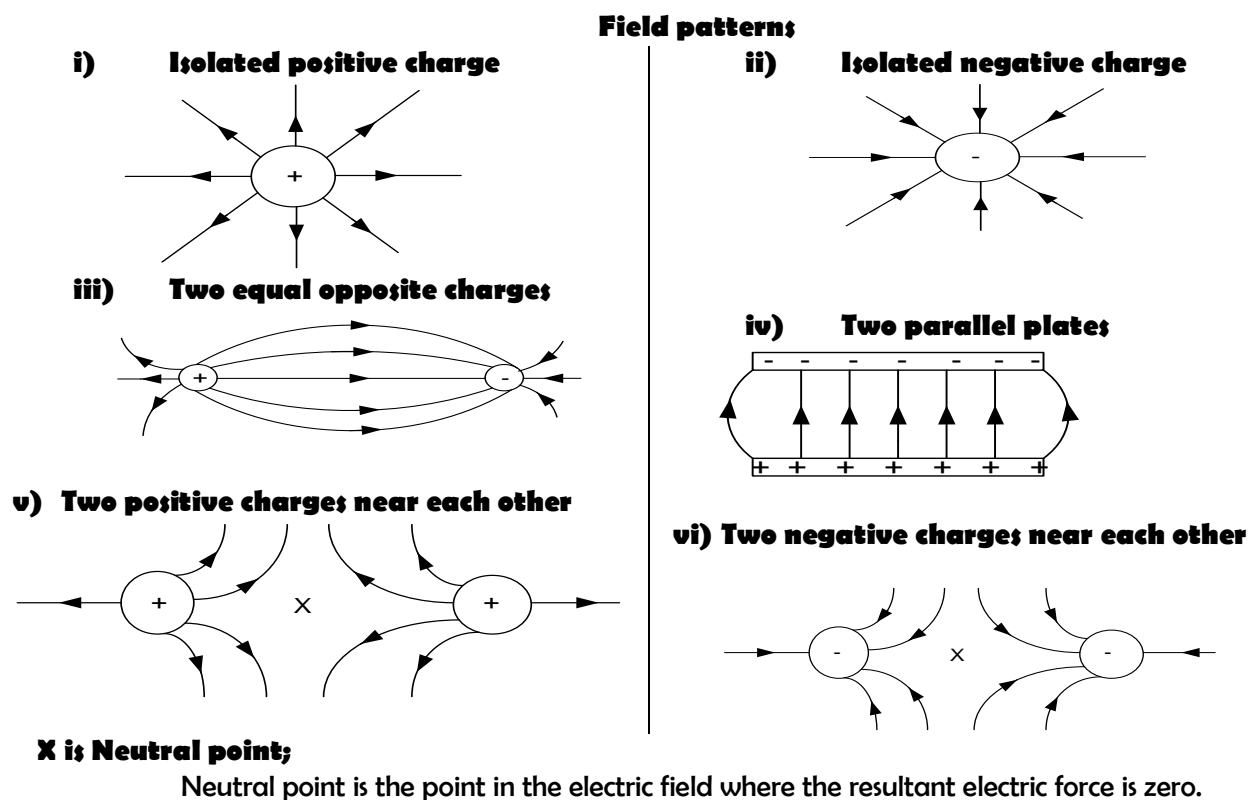
### Properties of electric field lines

- ❖ They originate from positive and end on negative.
- ❖ they are in a state of tension which causes them to shorten
- ❖ they repel one another side ways
- ❖ they travel in straight lines and never cross each other
- ❖ the number of field lines originating or terminating on a charge is proportional to the magnitude of the charge



**Explain what happens to the potential energy as two point charges of the same sign are brought together**

- ❖ Like charges repel. Work has to be done against the repulsive forces between them to bring them closer
- ❖ This work is stored as electric potential energy of the system
- ❖ The potential energy of the two like charges therefore increases when the charges are brought closer together

### ELECTRIC FIELD INTENSITY/ ELECTRIC FIELD STRENGTH

Electric field intensity at a point is the force experienced by a positive one coulomb charge placed in an electric field.

$$E = \frac{F}{Q}$$

Generally

$$E = \frac{Q}{4\pi\epsilon r^2}$$

But in air

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$$

$$\frac{1}{4\pi\epsilon_0} = 9 \times 10^9$$


$$E = \frac{9 \times 10^9 Q}{r^2}$$

S.I unit of electric field intensity is  $\text{NC}^{-1}$  or  $\text{Vm}^{-1}$

Electric field intensity is a vector quantity and therefore direction is important. The direction of E is radially outwards if the point charge is positive and radially inwards if the point charge is negative

### Examples

1.

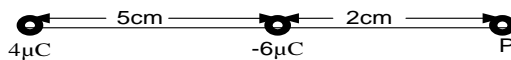

Find Electric field intensity at P

**Solution**

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$E_4 = \frac{9 \times 10^9 \times 4 \times 10^{-6}}{0.07^2}$$

$$E_4 = 7.347 \times 10^6 \text{ NC}^{-1} \text{ towards the right}$$


$$E_6 = \frac{9 \times 10^9 \times 6 \times 10^{-6}}{0.02^2}$$

$$E_6 = 1.35 \times 10^8 \text{ NC}^{-1} \text{ towards the left}$$

$$E = 1.35 \times 10^8 - 7.347 \times 10^6$$

$$E = 1.2765 \times 10^8 \text{ NC}^{-1} \text{ Towards left}$$

2.

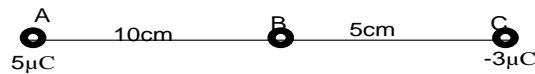

Find electric field intensity at B

**Solution**

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$E_A = \frac{9 \times 10^9 \times 5 \times 10^{-6}}{0.1^2}$$

$$E_A = 4.5 \times 10^6 \text{ NC}^{-1} \text{ towards the right}$$


$$E_C = \frac{9 \times 10^9 \times 3 \times 10^{-6}}{0.05^2}$$

$$E_C = 10.8 \times 10^6 \text{ NC}^{-1} \text{ towards the right}$$

$$E = 10.8 \times 10^6 + 4.5 \times 10^6$$


$$E = 15.3 \times 10^6 \text{ NC}^{-1} \text{ Towards Right}$$

3.

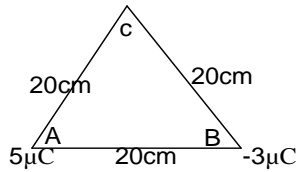

Find electric field intensity at B

**Solution**

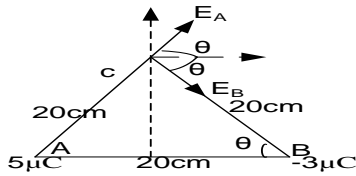

$$\cos\theta = \frac{10}{20}$$

$$\theta = \cos^{-1}\left(\frac{1}{2}\right) = 60^\circ$$

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$E_A = \frac{9 \times 10^9 \times 5 \times 10^{-6}}{0.2^2}$$


$$E_A = 1.125 \times 10^6 \text{ NC}^{-1}$$

$$E_B = \frac{9 \times 10^9 \times 3 \times 10^{-6}}{0.2^2}$$

$$E_B = 6.75 \times 10^5 \text{ NC}^{-1}$$

$$E = \begin{pmatrix} 1.125 \times 10^6 \cos 60 \\ 1.125 \times 10^6 \sin 60 \end{pmatrix} + \begin{pmatrix} 6.75 \times 10^5 \cos 60 \\ -6.75 \times 10^5 \sin 60 \end{pmatrix}$$
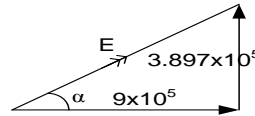
$$E = \begin{pmatrix} 9.0 \times 10^5 \\ 3.8971 \times 10^5 \end{pmatrix}$$



$$E^2 = (9.0 \times 10^5)^2 + (3.8971 \times 10^5)^2$$


$$E = 9.81 \times 10^5 \text{ NC}^{-1}$$

$$\tan\alpha = \frac{3.8971 \times 10^5}{9.0 \times 10^5}$$


$$\alpha = 23.4^\circ$$

Resultant electric field is  $9.81 \times 10^5 \text{ NC}^{-1}$  at  $23.4^\circ$  to the horizontal

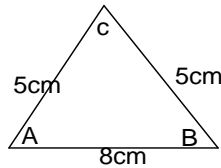4. Two point charges A and B of charges  $0.10 \mu\text{C}$  and  $0.05 \mu\text{C}$  respectively placed 8 cm apart as shown below



**Solution**

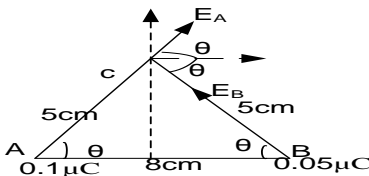

$$\cos\theta = \frac{4}{5}$$

$$\theta = \cos^{-1}\left(\frac{4}{5}\right) = 36.9^\circ$$

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$E_A = \frac{9 \times 10^9 \times 0.1 \times 10^{-6}}{0.05^2}$$


$$E_A = 3.6 \times 10^5 \text{ NC}^{-1}$$

$$E_B = \frac{9 \times 10^9 \times 0.05 \times 10^{-6}}{0.05^2}$$

$$E_B = 1.8 \times 10^5 \text{ NC}^{-1}$$

$$E = \begin{pmatrix} 3.6 \times 10^5 \cos 36.9 \\ 3.6 \times 10^5 \sin 36.9 \end{pmatrix} + \begin{pmatrix} -1.8 \times 10^5 \cos 36.9 \\ 1.8 \times 10^5 \sin 36.9 \end{pmatrix}$$
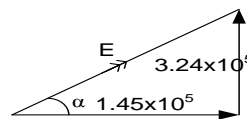
$$E = \begin{pmatrix} 1.45 \times 10^5 \\ 3.24 \times 10^5 \end{pmatrix}$$



$$E^2 = (1.45 \times 10^5)^2 + (3.24 \times 10^5)^2$$


$$E = 3.55 \times 10^5 \text{ NC}^{-1}$$

$$\tan\alpha = \frac{3.24 \times 10^5}{1.45 \times 10^5}$$

$$\alpha = 65.89^\circ$$


Resultant electric field is  $3.55 \times 10^5 \text{ NC}^{-1}$  at  $65.89^\circ$  to the horizontal

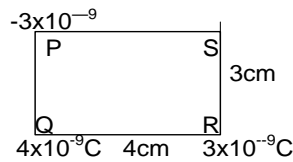5. Three charges  $-3 \times 10^{-9} \text{ C}$ ,  $3 \times 10^{-9} \text{ C}$  and  $4 \times 10^{-9} \text{ C}$  are placed in a vacuum at the vertices PRQ respectively at rectangle PQRS of sides 3 cm by 4 cm as shown below



Calculate the resultant electric field strength at S

**Solution**

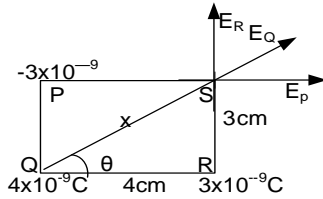


$$x^2 = 4^2 + 3^2$$

$$x = \sqrt{25} = 5\text{cm}$$

$$\tan\theta = \frac{3}{4}$$

$$\theta = 36.9^\circ$$
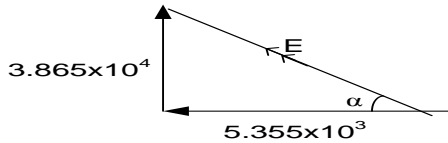
$$E = \begin{pmatrix} -5.355 \times 10^3 \\ 3.865 \times 10^4 \end{pmatrix}$$



$$E^2 = (-5.355 \times 10^3)^2 + (3.865 \times 10^4)^2$$

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$E_P = \frac{9 \times 10^9 \times 3 \times 10^{-9}}{0.04^2}$$

$$E_P = 1.687 \times 10^4 \text{NC}^{-1} \text{ towards left}$$

$$E_R = \frac{9 \times 10^9 \times 3 \times 10^{-9}}{0.03^2}$$

$$E_R = 3 \times 10^4 \text{NC}^{-1} \text{ upwards}$$

$$E_Q = \frac{9 \times 10^9 \times 4 \times 10^{-9}}{0.05^2}$$

$$E_Q = 1.44 \times 10^4 \text{NC}^{-1}$$

$$E = \begin{pmatrix} -1.687 \times 10^4 \\ 0 \end{pmatrix} + \begin{pmatrix} 0 \\ 3 \times 10^4 \end{pmatrix} + \begin{pmatrix} 1.44 \times 10^4 \cos 36.9 \\ 1.44 \times 10^4 \sin 36.9 \end{pmatrix}$$

$$E = 3.9 \times 10^4 \text{NC}^{-1}$$


$$\tan\alpha = \frac{3.865 \times 10^4}{5.355 \times 10^3}$$

$$\alpha = 82.11^\circ$$

Resultant electric field is  $3.9 \times 10^4 \text{NC}^{-1}$  at  $82.11^\circ$  to the horizontal

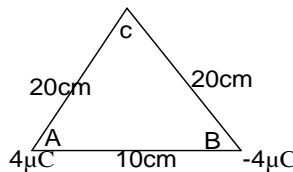**Exercise**


- The electric field intensity at the surface of the earth is about  $1.2 \times 10^2 \text{Vm}^{-1}$  at points towards the centre of the earth. Assuming that the earth is sphere of radius  $6.4 \times 10^6 \text{m}$ . Find the charge held by the earth surface **An**( $5.46 \times 10^5 \text{C}$ ).
- Two point charges  $+4\mu\text{C}$  and  $-4\mu\text{C}$  are placed 10cm apart in air.



Find the electric field intensity at point C which is a distance of 20cm from each charge.

**An**( $4.5 \times 10^5 \text{NC}^{-1}$ ).


3.

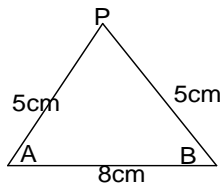

The point charges A and B of charges  $+0.10 \mu\text{C}$  and  $+0.05 \mu\text{C}$  are separated by a distance of 8.0 cm along the horizontal as shown above. Find the electric field intensity at P.


**An**( $3.55 \times 10^5 \text{NC}^{-1}$  at  $66^\circ$  to horizontal).

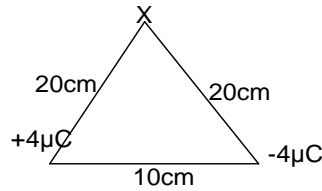4. Two point charges  $+4.0\mu\text{C}$  and  $-4.0\mu\text{C}$  are separated by  $10.0\text{ cm}$  in air as shown below




Find the electric field intensity at point x a distance of  $20.0\text{ cm}$  from each charge . **An( $4.5 \times 10^5 \text{ NC}^{-1}$  at  $75.52^\circ$  to the horizontal)**

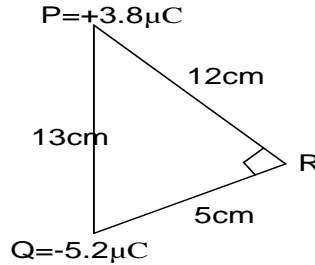5. Two point charges  $+3.8\mu\text{C}$  and  $-5.2\mu\text{C}$  are in air at points P and Q as shown below.



Find the electric field intensity at R. **An( $1.89 \times 10^7 \text{ NC}^{-1}$  at  $7.2^\circ$  to the horizontal)**

6. Find the electric field strength at P

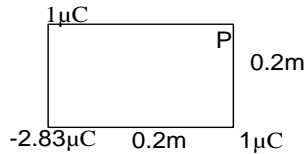


**An( $142.8 \text{ NC}^{-1}$  at  $45^\circ$  to the horizontal)**

7. The electric intensity at the surface of the earth is about  $1.2 \times 10^2 \text{ V m}^{-1}$  and points towards the centre of the earth. Assuming that the earth is a sphere of radius  $6.4 \times 10^6 \text{ m}$ , find the charge held by the earth's surface.
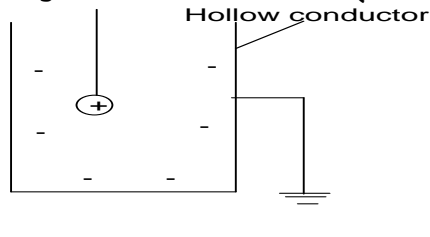
### ELECTROSTATIC SHIELDING OR SCREENING

It is the creation of an electrically neutral space in the neighborhood of an electric field however strong it is by enclosing it in a hollow conductor (faraday cage)



- ❖ The charged body is enclosed in a hollow conductor which is earthed.
- ❖ Equal but opposite charge is induced on the inner walls of the hollow conductor
- ❖ Electric field outside will not affect the charged body inside the conductor

### ELECTRIC FLUX $\Phi$

This is the product of electric field strength at any point and area normal to the field

$$\Phi = AE$$

### TOTAL ELECTRIC FLUX

Consider a spherical surface of radius concentric with point charge

$$E = \frac{Q}{4\pi\epsilon r^2}$$

But  $\Phi = AE$

$$\phi = A \frac{Q}{4\pi\epsilon r^2}$$

But  $A = 4\pi r^2$

$$\phi = 4\pi r^2 \frac{Q}{4\pi\epsilon r^2}$$

$$\phi = \frac{Q}{\epsilon}$$
 This is called Guass's law of electrostatics

Guass's theorem of electrostatic states that the total electric flux passing normally through a closed surface, whatever its shape is always constant

### Electric field intensity due to hollow charged sphere


(i) Outside the sphere

Since  $E = \frac{Q}{4\pi\epsilon_0 r^2}$  there  $E \propto \frac{1}{r^2}$


(ii) Inside the sphere

No charge resides on the inside of a hollow conductor therefore  $E = 0$
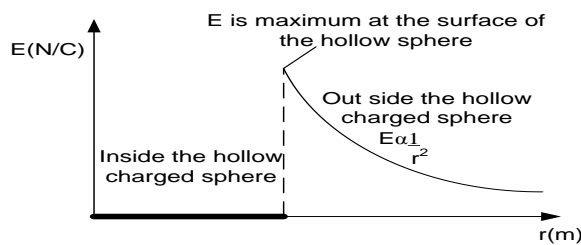
### A graph of E against the distance of a charge from a hollow charged sphere


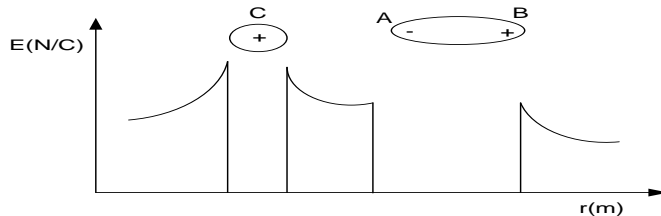
### A graph of E against the distance due to charges




### ELECTRIC POTENTIAL

This is the work done in moving a positive one coulomb charge from infinity to a point against an electric field.
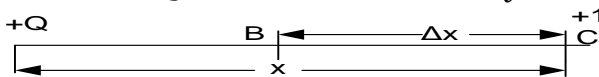
#### Expression for electric potential

Consider  $+1C$  charge  $xm$  away from  $+Q$  being moved from  $C$  to  $B$  through a small displacement  $\Delta x$  without affecting the electric field due to  $+Q$



Force on  $1C$  of charge,  $F = \frac{Q}{4\pi\epsilon x^2}$

Work done to move the charge through  $\Delta x$  against the field is  $\Delta w = -F\Delta x$

Total work done to bring the charge from infinity to a point a distance  $r$  from the charge of

$$w = \int_{\infty}^r -F dx$$

$$= \int_{\infty}^r -\frac{Q}{4\pi\epsilon x^2} dx$$



(c)

$$V_A = \frac{9 \times 10^9 x - 15 \times 10^{-6}}{0.05}$$

$$V_A = -2.7 \times 10^6 V$$

$$W = QV_{AB}$$

$$w = -10 \times 10^{-6} x (-2.7 \times 10^6 - -1.8 \times 10^6)$$

$$W = 9 J$$

### Potential due to hollow charged sphere


(i) Outside the sphere

Since  $V = \frac{Q}{4\pi\epsilon_0 r}$  there  $V \propto \frac{1}{r}$


(ii) Inside the sphere

No charge resides on the inside of a hollow conductor  $E = 0$ , therefore there no work done is done to transfer a charge from the suffice of the sphere to inside hence potential remains constant
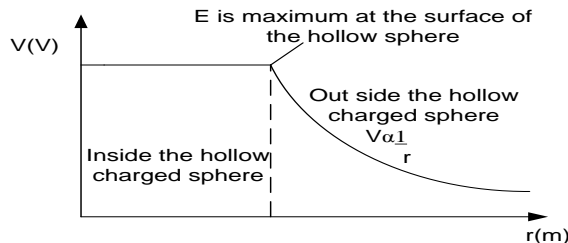
### A graph of V against the distance of a charge from a hollow charged sphere


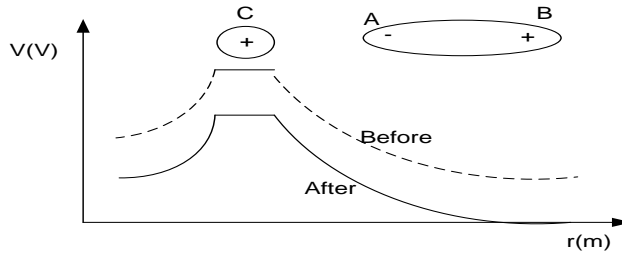
### A graph of V against the distance due to charges




### ELECTRIC POTENTIAL DIFFERENCE

Electric potential difference between two points is the work done to transfer  $+1C$  of charge form one point to the other against an electric field
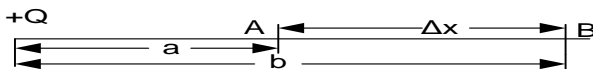
### Expression for electric potential

Consider two points A and B in an electric field which are  $\Delta x m$  apart



Force on  $1C$  of charge,  $F = \frac{Q}{4\pi\epsilon x^2}$

Work done to move the charge through  $\Delta x$  against the field is  $\Delta w = -F\Delta x$

Total work done to move the charge from point A to B

$$w = \int_a^b -F dx$$

$$= \int_a^b -\frac{Q}{4\pi\epsilon x^2} dx$$

$$= -\frac{Q}{4\pi\epsilon} \left[ -\frac{1}{x} \right]_a^b$$

$$= -\frac{Q}{4\pi\epsilon} \left( -\frac{1}{b} - -\frac{1}{a} \right)$$

$$\boxed{V_{AB} = \frac{Q}{4\pi\epsilon} \left( \frac{1}{b} - \frac{1}{a} \right)}$$

### Examples

1. Consider two points A and B at distances of 15.0 cm and 20.0 cm respectively, from a point charge of 6.0  $\mu\text{C}$  as shown below



- (i) Find the electric potential difference between A and B  
(ii) Calculate the energy required to bring a charge of +1.0  $\mu\text{C}$  from infinity to point A

#### Solution

(i)  $V = \frac{Q}{4\pi\epsilon_0 r}$

$$V_A = \frac{6.0 \times 10^{-6} \times 9 \times 10^9}{0.15} = 3.6 \times 10^5 \text{ V}$$

$$V_B = \frac{6.0 \times 10^{-6} \times 9 \times 10^9}{0.2} = 2.70 \times 10^5 \text{ V}$$

$$V_{AB} = V_A - V_B$$

$$V_{AB} = 3.6 \times 10^5 - 2.7 \times 10^5$$


$$V_{AB} = 9.0 \times 10^4 \text{ V}$$

(ii)  $W = QV_A$

$$W = 1.0 \times 10^{-6} \times 3.6 \times 10^5$$

$$W = 0.36 \text{ J}$$

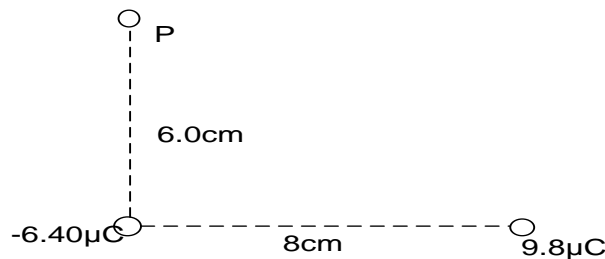2. Consider two point charges 9.8  $\mu\text{C}$  and -6.4  $\mu\text{C}$ , are placed as in figure below in air



Find the potential energy of a charge of 2.5  $\mu\text{C}$  placed at P

#### Solution

$$x^2 = 6^2 + 8^2$$

$$x = 10 \text{ cm}$$

$$V = \frac{Q}{4\pi\epsilon_0 r}$$

$$V_{9.8} = \frac{9.8 \times 10^{-6} \times 9 \times 10^9}{0.1} = 8.82 \times 10^5 \text{ V}$$

$$V_{6.4} = \frac{-6.4 \times 10^{-6} \times 9 \times 10^9}{0.06} = -9.6 \times 10^5 \text{ V}$$

$$V_P = V_{6.4} + V_{9.8}$$

$$V_P = -9.6 \times 10^5 + 8.82 \times 10^5$$


$$V_P = -7.8 \times 10^4 \text{ V}$$

$$P.e = QV_P$$

$$P.e = 2.5 \times 10^{-6} \times -7.8 \times 10^4$$

$$P.e = -0.195 \text{ J}$$

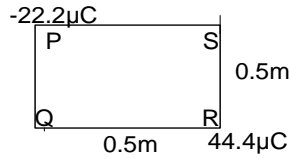3. The figure below shows point charges  $44.4 \mu\text{C}$  and  $-22.2 \mu\text{C}$  placed at the corners of a square of side  $0.5\text{m}$  as shown below



Calculate;

- (i) Electric potential at S
- (ii) Potential energy of  $10 \mu\text{C}$  charge placed at S

**Solution**

$$(i) \quad V = \frac{Q}{4\pi\epsilon_0 r}$$

$$V_R = \frac{44.4 \times 10^{-6} \times 9 \times 10^9}{0.5} = 7.99 \times 10^5 \text{V}$$

$$V_P = \frac{-22.2 \times 10^{-6} \times 9 \times 10^9}{0.5} = -3.99 \times 10^5 \text{V}$$

$$V_S = V_R + V_P$$

$$V_S = 7.99 \times 10^5 + -3.99 \times 10^5$$

$$V_S = 4.0 \times 10^5 \text{V}$$


$$(iii) \quad P.e = QV_S$$

$$P.e = 10 \times 10^{-6} \times 4.0 \times 10^5$$

$$P.e = 4 \text{J}$$
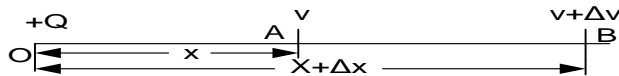
### ELECTRIC POTENTIAL GRADIENT (relation between E and V)

Consider two points A and B in an electric field which are  $\Delta x \text{m}$  apart



If the potential at A is  $v$  and that at B is  $v + \Delta v$ . Then potential difference between A and B is

$$V_{AB} = V_A - V_B$$

$$V_{AB} = v - (v + \Delta v)$$

$$V_{AB} = -\Delta v \dots \dots \dots (1)$$

Work done to move 1C of charge from A to B is equal to p.d and is given by

$$V_{AB} = E \Delta x \dots \dots \dots (2)$$

$$E \Delta x = -\Delta v$$

$$E = \frac{-\Delta v}{\Delta x}$$

Limit as  $\Delta x \rightarrow 0$

$$E = -\frac{dv}{dx}$$

### EQUIPOTENTIAL SURFACES

An equipotential surface is any two dimensional surface over which the electric potential is constant and work done moving charge from one point on surface to another is zero


The direction of force is always at right angles to equipotential surfaces. This implies that there is no component of electric field inside the surface

### Properties of equipotential surface

- ❖ Work done along an equipotential surface is zero
- ❖ Electric field intensity along surfaces is zero
- ❖ The surfaces are at right angles to the line of force

### Examples

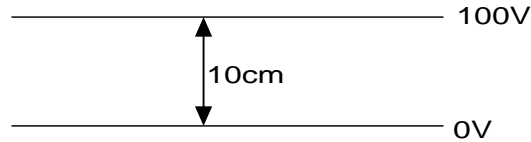1. Calculate the electric field intensity between plates




**Solution**

$$E = \frac{dv}{dx} \quad \Bigg| \quad E = \frac{100 - 0}{0.1} \quad \Bigg| \quad E = 1000Vm^{-1}$$

2. Points A and B are 0.1m apart, a point charge of  $3 \times 10^{-9}C$  is placed at A and another point charge  $-1 \times 10^{-9}C$  is placed at B. X is a point on straight line through A and B but between A and B where electric potential is zero. Calculate the distance AX

**Solution**

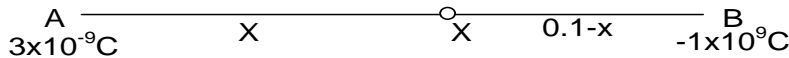


$$V = \frac{Q}{4\pi\epsilon_0 r}$$

$$0 = 9 \times 10^9 \times 3 \times 10^{-9} \times \left( \frac{3}{x} - \frac{1}{0.1 - x} \right)$$


$$x = 0.075m$$

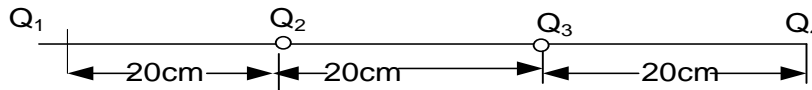**Exercise**


- Two point charge  $3 \times 10^{-9}C$  and  $-1 \times 10^{-9}C$  are placed at points A and B respectively. A and B are 0.2m apart and x is a point on a straight line through A and B but between A and B. Calculate distance BX for which electric potential at x is zero. **An(0.15m)**
- The figure shows charges  $Q_1, Q_2, Q_3,$  and  $Q_4,$  of  $-1\mu C, 2\mu C, -3\mu C$  and  $4\mu C$  are arranged on a straight line in vacuum



- Calculate potential energy at  $Q_2$  **An( $-1.8 \times 10^{11}J$ )**
  - what is the significance of the sign of the potential energy above
- Alpha particles of charge  $2e$  each having kinetic energy  $1.0 \times 10^{-12}J$  are incident head on, on a gold nuclide of charge  $79e$  in a gold foil. Calculate the distance of closest approach of an alpha particle and gold foil. ( $e = 1.6 \times 10^{-19}C$ ) **An( $3.64 \times 10^{-14}m$ )**
  - The figure shows charges  $Q_1, Q_2,$  and  $Q_3,$  of  $5\mu C, 6\mu C,$  and  $-20\mu C$  are arranged on a straight line in vacuum

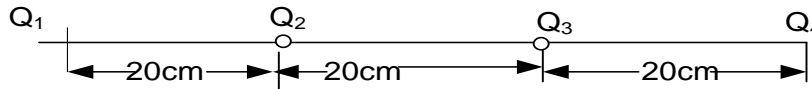


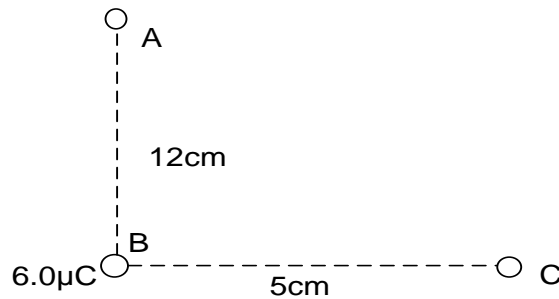- Calculate electric field intensity midway between  $Q_1$  and  $Q_2,$  **An( $4.44 \times 10^6Vm^{-1}$ )**
  - Calculate electric potential midway between  $Q_1$  and  $Q_2,$  **An( $7.85 \times 10^5V$ )**
- Consider two points A and C at distances of 12.0 cm and 5.0 cm respectively, from a point charge of  $6.0 \mu C$  situated at B as shown below



Calculate the energy required to bring a charge of  $+2.0 \mu\text{C}$  from A to point C. **An (1.26J)**

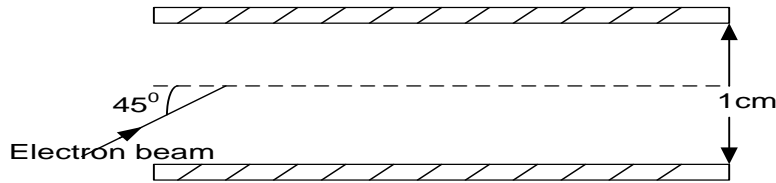6. Two large oppositely charged plates are fixed  $1.0 \text{ cm}$  apart as shown below. The p.d between the plates is  $50\text{V}$ .




An electron beam enters the region between the plates at an angle of  $45^\circ$  as shown. Find the maximum speed the electrons must have in order for them not to strike the upper plate

[Mass of an electron =  $9.11 \times 10^{-31} \text{ kg}$ .]

7. A conducting sphere of radius  $9.0 \text{ cm}$  is maintained at an electric potential of  $10\text{kV}$ . Calculate the charge on the sphere. **An( $1 \times 10^{-7} \text{ C}$ )**

### Uneb 2016

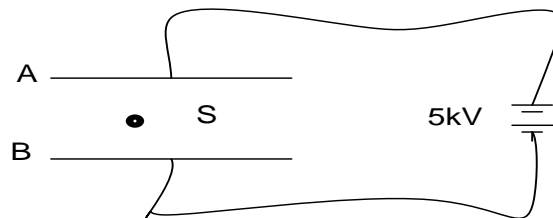- (a) (i) Explain an equipotential surface. (04marks)  
 (ii) Give an example of an equipotential surface. (01mark)
- (b) (i) State **coulomb's law**. (01mark)  
 (ii) With the aid of a sketch diagram, explain the variation of electric potential with distance from the centre of a charged metal sphere. (03marks)  
 (iii) Two metal plates A and B,  $30\text{cm}$  apart are connected to a  $5\text{kV}$  d.c supply as shown below




When a small charged sphere, S, of mass  $9.0 \times 10^{-3} \text{ kg}$  is placed between the plates, it remains stationary. Indicate the forces acting on the sphere and determine the magnitude of the charge on the sphere. (04marks)

- (c) (i) Define **electric field intensity** (01mark)  
 (ii) With the aid of a diagram, explain electrostatic shielding. (04marks)
- (d) Explain briefly a neutral metal body is attracted to a charged body when brought near it. (02marks)

### Uneb 2015

- (a) (i) Define **electric potential** (01mark)  
 (ii) Derive an expression for the electric potential at a point of a distance  $r$ , from a fixed charge. (04marks)

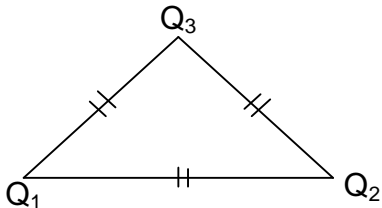- (b) With reference to a charged pear-shaped conductor.
- (i) Describe an experiment to show the distribution of charge on it. (03marks)
  - (ii) Show that the surface of the conductor is an equipotential surface. (03marks)
- (c) Explain how a lightning conductor protects a house from lightning. (04marks)
- (d) Three charges  $Q_1$ ,  $Q_2$  and  $Q_3$  of magnitude  $2\mu C$ ,  $-3\mu C$ , and  $5\mu C$  respectively are situated at corners of an equilateral triangle of sides 15cm as shown below.



Calculate the net force on  $Q_3$ .

(05marks)

## CAPACITORS


A capacitor is a device which stores charge

A capacitor consists of a pair of oppositely charged plates separated by an insulator called a dielectric.


A dielectric is an insulator which breaks down when the potential difference is very high

The dielectric is can be air, oil, glass or a paper

The symbol of a capacitor is

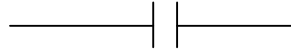

### Charging and Discharging process

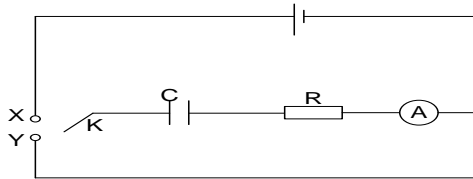


- ❖ When switch k is brought to contact x, the capacitor, c charges. Current flowing through

the ammeter is initially high but slowly comes to zero with time when the capacitor is fully charged

- ❖ If switch k is brought in contact with y, capacitor c is discharged. The current is initially high but eventually comes to zero and in opposite direction to that when the capacitor is being charged.

### Explanation of charging process

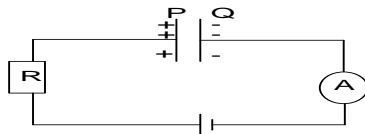


- ❖ When the capacitor is connected to a battery, electrons flow from the negative terminal of the battery to the adjacent plate of the capacitor and at the same rate electrons flow from plate P of the capacitor towards the



positive terminal of the battery leaving positive charges at P.

- ❖ Positive and negative charges therefore appear on the plate and oppose the flow of electrons that cause them
- ❖ As charge accumulates the p.d between the plates increase and charge current falls to zero when the p.d between the plates of the capacitor is equal to battery voltage

### Explanation of discharging process

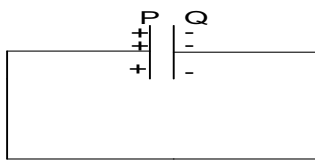

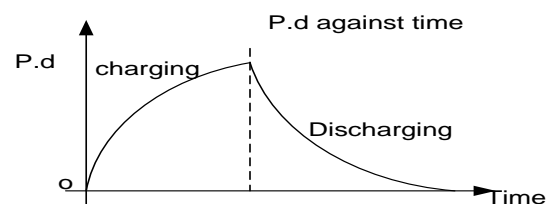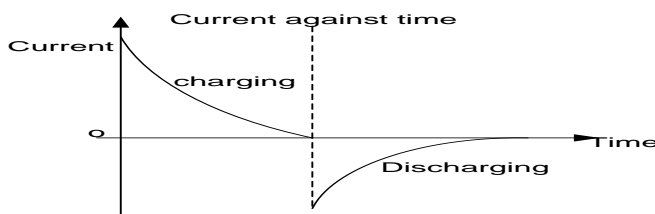Connect a wire from the positive plate to the negative plate. Electrons flow from the negative plate to positive plate through wire until the p.d is zero. The capacitor is fully discharged



**Note**

Energy changes in charging a capacitor include Chemical energy is changed to heat and electrical energy which is stored in the plates of the capacitor.

**Capacitance of capacitor**

This is the ratio of the magnitude of charge on either of the plates of a capacitor to the p.d between the plates of the capacitor

$$C = \frac{Q}{V}$$

The S.I unit of capacitance is farad, F

**Definition**

The farad is the capacitance of the capacitor when one coulomb of charge changes its potential difference by one volt.

**Examples**

Given the capacitance of capacitor of  $4\mu\text{F}$  and charge on the plate is  $5\mu\text{C}$ . Find the p.d across the plate.

**Solution**


$$C = \frac{Q}{V}$$

$$V = \frac{5 \times 10^{-6}}{4 \times 10^{-6}}$$

$$V = 1.25\text{V}$$

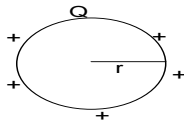**Capacitance of an isolated sphere**

Consider an isolated sphere of radius  $r$ . If the conductor is given charge  $Q$ , then its p.d is



$$V = \frac{Q}{4\pi\epsilon_0 r}$$

Where  $\epsilon_0$  – is permittivity of free space

$$4\pi\epsilon_0 r = \frac{Q}{V}$$

$$C = 4\pi\epsilon_0 r$$

**Example**

Calculate the capacitance of the earth given that the radius of the earth is  $6.4 \times 10^6\text{m}$

**Solution**


$$C = 4\pi\epsilon_0 r$$

$$C = 4 \times 3.14 \times 8.85 \times 10^{-12} \times 6.4 \times 10^6$$

$$C = 7.12 \times 10^{-4}\text{F}$$

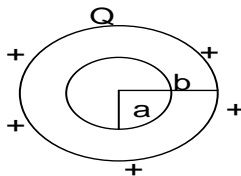**Capacitance of concentric spheres**

Consider two concentric sphere A and B each of radius  $a$  and  $b$  respectively.



$$V = \frac{Q}{4\pi\epsilon_0} \left( \frac{1}{a} - \frac{1}{b} \right)$$

$$\frac{V}{Q} = \frac{1}{4\pi\epsilon_0} \left( \frac{b-a}{ab} \right)$$

$$\frac{Q}{V} = 4\pi\epsilon_0 \left( \frac{ab}{b-a} \right)$$

$$C = 4\pi\epsilon_0 \left( \frac{ab}{b-a} \right)$$

**Example**

- Find the capacitance of concentric spheres of radius 9cm and 10cm. Given that  $\epsilon_0 = 8.85 \times 10^{-12}\text{Fm}^{-1}$

**Solution**

$$C = 4\pi\epsilon_0 \left( \frac{ab}{b-a} \right)$$

$$C = 4 \times 3.14 \times 8.85 \times 10^{-12} \left( \frac{0.1 \times 0.09}{0.1 - 0.09} \right)$$

$$C = 1.0 \times 10^{-10}\text{F}$$

- Given two concentric sphere of radius 5cm and 2cm separated by material of permittivity  $8.0 \times 10^{-11}\text{Fm}^{-1}$ . Calculate it capacitance

**Solution**

$$C = 4\pi\epsilon_0 \left( \frac{ab}{b-a} \right)$$

$$C = 4 \times 3.14 \times 8.0 \times 10^{-11} \left( \frac{0.02 \times 0.05}{0.05 - 0.01} \right)$$

$$C = 3.352 \times 10^{-11} F$$

**Capacitance of a parallel plate capacitor**

Consider two parallel plate of capacitors each having charge Q and an area A separated by a distance d by a dielectric of permittivity  $\epsilon$ . Total electric flux  $\phi$  through the surface is given by:  $\phi = AE$ .....(1)

Where E is electric field intensity

From Gauss law  $\phi = \frac{Q}{\epsilon}$ .....(2)

Equating (1) and (2)  $\frac{Q}{\epsilon} = AE$

But  $E = \frac{V}{d}$

**Example**

4. Calculate the capacitance of a parallel capacitor whose plates are 10 cm by 10 cm separated by an air gap of 5 mm

**Solution**

$$C = \frac{\epsilon_0 A}{d} \quad \left| \quad C = \frac{8.85 \times 10^{-12} \times 0.1 \times 0.1}{0.005} \quad \right| \quad C = 1.77 \times 10^{-11} F$$

5. A parallel plate capacitor consists of two separate plates each of size 25cm and 3.0mm apart. If a p.d of 200V is applied to the capacitor. Calculate the charge in the plates

**Solution**

$$C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{8.85 \times 10^{-12} \times 0.25 \times 0.25}{0.003}$$

$$C = 1.854 \times 10^{-10} F$$

$$C = \frac{Q}{V}$$

$$Q = 1.854 \times 10^{-10} \times 200$$

$$Q = 3.708 \times 10^{-8} C$$

6. The plates of a parallel plate capacitor each of area 2.0 cm<sup>2</sup> are 5 mm apart. The plates are in vacuum and a potential difference of 10,000V is applied across the capacitor. Find the magnitude of the charge on the capacitor.

**RELATIVE PERMITTIVITY / DIELECTRIC CONSTANT**

It is defined as the ratio of capacitance of a capacitor when the insulating material (dielectric) between its plates to the capacitance of the same capacitor with a vacuum between its plates

$$\epsilon_r = \frac{C}{C_0} \dots\dots\dots(1)$$

$$C = \epsilon_r C_0$$

**But**

$C = \frac{\epsilon A}{d}$  and  $C = \frac{\epsilon_0 A}{d}$  put into (1)

$$\epsilon_r = \frac{\left( \frac{\epsilon A}{d} \right)}{\left( \frac{\epsilon_0 A}{d} \right)}$$

$$\epsilon_r = \frac{\epsilon}{\epsilon_0} \dots\dots\dots(2)$$

$$\epsilon = \epsilon_r \epsilon_0$$

Relative permittivity can also be defined as the ratio of the permittivity of a material to permittivity of free space

**Examples**

1. A parallel plate capacitor was charged to 100V and then isolated. When a sheet of a dielectric is inserted between its plates, the p.d decreases to 30V. Calculate the dielectric constant of the dielectric.

**Solution**

By law of conservation of charge

$$Q_0 = Q$$

$$C_0 V_0 = CV$$

$$\frac{V_0}{V} = \frac{C}{C_0}$$

$$\epsilon_r = \frac{100}{30}$$

$$\epsilon_r = 3.33$$

2. A  $2\mu F$  capacitor that can just withstand a p.d of 5000V uses a dielectric with a dielectric constant 6 which breaks down if the electric field strength in it exceeds  $4 \times 10^7 Vm^{-1}$ . Find the;

- (i) Thickness of the dielectric  
(ii) Effective area of each plate  
(iii) Energy stored per unit volume of dielectric

**Solution**

(i)  $E = \frac{V}{d}$

$$4 \times 10^7 = \frac{5000}{d}$$

$$d = 1.25 \times 10^{-4} m$$

(ii)  $C = \frac{\epsilon A}{d}$

$$\epsilon = \epsilon_r \epsilon_0$$

$$2 \times 10^{-6} = \frac{6 \times 8.85 \times 10^{-12} \times A}{1.25 \times 10^{-4}}$$

$$A = 4.71 m^2$$

(iii)  $\frac{\text{Energy}}{\text{volume}} = \frac{\frac{1}{2} CV^2}{Ad}$

$$= \frac{\frac{1}{2} \times 2 \times 10^{-6} \times 5000^2}{4.71 \times 1.25 \times 10^{-4}}$$

$$= 4.246 \times 10^4 Jm^{-3}$$

3. A parallel plate capacitor has an area of  $100 cm^2$ , plate separation of 1cm and charged initially with the p.d of 100V supply, it is disconnected and a slab of dielectric 0.5cm thick and relative permittivity 7 is then placed between plates.

- (a) Before the slab was inserted calculate;
- (i) Capacitance  
(ii) Charge on the plates  
(iii) Electric field strength in the gap between plates
- (b) After the dielectric was inserted, find;
- (i) Electric field strength  
(ii) P.d between the plates  
(iii) capacitance

**Solution**

(a) (i)  $C = \frac{\epsilon_0 A}{d}$

$$C = \frac{8.85 \times 10^{-12} \times 100 \times 10^{-4}}{1 \times 10^{-2}}$$

$$C = 8.85 \times 10^{-12} F$$

(ii)  $Q = CV$

$$Q = 8.85 \times 10^{-12} \times 100$$

$$Q = 8.85 \times 10^{-10} C$$

(iii)  $E = \frac{V}{d}$

$$E = \frac{100}{1 \times 10^{-2}}$$

$$E = 1 \times 10^4 Vm^{-1}$$

(b) (i)  $E = \frac{Q}{\epsilon A}$

$$\epsilon = \epsilon_r \epsilon_0$$

$$E = \frac{8.85 \times 10^{-10}}{7 \times 8.85 \times 10^{-12} \times 100 \times 10^{-4}}$$

$$E = 1.43 \times 10^3 Vm^{-1}$$

(ii)  $E = \frac{V}{d}$

$$1.43 \times 10^3 = \frac{V}{0.5 \times 10^{-2}}$$

$$V = 7.15 V$$

(iii)  $C = \frac{\epsilon A}{d}$

$$\epsilon = \epsilon_r \epsilon_0$$

$$C = \frac{7 \times 8.85 \times 10^{-12} \times 100 \times 10^{-4}}{0.5 \times 10^{-2}}$$

$$C = 1.24 \times 10^{-10} F$$

## DIELECTRIC STRENGTH

It is the maximum electric field intensity an insulator can withstand without conducting

Or It is the maximum potential gradient an insulator can withstand without conducting


## USES OF DIELECTRIC

- ❖ It should increase the capacitance of a capacitor
- ❖ It is used to separate the plates of a capacitor
- ❖ It reduces the chance of dielectric breakdown

## QUALITIES OF GOOD DIELECTRIC

- ❖ It should have a large dielectric constant
- ❖ It should have high dielectric strength

## ACTION OF DIELECTRIC

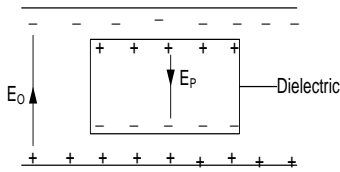

- ❖ The molecules of the insulator get polarized. Charge inside the material cancel each other's

- influence but the surfaces adjacent to the plates develop charge opposite to that on the near plate.
- ❖ Since charges are bound, electric field intensity,  $E_p$  develops between the opposite faces of the insulator in opposition to the applied field,  $E_0$

- ❖ The resultant electric field intensity between the plates is thus reduced. But electric field intensity,  $E = \frac{V}{d}$  thus p.d between the plates reduces, since capacitance,  $C = \frac{Q}{V}$  hence capacitance increases

### Note:


If a conductor instead a dielectric is placed between the plates of a charged capacitor, charge reduces to zero on the plates. This is because electrons move from the negative plate to the positive plate to neutralize the positive charge

## FACTORS THAT AFFECT CAPACITANCE OF A CAPACITOR

Capacitance of a capacitor is affected by;

- (i) Area of overlap of the plates
- (ii) Distance of separation of the plates
- (iii) Dielectric

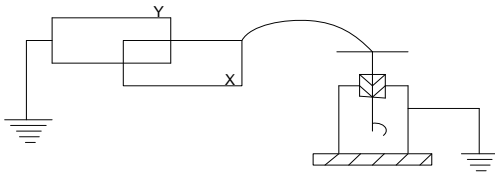
### Experiment to show the effect of area of overlap on capacitance



- ❖ Plate x is charged and divergence of the leaf of the electrostatic induction coil is noted

- ❖ Plate y is then displaced upwards relative to x and the divergence of the leaf of the electrostatic induction coil is seen to increase
- ❖ The p.d between the plates has increased. Since  $C = \frac{Q}{V}$ , capacitance has decreased with decrease in area and  $C \propto A$

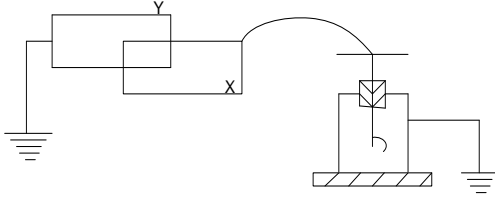
### Experiment to show the effect of plate separation on capacitance



- ❖ XY are metal plates near each other but not touching.

- ❖ Plate x is charged and divergence of the leaf of the electroscope noted
- ❖ Plate y is then moved closer to x and the divergence of the leaf of the electroscope is seen to decrease
- ❖ The p.d between the plates has decreased. Since  $C = \frac{Q}{V}$ , capacitance has increased with decrease plate separation and  $C \propto \frac{1}{d}$

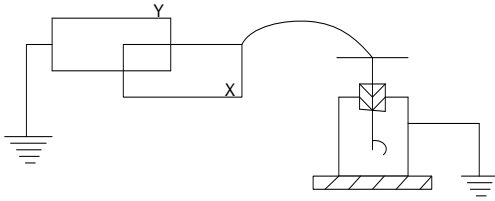
### Experiment to show the effect of dielectric on capacitance



- ❖ XY are metal plates near each other but not touching.

- ❖ Plate x is charged and divergence of the leaf of the electroscope noted
- ❖ Insert a dielectric between the plates and the divergence of the leaf of the electroscope is seen to decrease
- ❖ The p.d between the plates has decreased. Since  $C = \frac{Q}{V}$ , capacitance has increased and  $C \propto \epsilon$
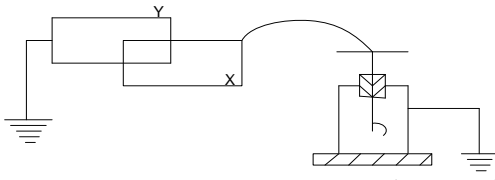
### Investigation of all factors that affect capacitance of a parallel plate capacitor




- ❖ Plate x is charged and divergence of the leaf of the electroscope noted
- ❖ Plate y is then displaced upwards relative to x and the divergence of the leaf of the electroscope is seen to increase. The p.d between the plates has increased. Since  $C = \frac{Q}{V}$ , capacitance has decreased with decrease in area and  $C \propto A$

- ❖ Plate y is now restored to its initial position. Plate y is then moved closer to x and the divergence of the leaf of the electroscope is seen to decrease. The p.d between the plates has decreased. Since  $C = \frac{Q}{V}$ , capacitance has increased with decrease plate separation and  $C \propto \frac{1}{d}$
- ❖ The plates are restored, an insulator inserted between the plates. Divergence of the leaf decreases. Since  $C = \frac{Q}{V}$ , capacitance has increased and  $C \propto \epsilon$

### Measurement of capacitance

#### (a) Using a reed switch

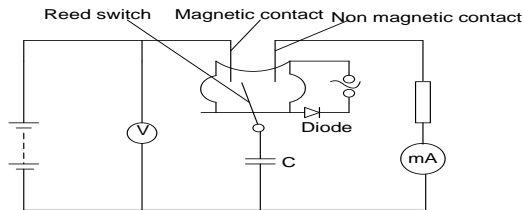

- ❖ The circuit is connected as above

- ❖ The switch is closed, the microammeter reading  $I$  is taken together with the voltmeter reading
- ❖ Knowing the frequency  $f$  of the A.C in the reed switch circuit, the capacitance of the capacitor is calculated from

$$C = \frac{I}{fV}$$

### Example

1. A capacitor filled with a dielectric is charged and then discharged through a milliammeter. The dielectric is then withdrawn half way and the capacitor charged to the same voltage, and discharged through the milliammeter again, show the relative permittivity,  $\epsilon_r$  of the dielectric is given by

$$\epsilon_r = \frac{I}{2I^1 - I}$$

Where  $I$ , and  $I^1$  are the readings of the milliammeter respectively

**Solution**

$$I = cfV$$

$$I = \frac{\epsilon A}{d} fV \dots \dots \dots (i)$$

When the dielectric is withdrawn half way, the area is halved and both portions one with a dielectric and the other with out a dielectric contribute to current.

$$I^1 = \frac{\epsilon AfV}{2d} + \frac{\epsilon_0 AfV}{2d}$$

$$2 I^1 = \frac{\epsilon AfV}{d} + \frac{\epsilon_0 AfV}{d}$$

$$2 I^1 = I + \frac{\epsilon_0 AfV}{d}$$

$$2 I^1 - I = \frac{\epsilon_0 AfV}{d} \dots \dots \dots (ii)$$


eq (i) ÷ (ii)

$$\frac{I}{2 I^1 - I} = \frac{\frac{\epsilon AfV}{d}}{\frac{\epsilon_0 AfV}{d}}$$

$$\frac{I}{2 I^1 - I} = \frac{\epsilon}{\epsilon_0} = \epsilon_r$$

$$\epsilon_r = \frac{I}{2 I^1 - I}$$


**(b) Using a Ballistic galvanometer**

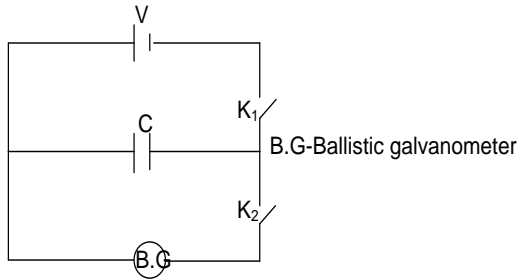

❖ The circuit is connected as shown above

- ❖ First with a standard capacitor of capacitance,  $C_s$  switch  $K_1$  is closed and after a short time it is opened
- ❖ Switch  $K_2$  is now closed and the deflection of B.G,  $\theta_s$  is noted
- ❖ The capacitor is replaced with the test capacitor of capacitance C and the procedure repeated. The deflection,  $\theta$  of B.G is noted
- ❖ Capacitance, C is calculated from  $C = \frac{\theta}{\theta_s} C_s$

**Comparing capacitance using B.G**

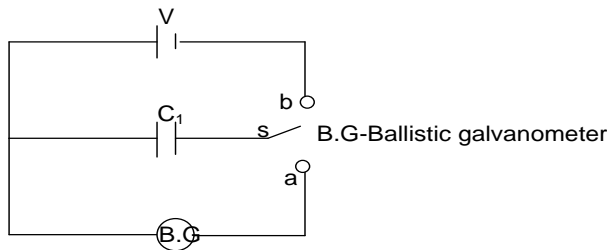


❖ The capacitor of capacitance  $C_1$  is charged by connecting  $s$  to b. After sufficiently charging,  $s$

- is now connected to a. The deflection  $\theta_1$  of the B.G is noted
- ❖ The capacitor of capacitance  $C_1$  is then replaced by one of capacitance  $C_2$
- ❖ The capacitor is charged by connecting  $s$  to b. It is then discharged through a B.G by connecting  $s$  to a. The deflection  $\theta_2$  of the B.G is noted

Then  $\frac{C_1}{C_2} = \frac{\theta_1}{\theta_2}$

**CAPACITOR NETWORKS**

**(a) Capacitors in parallel**

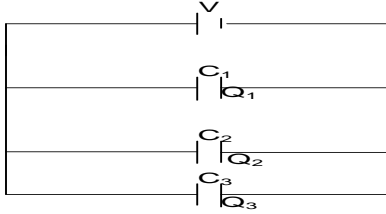

For capacitors connected in parallel p.d across the plate of capacitors is the same

$$Q = Q_1 + Q_2 + Q_3$$

But  $Q_1 = C_1V, Q_2 = C_2V$  and  $Q_3 = C_3V$


$$Q = C_1V + C_2V + C_3V$$

$$\frac{Q}{V} = C_1 + C_2 + C_3$$

but  $\frac{Q}{V} = C$

$$C = C_1 + C_2 + C_3$$

**(b) Capacitors in series**

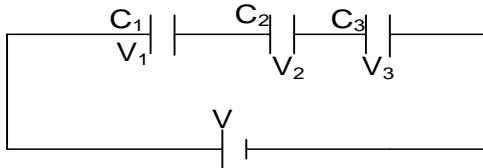

For capacitors connected in series charge stored on the plates of capacitor is the same

$$V = V_1 + V_2 + V_3$$

But  $V_1 = \frac{Q}{C_1}, V_2 = \frac{Q}{C_2}$  and  $V_3 = \frac{Q}{C_3}$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$


$$\frac{V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

but  $\frac{V}{Q} = \frac{1}{C}$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

**Examples**

1.

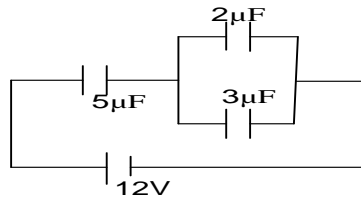

A battery of *emf* 12V is connected across a system of capacitor. Calculate the total energy stored in capacitor network.

**Solution**

$$C_p = 2\mu F + 3\mu F$$

$$C_p = 5\mu F$$

$$\frac{1}{C} = \frac{1}{C_5} + \frac{1}{C_p}$$

$$\frac{1}{C} = \frac{1}{5} + \frac{1}{5}$$

$$\frac{1}{C} = \frac{2}{5+2}$$

$$\frac{1}{C} = \frac{2}{2x5}$$


$$C = 2.5\mu F$$

$$\text{Energy stored} = \frac{1}{2}CV^2$$

$$\text{Energy stored} = \frac{1}{2} \times 2.5 \times 10^{-6} \times 12^2$$

$$\text{Energy stored} = 1.8 \times 10^{-4} J$$

2.

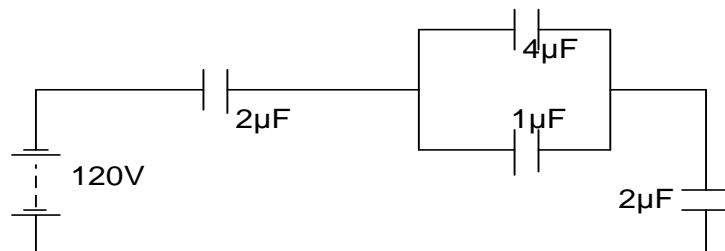

The diagram above shows a network of capacitors connected to a 120V supply. Calculate the;

- (i) Charge on the  $4\mu F$  capacitor  
(ii) Energy stored in  $1\mu F$  capacitor

**Solution**

$$C_p = 4\mu F + 1\mu F$$

$$C_p = 5\mu F$$

$$\frac{1}{C} = \frac{1}{C_2} + \frac{1}{C_p} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{2} + \frac{1}{5} + \frac{1}{2}$$

$$\frac{1}{C} = \frac{1}{6} + \frac{1}{5}$$

$$C = \frac{5}{6}\mu F$$

Total charge flowing in the circuit,  $Q = CV$

$$Q = \frac{5}{6} \times 10^{-6} \times 120$$

$$Q = 1.0 \times 10^{-4} C$$

p.d across the parallel combination;  $V_p = \frac{Q}{C}$

$$V = \frac{1.0 \times 10^{-4}}{5 \times 10^{-6}}$$

$$V = 20V$$

Charge on  $4\mu F$  Capacitor  $Q_4 = CV$

$$Q_4 = 4 \times 10^{-6} \times 20$$


$$Q_4 = 8.0 \times 10^{-5} C$$

Energy stored  $1\mu F$  Capacitor  $= \frac{1}{2} CV^2$

$$\text{Energy stored} = \frac{1}{2} \times 1 \times 10^{-6} \times 20^2$$

$$\text{Energy stored} = 2 \times 10^{-4} J$$

3.

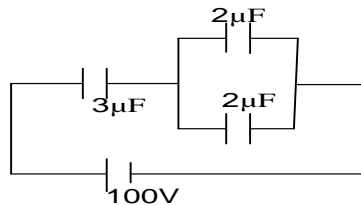

Calculate energy stored in a system of capacitors, if the space between the  $3\mu F$  is filled with an insulator of dielectric constant 3 and capacitors are fully charged

**Solution**

$$C_p = 2\mu F + 2\mu F$$

$$C_p = 4\mu F$$

$$C_3' = \epsilon_r C_0$$

$$C_3' = 3 \times 3\mu F$$

$$C_3' = 9\mu F$$

$$\frac{1}{C} = \frac{1}{C_3'} + \frac{1}{C_p}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{4}$$

$$\frac{1}{C} = \frac{4 + 9}{9 \times 4}$$

$$C = \frac{36}{13} \mu F$$

$$\text{Energy stored} = \frac{1}{2} CV^2$$

$$\text{Energy stored} = \frac{1}{2} \times \frac{36}{13} \times 10^{-6} \times 12^2$$

$$\text{Energy stored} = 13.8 \times 10^{-3} J$$

4. A  $47\mu F$  capacitor is used to power the flash gun of a camera. The average power output of the gun is  $4.0kW$  for a duration of the flash which is  $2.0ms$ . Calculate the;

- (i) Potential difference between the terminals of the capacitor immediately before a flash  
(ii) Maximum charge stored by the capacitor  
(iii) Average current provided by the capacitor during a flash

**Solution**

$$\frac{1}{2} CV^2 = pt$$

$$\frac{1}{2} \times 47 \times 10^{-6} \times (V)^2$$

$$= 4 \times 10^3 \times 2 \times 10^{-3}$$

$$V = 583.5V$$

$$Q = CV$$

$$Q = 47 \times 10^{-6} \times 583.5$$


$$Q = 2.74 \times 10^{-2} C$$

$$I = \frac{Q}{t}$$

$$I = \frac{2.74 \times 10^{-2}}{2 \times 10^{-3}}$$

$$I = 13.7A$$

5.

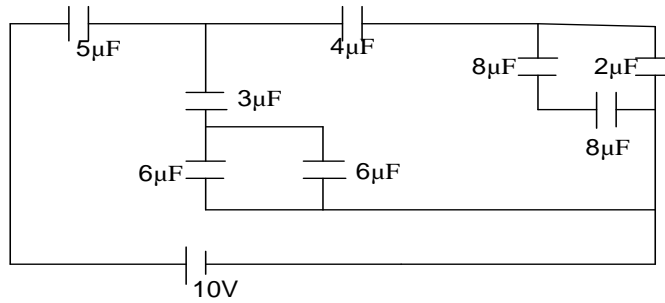

The figure above shows a network of capacitors connected to a 10V battery. Calculate the total energy stored in the network.

**Solution**

$8\mu F$  and  $8\mu F$  are in series

$$\frac{1}{C} = \frac{1}{8} + \frac{1}{8}$$

$$\frac{1}{C} = \frac{1}{8+8}$$

$$C = 4\mu F$$

$2\mu F$  is in parallel with  $4\mu F$


$$C = 4 + 2$$

$$C = 6\mu F$$

$6\mu F$  is in parallel with  $6\mu F$

$$C = 6 + 6$$

$$C = 12\mu F$$

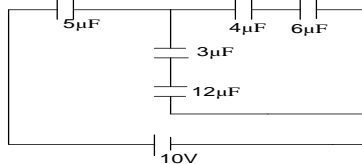

$4\mu F$  and  $6\mu F$  are in series

$$\frac{1}{C} = \frac{1}{4} + \frac{1}{6}$$

$$\frac{1}{C} = \frac{1}{4+6}$$

$$C = \frac{4 \times 6}{12}$$

$$C = \frac{12}{5} \mu F$$

$3\mu F$  and  $12\mu F$  are in series

$$\frac{1}{C} = \frac{1}{3} + \frac{1}{12}$$

$$\frac{1}{C} = \frac{1}{3+12}$$

$$C = \frac{3 \times 12}{15}$$

$$C = \frac{12}{5} \mu F$$

$$C_p = \frac{12}{5} \mu F + \frac{12}{5} \mu F$$

$$C_p = \frac{24}{5} \mu F$$

$$\frac{1}{C} = \frac{1}{C_5} + \frac{1}{C_p}$$

$$\frac{1}{C} = \frac{1}{5} + \frac{1}{\left(\frac{24}{5}\right)}$$

$$\frac{1}{C} = \frac{24}{5} + 5$$

$$C = \frac{120}{49} \mu F$$

$$\text{Energy stored} = \frac{1}{2} CV^2$$

$$E = \frac{1}{2} \times \frac{120}{49} \times 10^{-6} \times 10^2$$

$$E = 1.224 \times 10^{-4} J$$

**ENERGY STORED IN A CAPACITOR**

Suppose the p.d between the plates at some instant was  $V$ . When a small charge of  $+\delta q$  is transferred from the negative plate to the positive plate, the p.d increases by  $\delta v$ .

Work done to transfer charge,

$$\delta w = (V + \delta v)\delta q$$

$$\delta w \approx V\delta q$$

But  $V = \frac{q}{C}$

$$\delta w = \frac{q}{C} \delta q$$

Total work done to charge the capacitor to  $Q$  is

$$W = \int_0^Q \frac{q}{C} dq$$

$$= \frac{1}{2} \frac{Q^2}{C}$$


but  $Q = CV$

$$W = \frac{1}{2} CV^2$$

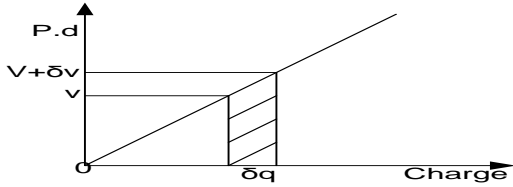**ALTERNATIVELY**

From  $q = CV$

$V$  is proportional to  $q$ , giving a graph of  $v$  against  $q$



Area of the shaded part =  $\frac{1}{2}(V + V + \delta v)\delta q$   
 =work done to increase charge on the capacitor from  $q = 0$  to  $q = Q$

Work done  $w = \text{average voltage} \times \text{charge}$

$$= \frac{1}{2}(0 + V)Q$$

$$= \frac{1}{2}QV$$

but  $Q = CV$

$$W = \frac{1}{2}CV^2$$

### JOINING TWO CAPACITORS

When two capacitors are joined together;

- ❖ Charge flows until p.d across the capacitors is the same
- ❖ Total charge on the circuit is conserved
- ❖ Capacitors are in parallel ie  $C = C_1 + C_2$

### NOTE

There is loss of energy when capacitors are joined together. This is because charge flows until the p.d across the capacitor is the same. The flow of charge results in heating of the wire and hence loss in energy

### Examples

- b. A  $5\mu F$  capacitor is charged by a 40V supply and then connected to an un charged  $20\mu F$  capacitor. Calculate;

- (i) Final p.d across each capacitor
- (ii) Final charge on each
- (iii) Energy lost

#### Solution

$$(i) \quad C = C_1 + C_2$$

$$C = 5 \times 10^{-6} + 20 \times 10^{-6}$$

$$C = 2.5 \times 10^{-5} F$$

Charge before = charge after connection

$$Q_1 + Q_2 = Q$$

$$C_1 V_1 + C_2 V_2 = CV$$

$$5 \times 10^{-6} \times 40 + 20 \times 10^{-6} \times 0 = 2.5 \times 10^{-5} V$$

$$V = 8V$$

$$(ii) \quad Q = Q_1 + Q_2$$

$$Q = C_1 V_1 + C_2 V_2$$

$$Q = 5 \times 10^{-6} \times 40 + 20 \times 10^{-6} \times 0$$

$$Q = 2 \times 10^{-4} C$$

#### OR

$$Q = CV$$

$$Q = 2.5 \times 10^{-5} \times 8$$

$$Q = 2 \times 10^{-4} C$$

$$(iii) \quad \text{Energy lost} = \text{energy before} - \text{energy after}$$

$$= \left( \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right) - \frac{1}{2} CV^2$$

$$= \left( \frac{1}{2} \times 5 \times 10^{-6} \times 40^2 + \frac{1}{2} \times 20 \times 10^{-6} \times 0^2 \right)$$

$$- \left( \frac{1}{2} \times 2.5 \times 10^{-5} \times 8^2 \right)$$

$$= 0.0032 J$$

- c. A capacitor of  $20\mu F$  is connected across 50V battery supply. When it has fully charged it is then disconnected and joined to capacitor of  $40\mu F$  having a p.d of 100V. Calculate;

- (i) Effective capacitance after joining
- (ii) The p.d on each capacitor
- (iii) Energy lost

#### Solution

$$(i) \quad C = C_1 + C_2$$

$$C = 20 \times 10^{-6} + 40 \times 10^{-6}$$

$$C = 6.0 \times 10^{-5} F$$

$$(ii) \quad \text{Charge before} = \text{charge after connection}$$

$$Q_1 + Q_2 = Q$$

$$C_1 V_1 + C_2 V_2 = CV$$

$$20 \times 10^{-6} \times 50 + 40 \times 10^{-6} \times 100 = 6.0 \times 10^{-5} V$$

$$V = 83.33 V$$

(iii) Energy lost = energy before – energy after

$$= \left( \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right) - \frac{1}{2} C V^2$$

$$= \left( \frac{1}{2} \times 20 \times 10^{-6} \times 50^2 + \frac{1}{2} \times 40 \times 10^{-6} \times 100^2 \right) - \left( \frac{1}{2} \times 6.0 \times 10^{-5} \times 83.33^2 \right)$$

$$= 0.017 J$$

- d. A parallel plate air-capacitor is charged to a potential difference of 20V. It is then connected in parallel with an uncharged capacitor of similar dimensions but having ebonite as its dielectric medium. The potential difference of the combination falls to 15V. Calculate the dielectric constant of the ebonite

**Solution**

Charge before = charge after connection

$$Q_0 = Q$$

$$C_0 V_0 = C V$$

$$C_0 V_0 = (C_0 + \epsilon_r C_0) V$$

$$29 = (1 + \epsilon_r) 15$$


$$\epsilon_r = 0.33$$

### Exercise

- A capacitor is charged by a 30V d.c supply. When the capacitor is fully charged, it is found to carry a charge of  $6.0 \mu C$ . find the;
  - Capacitance of the capacitor
  - Energy stored in the capacitor

**An((i)  $2.0 \times 10^{-7} F$ , (ii)  $9.0 \times 10^{-5} J$ ,  $1.5 \times 10^{-2} J$ )**
- Two capacitors of  $2 \mu F$  and  $3 \mu F$  are charged to a p.d of 50V and 100V respectively. Calculate;
  - Charge stored in each
  - Energy stored in each
  - Suppose capacitors are now joined with plate of the same charge connected together. Find the energy lost in the circuit


**An((i)  $1 \times 10^{-4} C$ ,  $3 \times 10^{-4} C$  (ii)  $2.5 \times 10^{-3} J$ ,  $1.5 \times 10^{-2} J$  (iii)  $1.5 \times 10^{-3} J$ )**
- A  $100 \mu F$  is charged from a supply of 1000V. it is then disconnected and then connected to an uncharged  $50 \mu F$  capacitor. Calculate;
  - Total energy stored initially and finally in the two capacitors
  - Energy lost **An(50J, 0.333J, 49.667J)**
- A  $20 \mu F$  capacitor was charged to 1000V and then connected across an uncharged  $60 \mu F$  capacitor. Calculate the p.d across a  $60 \mu F$  capacitor **An(10V)**
- A  $10 \mu F$  capacitor was charged to 300V and then connected across an uncharged  $60 \mu F$  capacitor. Calculate the total energy stored in both capacitors before and after connection. **An(0.45J, 0.064J)**
- A  $60 \mu F$  capacitor was charged from a 100V supply and then connected across an uncharged  $15 \mu F$  capacitor. Calculate the final p.d across the combination and the energy lost **An(80V, 23.7J)**
- A  $20 \mu F$  capacitor is charged to 40V and then connected across an uncharged  $60 \mu F$  capacitor. Calculate the potential difference across the  $60 \mu F$  capacitor. **An(10V)**
- An air capacitor of capacitance  $400 \mu F$ . is charged to 180V and the connected across un charged capacitor of capacitance  $500 \mu F$ .
  - Find the energy stored in the  $500 \mu F$  capacitor
  - With the two capacitors still connected, a dielectric of dielectric constant 1.5 is inserted between the plates of the  $400 \mu F$ . capacitor. If the separation between the plates remains the same, find the new p.d across the two capacitors. **An(116J, 65.5J)**
- A battery of e.m.f 15V is connected across a system of capacitors as shown below .

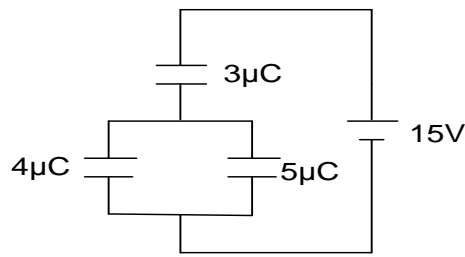

Find the

- (i) charge on the  $4\mu\text{F}$  capacitor
- (ii) energy stored in the  $3\mu\text{F}$  capacitor

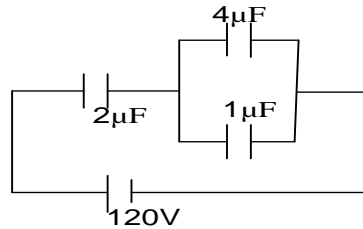10. Figure 9 shows a network of capacitors connected to a d.c. supply of 120 V.



Calculate the

- (i) charge on  $4\mu\text{F}$  capacitor
- (ii) energy stored in  $1\mu\text{F}$  capacitor


11. A  $20\mu\text{F}$  capacitor is charged to 40V and then connected across an uncharged  $60\mu\text{F}$  capacitor.

Calculate the potential difference across the  $60\mu\text{F}$  capacitor

12. A  $60\mu\text{F}$  capacitor is charged from a 100V supply. It is then connected across the terminals of a  $15\mu\text{F}$  uncharged capacitor. Calculate

- (i) the final p.d across the combination **An( 80V)**
- (ii) the difference in the initial and final energies stored in the capacitors and comment on the difference **An(0.06J)**


13.

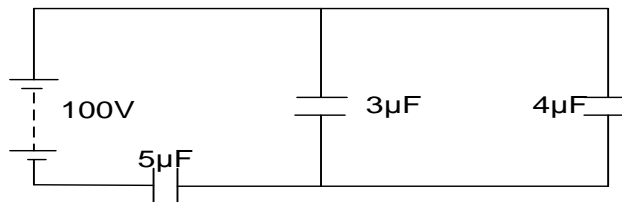

- (i) Find the resultant capacitance in the circuit
- (ii) Calculate the charge stored in each capacitor

**An(  $\frac{35}{12}\mu\text{F}, \frac{35}{12} \times 10^{-4}\text{C}, 1.25 \times 10^{-4}\text{C}, 1.67 \times 10^{-4}\text{C}$ )**


14.

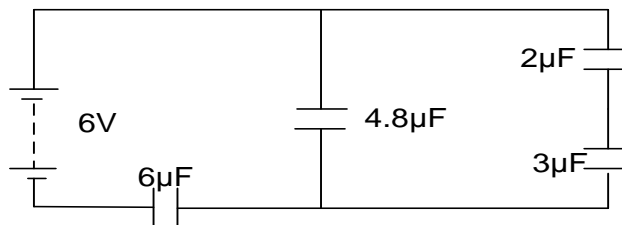

Find;

- (i) Effective capacitance
- (ii) Energy stored in the 2 capacitor **An(  $3\mu\text{F}, 3.24 \times 10^{-6}\text{J}$ )**


15.

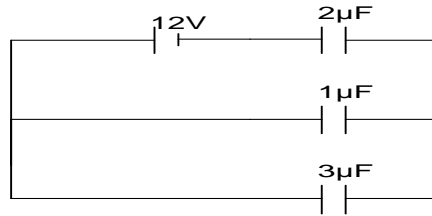

Find the energy stored in the capacitor of capacitance  $3\mu\text{F}$  shown in figure above, when the capacitor is fully charged

**Uneb 2016**

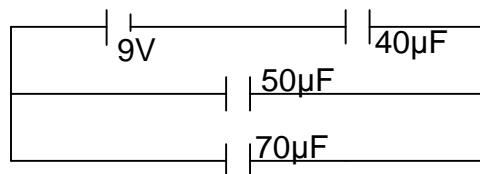- (a) (i) What is meant by capacitance of a capacitor. (01mark)  
 (ii) A parallel plate capacitor is connected across a battery and charged fully. When a dielectric material is now inserted between its plate, the amount of charge stored in the capacitor changes. Explain the change. (04marks)  
 (iii) Describe an experiment to determine the relative permittivity of a dielectric. (04marks)
- (b) A network of capacitors of capacitance  $40\mu\text{F}$ ,  $50\mu\text{F}$ , and  $70\mu\text{F}$  is connected to a battery of  $9\text{V}$  as shown below.




Calculate;

- (i) Charge stored in the  $50\mu\text{F}$  capacitor (05marks)  
 (ii) Energy stored in the  $40\mu\text{F}$  capacitor (03marks)
- (c) Explain **corona discharge**. (03marks)

**Uneb 2015**

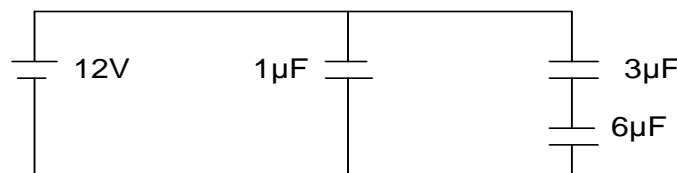- (a) (i) Define **capacitance** of a capacitor. (01mark)  
 (ii) Describe briefly an experiment to show the effect of placing a sheet of glass or mica between the plates of a capacitor on capacitance. (05marks)
- (b) Describe how capacitance of a capacitor can be measured using a ballistic galvanometer. (04marks)
- (c) Explain briefly how a charged capacitor can be fully discharged. (02marks)
- (d) A network of capacitors of capacitance  $3\mu\text{F}$ ,  $6\mu\text{F}$ , and  $1\mu\text{F}$  is connected to a battery of  $12\text{V}$  as shown below.



Calculate;

- (i) Charge stored by each capacitor (05marks)  
 (ii) Energy stored in the  $6\mu\text{F}$  capacitor when fully charged (03marks)

## CURRENT ELECTRICITY

Current is the rate of flow of electric charge.

If charge  $Q$ , coulombs flows through a circuit in a time  $t$  seconds, then the current  $I$ , amperes is given by

$$I = \frac{Q}{t}$$

$$\boxed{Q = I t}$$

The S.I unit of current is Amperes(A) and current is measured using an instrument called an Ammeter.

### Submultiples of A:

(i)  $1 \text{ mA} = 1 \times 10^{-3} \text{ A}$

(ii)  $1 \mu\text{A} = 1 \times 10^{-6} \text{ A}$

(iii)  $1 \text{ nA} = 1 \times 10^{-9} \text{ A}$

(iv)  $1 \text{ pA} = 1 \times 10^{-12} \text{ A}$

### Ampere;

Ampere is the current which, if flowing in two straight parallel wires of infinite length placed one meter apart in a vacuum, will produce on each of the wires a force of  $2 \times 10^{-7} \text{ Nm}^{-1}$ .

The S.I unit of charge is coulomb.

### Coulomb;

Is the quantity of electricity which passes any point in a circuit in 1 second when a steady current of 1 ampere is flowing.

### Examples

1. A charge of 180C flows through a lamp every 2 minutes. What is the electric current in the lamp.

#### Solution

$$I = \frac{Q}{t} \quad \Bigg| \quad I = \frac{180}{2 \times 60} \quad \Bigg| \quad I = 1.5 \text{ A}$$

2. A charge of 20 kC crosses two sections of a conductor in 1minute. Find the current through the conductor.

#### Solution

$$I = \frac{Q}{t} \quad \Bigg| \quad I = \frac{20 \times 1000}{1 \times 60} \quad \Bigg| \quad I = 333.33 \text{ A}$$

## POTENTIAL DIFFERENCE ( P. d )

*P. d* is defined as the work done in moving one coulomb charge from one point to another across a conductor.


Current will flow through a conductor if there **a potential difference** between the ends of a conductor.

The S. I unit of *P. d* is volt and *P. d* is measured using an instrument called a voltmeter

### A volt;

A volt is the potential difference between two points when one joule of work is done in transferring one coulomb of charge from one point to another.
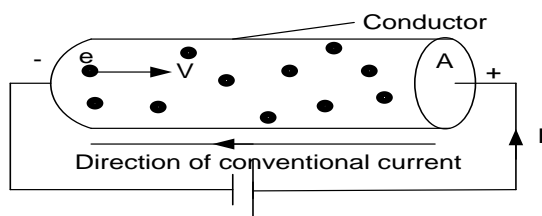
### Mechanism of electrical conduction in metals



- ❖ In metals there are free electrons in random motion. When a battery (cell) is connected across the ends of a metal, an electric field is set up between its ends.
- ❖ The conduction electrons are accelerated by the field and gain velocity and energy. On collision with atoms vibrating about fixed

mean positions, they give up some of their energy to the atoms.

- ❖ The amplitude of vibration of the atoms increases and the temperature of the metal rises. The electric field continuously accelerates the free electrons and on average

the electrons drift in the direction of the field with a mean speed.


- ❖ The continuous drift of the electrons in the same direction constitutes an electric current. The current produced is direct current (d.c) because the direction of flow is constant.

### Heating Effect of Current

- ❖ When a p.d is applied across the wire, the conduction electrons gain kinetic energy from the applied field.
- ❖ As the electrons drift along the wire in a direction opposite to the applied field, they collide with the ions and lose their kinetic energy to the ions.
- ❖ The ions vibrate with increased amplitudes as a result temperature of the wire rises due to collision
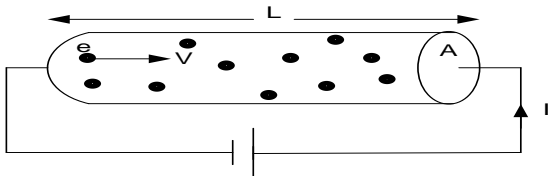
### Drift velocity of electrons

Consider a conductor of length  $l$  and cross-sectional area  $A$  having  $n$  free electrons per unit volume each carrying a charge,  $e$ .



Volume of the conductor =  $Al$

Number of free electrons in the conductor =  $nAl$ .

Total charge,  $Q$  of free electron =  $nAle$ .

Suppose a battery connected across the ends of the conductor causes a total charge  $Q$  to pass

through the conductor in time  $t$  with average drift velocity,  $v$ .

The resulting steady current  $I$ , is given by

$$I = \frac{Q}{t}$$

$$I = \frac{nAle}{t}$$

But the mean speed,  $v = \frac{l}{t}$

$$\boxed{I = nAve}$$

From  $I = nAve$

we can write  $\frac{I}{A} = nve$ . The quantity  $\frac{I}{A}$  is called the current density and is denoted by  $J$ .

Thus  $J = \frac{I}{A}$

**Definition:** Current density is the current flowing through a conductor of cross sectional area  $1 \text{ m}^2$ .

### Example

- (e) A current of 10A flows through a copper wire of area  $1 \text{ mm}^2$ . The number of free electrons per  $\text{m}^3$  is  $10^{29}$ . Find the drift velocity of the electron.

#### Solution

$$v = \frac{I}{nAe}$$

$$v = \frac{10}{10^{29} \times 1 \times 10^{-6} \times 1 \times 10^{-6}}$$

$$v = 6.25 \times 10^{-4} \text{ m/s}$$

- (f) A metal wire contains  $5 \times 10^{22}$  electrons per  $\text{cm}^3$  and has cross sectional area of  $1 \text{ mm}^2$ . If the electrons move along the wire with a mean drift velocity of  $1 \text{ mm s}^{-1}$ , Calculate:

- (i) current density
- (ii) current in the wire.

**Solution**

- (i) current density =  $\frac{I}{A} = nev = 5 \times 10^{22} \times 10^{-3} \times 1.6 \times 10^{-19} = 8 \times 10^6 \text{ Am}^{-2}$
- (ii) current = current density x Area, =  $8 \times 10^6 \times 10^{-6}$

**Conductivity,  $\sigma$**

The conductivity of a material is the reciprocal of its resistivity. It is denoted by  $\sigma$ .

$$\sigma = \frac{1}{\rho}$$

The S.I unit of conductivity is  $\Omega^{-1}m^{-1}$

**Example:**

- (a) Calculate the drift velocity of the free electrons in a copper wire of cross-sectional area  $1.0 \text{ mm}^2$  when the current flowing through the wire is  $2.0 \text{ A}$ . (Number of free electrons in copper is  $1 \times 10^{29} \text{ m}^{-3}$ )
- (b) Explain how the drift velocity of free electrons in a metal conductor carrying a steady current changes when
  - (i) The p.d between the ends of the conductor is increased
  - (ii) The temperature of the conductor increases but the current remains unchanged.

**Solution:**

- (a) Using the equation,  $I = nAve$

Drift velocity,  $v = \frac{I}{nAe}$

$$v = \frac{2.0}{(1.0 \times 10^{29})(1.0 \times 10^{-6})(1.6 \times 10^{-19})}$$

$$v = 1.25 \times 10^{-4} \text{ m s}^{-1}$$

- (b) (i) The drift velocity increases as the higher p.d would accelerate the free electrons to a higher velocity.
- (ii) The drift velocity decreases as the temperature increases. At a higher temperature, the ions in the metal lattice vibrate with greater amplitude, the mean free path decreases and the free electrons are unable to accelerate to a higher velocity. This results in increase of resistance to current flow.

**OHM'S LAW**


It states that the current flowing through a conductor is proportional to the potential difference across its ends provided temperature and other physical conditions remain constant.

ie  $V \propto I$  at constant temperature

$$\boxed{V = IR}$$

$R$  is resistance,  $V$  is p.d,  $I$  is current

**Verification of ohm's law**

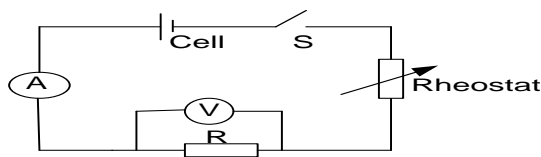

- ❖ A-ammeter, V- voltmeter, R-resistor, S- switch
- ❖ Arrange the apparatus as shown above.
- ❖ Switch is closed and rheostat adjusted so that A and V read suitable values of I and V respectively

- ❖ Ammeter reading I and voltmeter reading V are note and recorded
- ❖ The procedures above are repeated to obtain several values of I and V
- ❖ Tabulate the results in a suitable table
- ❖ A graph of V against I is plotted.
- ❖ A straight line through the origin verifies Ohms law

### Limitations of ohm's law

- It does not apply to semiconductors and gases.
- It is only obeyed if physical conditions like temperature are constant.


### Ohmic and non ohmic conductors

An ohmic conductor is one which obeys ohm's law.

Non ohmic conductor s one which doesnot obey ohm's law.


When we plot I against V between ends of a conductor, the shape of the curve is known as the characteristic of the conductor.

#### a) Ohmic conductors eg a metal

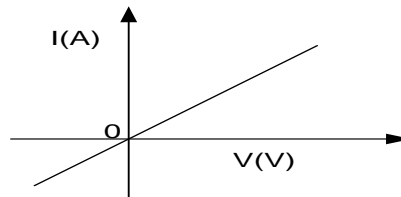


#### b) Non ohmic conductor


##### i) Filament lamp

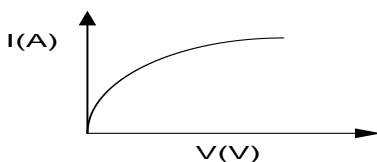


##### ii) Gas discharge tube

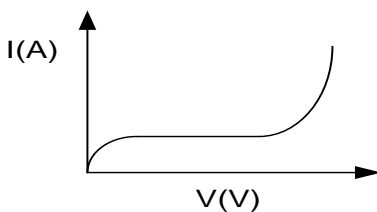


##### iii) Thermionic diode

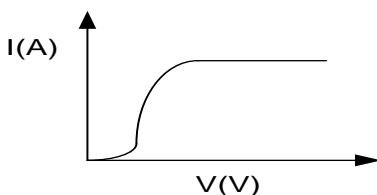


##### iv) Junction diode

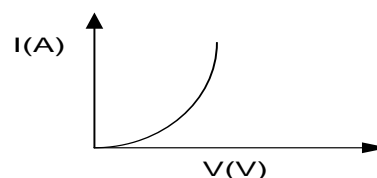

##### v) Thermistor

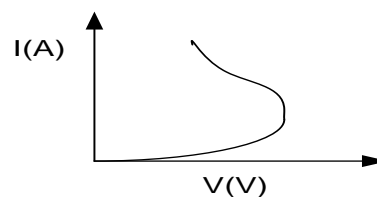
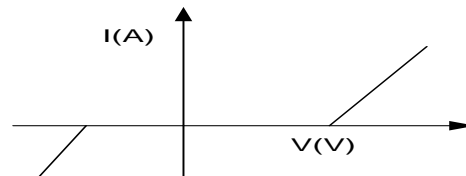
##### vi) Electrolyte eg dilute sulphuric acid




## Resistance

This is the opposition of a conductor to the flow of current.

It is measured in ohms ( $\Omega$ )

**OR :** Resistance of a conductor is the ratio of the potential difference across its ends to the current flowing through it.

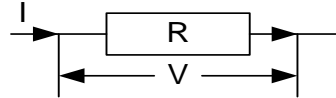A good conductor has low resistance while a good insulator has high resistance



$$R = \frac{V}{I} \dots\dots\dots 1$$

The S.I unit of electrical resistance is the ohm, symbol  $\Omega$ .

### Definition


#### An ohm ( $\Omega$ )

is defined as the resistance of a conductor if a current of 1A flows through when the p.d across it is 1V.

$$(1 \Omega = 1 \text{ V A}^{-1})$$

## ARRANGEMENT OF RESISTORS

### a) Resistors in series

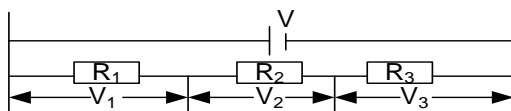

When resistors are in series, current flowing through them is the same.

$$\text{Total P. d. } V = V_1 + V_2 + V_3$$

$$V_1 = I R_1, V_2 = I R_2 \text{ and } V_3 = I R_3$$

$$V = I R_1 + I R_2 + I R_3$$

$$V = I (R_1 + R_2 + R_3)$$


$$\frac{V}{I} = R_1 + R_2 + R_3 \text{ but } \frac{V}{I} = R$$

$$\boxed{R = R_1 + R_2 + R_3}$$

Where R is equivalent resistance
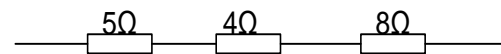
### Example

Find the total resistance in the circuits below




### Solution

$$R = (5 + 4 + 8) \Omega$$

$$R = 17\Omega$$

### b) Resistors in parallel

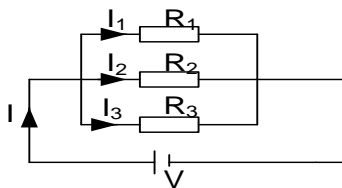

When resistors are in parallel, p.d across the ends is the same.

$$\text{Total current, } I = I_1 + I_2 + I_3$$

$$\text{Where } I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2} \text{ and } I_3 = \frac{V}{R_3}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{I}{V} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \text{ but } \frac{I}{V} = \frac{1}{R}$$


$$\frac{1}{R} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Where R is equivalent resistance

### Example

a) Find the effective resistance of the following circuit

1.

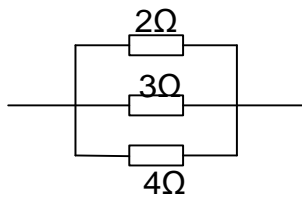

**Solution**

$$\frac{1}{R} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\frac{1}{R} = \left( \frac{1}{2} + \frac{1}{3} + \frac{1}{4} \right)$$

$$\frac{1}{R} = \frac{13}{12}$$

$$R = \frac{12}{13}$$

$$R = 0.92\Omega$$

2.

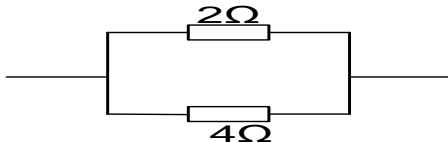

**Solution**


$$\frac{1}{R} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R} = \left( \frac{1}{2} + \frac{1}{4} \right)$$

$$\frac{1}{R} = \frac{3}{4}$$

$$R = \frac{4}{3} \quad R = 1.33\Omega$$

**Note for two resistors in parallel**

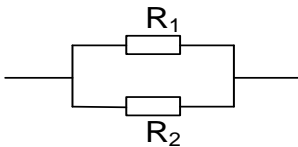

$$\frac{1}{R} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\frac{1}{R} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$R = \frac{\text{product of resistance}}{\text{sum of resistance}}$$

b) Calculate the effective resistance in each of the following circuits

(i)

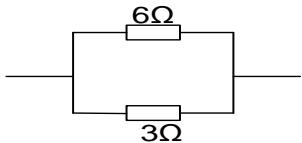

**Solution**


$$R = \frac{\text{product of resistance}}{\text{sum of resistance}}$$

$$R = \frac{6 \times 3}{6 + 3}$$

$$R = \frac{18}{9}$$

$$R = 2\Omega$$

(ii)

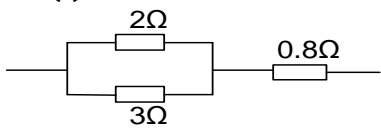


**Solution**

$$R = 0.8 + \frac{2 \times 3}{2 + 3}$$

$$R = 0.8 + \frac{6}{5}$$

$$R = 2\Omega$$

(iii)

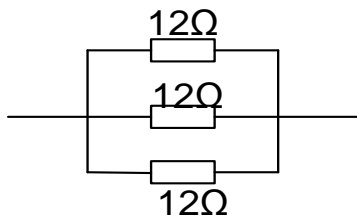

$$\frac{1}{R} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\frac{1}{R} = \left( \frac{1}{12} + \frac{1}{12} + \frac{1}{12} \right)$$

$$\frac{1}{R} = \frac{3}{12}$$

$$R = \frac{12}{3} \quad R = 4\Omega$$

**Solution**

(iv)

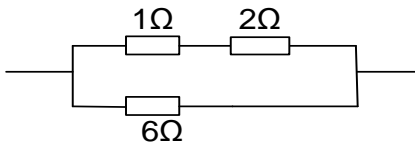


**Solution**

For series

$$R = (1 + 2)\Omega = 3\Omega$$

(v)

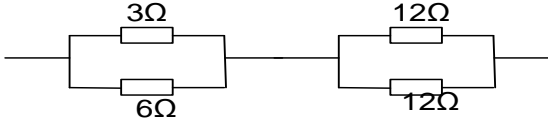


**Solutions:**

For the first set of parallel resistors

$$R = \frac{6 \times 3}{6 + 3}$$


(vi)

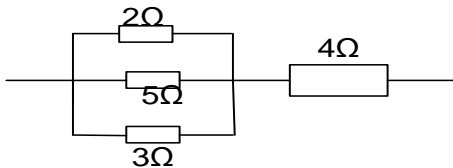

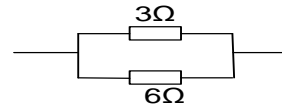**Solution**

For parallel combination

$$\frac{1}{R} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$




$$R = \frac{6 \times 3}{6 + 3}$$

$$R = \frac{18}{9} = 2\Omega$$

$$R = 2\Omega$$

For the second set of parallel resistors
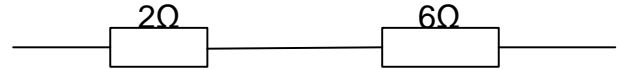
$$R = \frac{12 \times 12}{12 + 12} = 6\Omega$$




$$\text{Total resistance} = 2 + 6 = 8\Omega$$

$$\frac{1}{R} = \left( \frac{1}{2} + \frac{1}{5} + \frac{1}{3} \right)$$

$$\frac{1}{R} = \frac{31}{30}$$

$$R = \frac{30}{31}$$

$$R = 0.97\Omega$$

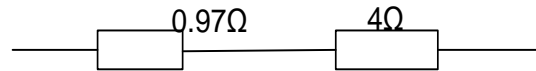


$$\text{Total resistance} = 0.97 + 4 = 4.97\Omega$$

### Further examples

1. Find the ammeter readings in each of the circuits below


i)

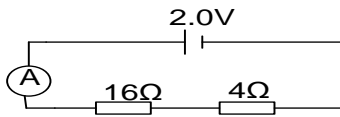

**Solution**

$$V = IR$$

ii)

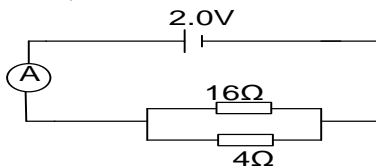

**Solution**

$$V = IR$$

$$I = \frac{V}{R}$$

iii)

$$I = \frac{V}{R}$$

$$I = \frac{2}{16 + 4}$$

$$I = 0.1 \text{ A}$$


$$R = \frac{\text{product of resistance}}{\text{sum of resistance}}$$

$$R = \frac{16 \times 4}{16 + 4}$$

$$R = 3.2\Omega$$

$$I = \frac{2}{3.2}$$

$$I = 0.625 \text{ A}$$

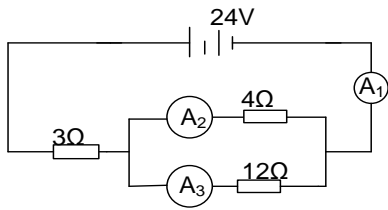

**Solution**

$$A_1 = A_2 + A_3$$

$A_1$  reads current in the whole circuit

$$V = IR$$

$$I_1 = \frac{V}{R}$$

$$\text{Total } R = \left[ 3 + \left( \frac{4 \times 12}{4 + 12} \right) \right]$$

$$R = 3\Omega + 3\Omega$$

$$R = 6\Omega$$

$$I_1 = \frac{24}{6}$$

$$I_1 = 4A$$

To find  $A_2$  and  $A_3$ , we need to first find voltage across parallel combination

$$V = IR_p$$

$I$  is the current through the parallel combination and  $R_p$  is total resistance of the parallel combination

$V = 4 \times \left( \frac{4 \times 12}{4 + 12} \right)$

$$V = 4 \times 3$$

$$V = 12V$$

**Note :** For any resistors in parallel, they have the same  $p.d$

$$\text{Current in } A_2: I_2 = \frac{V}{R}$$

$$I_2 = \frac{12}{4}$$

$$I_2 = 3A$$

$$\text{Current in } A_3: I_3 = \frac{V}{R}$$

$$I_3 = \frac{12}{12}$$

$$I_3 = 1A$$

**To quickly confirm the currents;**

$$\text{Current in } A_2: I_2 = \frac{R_3}{R_2 + R_3} \times I$$

$$I_2 = \frac{12}{16} \times 4$$


$$I_2 = 3A$$

$$\text{Current in } A_3: I_3 = \frac{R_2}{R_2 + R_3} \times I$$

$$I_3 = \frac{4}{16} \times 4$$

$$I_3 = 1A$$

2.

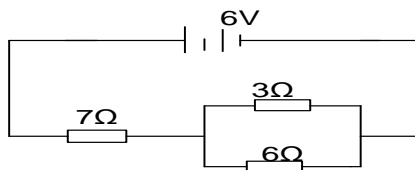

In the figure above find;

- (i) Current through the circuit
- (ii) Current across 3Ω and 6Ω resistor
- (iii)  $P.d$  across the 7Ω resistor
- (iv)  $P.d$  across the 3Ω and 6Ω resistor

**Solution**

i) Total resistance,  $R = \left[ 7 + \left( \frac{6 \times 3}{6 + 3} \right) \right]$

$$R = 7\Omega + 2\Omega$$

$$R = 9\Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{6}{9}$$

$$I = 0.667 A$$

Current in the circuit is 0.667 A

- ii) Voltage across the parallel combination

$$V = IR_p$$

$$V = 0.667 \times \left( \frac{6 \times 3}{6 + 3} \right)$$

$$V = 0.667 \times 2$$

$$V = 1.334V$$

**Note :** For any resistors in parallel, they have the same  $p.d$

$$\text{Current in } 3\Omega \text{ resistor: } I = \frac{V}{R}$$

$$I = \frac{1.334}{3}$$

$$I = 0.445A$$

$$\text{Current in } 6\Omega \text{ resistor: } I = \frac{V}{R}$$

$$I = \frac{1.334}{6}$$

$$I = 0.223A$$

**To quickly confirm the currents;**

$$\text{Current in } 3\Omega \text{ resistor: } I = \frac{6}{6+3} \times 0.667$$

$$I = \frac{6}{9} \times 0.667$$

$$I = 0.445A$$

$$\text{Current in } 6\Omega \text{ resistor: } I = \frac{3}{6+3} \times 0.667$$

$$I = \frac{3}{9} \times 0.667$$

$$I = 0.223A$$

- iii)  $P.d$  across the 7Ω resistor  
0.6A Passes through the 7Ω resistor

$$V = IR$$

$$V = 7 \times 0.667$$

$$V = 4.669V$$


- iv)  $P.d$  across the 3Ω resistor and 6Ω resistor

$$V = (6 - 4.669)V$$

$$V = 1.33V$$

since the two resistors are in parallel therefore, they have the same  $p.d$  of 1.33V

3.

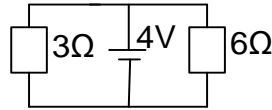

Two resistors of  $3\Omega$  and  $6\Omega$  are connected across a battery of *emf* of  $4V$  as show, find

- i) the combined resistance
- ii) the current supplied by the battery

**Solution**

$$i) \quad R = \frac{\text{product of resistance}}{\text{sum of resistance}}$$

$$R = \frac{6 \times 3}{6 + 3}$$

$$R = 2\Omega$$


$$ii) \quad I = \frac{V}{R}$$

$$I = \frac{4}{2}$$

$$I = 2A$$


**Exercise**

1.

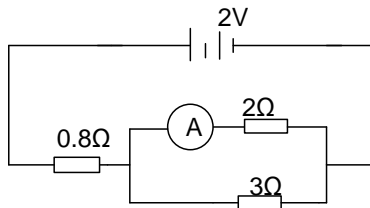

Find the ammeter reading  
**[0.6A]**

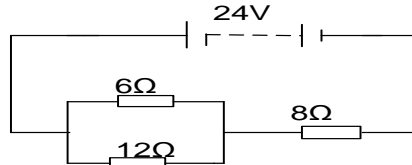
2. A *p.d* of  $24V$  from a battery is applied to a network of resistors as shown below



- i) find the current through the circuit
- ii) find the *p.d* across the  $8\Omega$  resistor
- iii) find the current through the  $6\Omega$  resistor


**[2A]**  
**[16V]**  
**[1.3A]**

3.

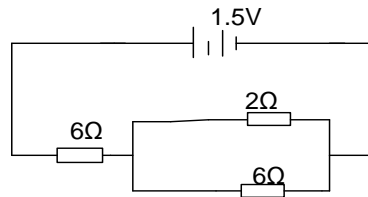

Find the current through the  $2\Omega$  resistor

4.

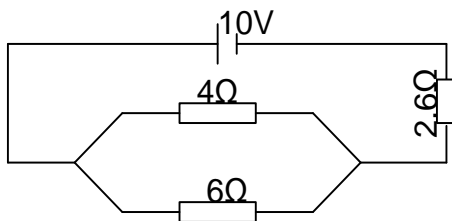

A battery of *emf*  $10V$  and negligible internal resistance is connected across a network of resistors as shown above. calculate the current through the  $6\Omega$  resistor.

**[0.8A]**

## Factors that affect resistance

### a) Temperature

- ❖ Conduction in metals is by free electrons. The drift electrons however are obstructed by atoms in their lattice positions.
- ❖ When temperature of the metal increases, the atoms vibrate with a larger amplitude thus reducing the mean free path of the free electrons reducing the drift velocity of free electrons hence increase in resistance

### b) Length

The longer the conductor, the higher the resistance and the shorter the conductor the lower resistance. Free electrons collide more frequently with atoms, at each collision they lose some kinetic energy to atoms vibrating at fixed mean positions. This leads to a decrease in the drift velocity of the electrons and hence an increase in resistance

### c) Cross sectional area

The thinner the conductor, the higher the resistance and the thicker the conductor, the lower the resistance. When there is an increase in the cross sectional area the number of free electrons that drift along the conductor also increases. This leads to an increase in current hence a decrease in resistance.

The above factors can be combined as;

$$\rho \propto L/A$$

$$R = \frac{\rho L}{A}$$

Where  $\rho$  is resistivity

### Definition

Electrical Resistivity is the resistance across opposite faces of a 1m-cube of a material

Resistivity is the electrical resistance across opposite faces of a 1m-cube of a material

### Examples

1. A conductor of length 20cm has a cross sectional area of  $2 \times 10^{-4} \text{ m}^2$ . Its resistance at  $20^\circ\text{C}$  is  $0.6\Omega$ . find the resistivity of the conductor at  $20^\circ\text{C}$ .

#### Solution

$$R = \frac{\rho L}{A}$$

$$\rho = \frac{RA}{L}$$

$$\rho = \frac{0.6 \times 2 \times 10^{-4}}{0.2}$$

$$\rho = 6 \times 10^{-4} \Omega \text{ m}$$

2. A wire of diameter 14mm and length 50cm has its resistivity as  $1.0 \times 10^{-7} \Omega \text{ m}$ . What is the resistance of the wire at room temperature?

#### Solution

$$d = 14\text{mm}, r = \frac{14}{2} = 7\text{mm}$$

$$l = 50\text{cm}, l = 0.5\text{m}$$

$$A = \pi r^2$$

$$A = \frac{22}{7} \times \left(\frac{7}{1000}\right)^2$$

$$A = 1.54 \times 10^{-4} \text{ m}^2$$

$$R = \frac{\rho L}{A}$$

$$R = \frac{0.5 \times 1 \times 10^{-7}}{1.54 \times 10^{-4}}$$

$$R = 3.25 \times 10^{-4} \Omega$$

3. A steady uniform current of 5mA flows along a metal cylinder of cross sectional area of  $0.2\text{mm}^2$ , length, 5m and resistivity  $3 \times 10^{-5} \Omega \text{ m}$ . find the p.d across the ends of the cylinder.

#### Solution

$$R = \frac{\rho L}{A}$$


$$R = \frac{5 \times 3 \times 10^{-5}}{2 \times 10^{-7}}$$

$$R = 750 \Omega$$

$$V = IR$$

$$V = 5 \times 10^{-3} \times 750 = 3.75V$$

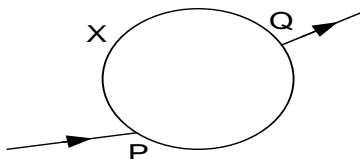4. A wire of diameter  $d$ , length  $l$  and resistivity  $\rho$  forms a circular loop. Current enters and leaves at points P and Q.



Show that the resistance  $R$  of the wire is given by  $R = \frac{4 \rho x(l-x)}{\pi d^2 l}$

### Solution

Let  $R_1$  and  $R_2$  be resistance of portion  $x$  and  $l - x$  of the wire respectively.

$$R_1 = \frac{\rho x}{A} \text{ and } R_2 = \frac{\rho(l-x)}{A}$$

The two portions are in parallel, hence  $R = \frac{R_1 R_2}{R_1 + R_2}$

$$R = \frac{\left(\frac{\rho x}{A}\right) \left(\frac{\rho(l-x)}{A}\right)}{\left(\frac{\rho x}{A}\right) + \left(\frac{\rho(l-x)}{A}\right)} = \frac{\rho x(l-x)}{Al}$$

But  $A = \frac{\pi d^2}{4}$

$$R = \frac{\rho x(l-x)}{Al} = \frac{4 \rho x(l-x)}{\pi d^2 l}$$

### Question

A p.d of 4.5V is applied to the ends of a 0.69m length of a wire of cross sectional area  $6.6 \times 10^{-7} \text{m}^2$ . Calculate the drift velocity of electrons across the wire. ( $\rho$  of wire is  $4.3 \times 10^{-7} \Omega \text{m}$ , number of electrons per  $\text{m}^3$  is  $10^{28}$  and electronic charge is  $1.6 \times 10^{-19} \text{C}$ )

### Temperature coefficient of resistance ( $\alpha$ ),

The temperature coefficient of resistance of a material is the fractional change in the resistance at  $0^\circ \text{C}$  per degree celcius rise in temperature.

If a material has resistance  $R_0$  at  $0^\circ \text{C}$  and its resistance increases to  $R_\theta$  when heated through a temperature  $\theta$ , then


$$\alpha = \frac{R_\theta - R_0}{R_0 \theta}$$

The S.I unit of  $\alpha$  is  $\text{K}^{-1}$  or  $^\circ \text{C}^{-1}$

The above equation can be rearranged;

$$R_\theta = R_0(1 + \alpha\theta)$$

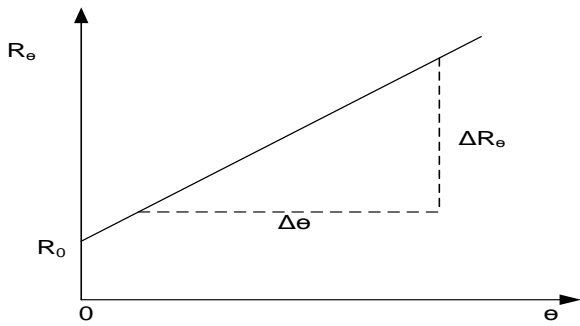A graph of  $R_\theta$  against  $\theta$  is a straight line whose intercept on the  $R_\theta$  - axis is equal to  $R_0$  and the slope =  $\alpha R_0$ .



$$S = \frac{\Delta R_\theta}{\Delta \theta} = \alpha R_0$$

$$\alpha = \frac{S}{R_0}$$

If  $R_1$  and  $R_2$  are the resistances of a conductor at temperatures  $\theta_1$  and  $\theta_2$ , then

$$R_1 = R_0(1 + \alpha\theta_1) \dots \dots \dots \text{i}$$

$$R_2 = R_0(1 + \alpha\theta_2) \dots \dots \dots \text{ii}$$

Divide i by ii  $\boxed{\frac{R_1}{R_2} = \frac{1 + \alpha\theta_1}{1 + \alpha\theta_2}}$

**Note:**

Super conductors are materials whose resistance vanishes when cooled to about  $-273^\circ\text{C}$

**Why metals have positive temperature coefficient of resistance**

When the temperature of the metal increases, the amplitude of vibration of its atoms increases. This reduces the mean free path for the conduction electrons. Thus fewer electrons now flow per second through the metal and hence less which increases the resistance.

**Why semi-conductors have negative temperature coefficient of resistance**

Semi-conductors have few electrons available for conduction at room temperature. When current is passed through it, the material heats up. As the temperature increases, loosely bound electrons are released for conduction thus current increases hence resistance reduces

**Examples**

- The resistivity of mild steel is  $15 \times 10^{-8} \Omega \text{ m}$  at  $20^\circ\text{C}$  and its temperature coefficient of resistance is  $50 \times 10^{-4} \text{ K}^{-1}$ . Calculate the resistivity at  $60^\circ\text{C}$ .

**Solution**

Since the resistance of a conductor when heated is proportional to resistivity, it follows that the resistivity at temperature  $\theta$  is given by

$$\rho_\theta = \rho_0(1 + \alpha\theta)$$

Where  $\alpha$  is the temperature coefficient of resistivity.

At  $20^\circ\text{C}$ ,

$$15 \times 10^{-8} = \rho_0(1 + 50 \times 10^{-4} \times 20)$$

$$15 \times 10^{-8} = 1.1\rho_0$$

$$\rho_0 = \frac{15 \times 10^{-8}}{1.1} = 13.64 \times 10^{-8} \Omega \text{ m}$$

At  $60^\circ\text{C}$ ,

$$\rho_{60} = 13.64 \times 10^{-8}(1 + 60 \times 50 \times 10^{-4})$$

$$\rho_{60} = 17.7 \times 10^{-8} \Omega \text{ m}$$

- A coil of wire has resistances of  $30 \Omega$  at  $20^\circ\text{C}$  and  $34.5 \Omega$  at  $60^\circ\text{C}$ . Calculate

(i) The temperature coefficient of resistance of the wire

(ii) The resistance of the wire at  $0^\circ\text{C}$ .

**Solution:**

(i) At  $20^\circ\text{C}$ ,

$$R_{20} = 30 \Omega$$

$$30 = R_0(1 + 20\alpha) \dots \dots \dots \text{1}$$

At  $60^\circ\text{C}$ ,

$$R_{60} = 34.5 \Omega$$

$$R_{60} = R_0(1 + 60\alpha) \dots \dots \dots \text{2}$$

Divide equation 1 by 2

$$\frac{30}{34.5} = \frac{R_0(1 + 20\alpha)}{R_0(1 + 60\alpha)}$$

$$\frac{30}{34.5} = \frac{1 + 20\alpha}{1 + 60\alpha}$$

$$30 + 1800\alpha = 34.5 + 690\alpha$$

$$1110\alpha = 4.5$$

$$\alpha = 4.05 \times 10^{-3} K^{-1}$$

- (ii) Substitute for  $\alpha$  in equation 1 or 2 to solve for  $R_0$

$$30 = R_0 + 20 \times 0.00405 \times R_0$$

$$R_0 = 27.75 \Omega$$

3. The resistance of a nichrome element of an electric fire is  $50.9 \Omega$  at  $20^\circ C$ . When operating on at  $240 V$  supply, the current flowing in it is  $4.17 A$ . Calculate the steady temperature reached by the electric fire if the temperature coefficient of resistance of nichrome is  $1.7 \times 10^{-4} K^{-1}$ .

**Solution:**

At  $20^\circ C$ ,  $R_{20} = 50.9 \Omega$

From  $R_\theta = R_0(1 + \alpha\theta)$

$$50.9 = R_0(1 + 20 \times 1.7 \times 10^{-4})$$

$$R_0 = \frac{50.9}{1.0034} = 50.7275 \Omega$$

Let the unknown temperature to which the element heats up be,  $\beta$ .

At  $\beta^\circ C$ ,

$$V = 240 V, I = 4.17 A$$

$$R_\beta = \frac{240}{4.17} = 57.554 \Omega$$

$$R_\beta = R_0(1 + \alpha\beta)$$

$$57.554 = 50.7275(1 + 1.7 \times 10^{-4}\beta)$$

$$6.8265 = 8.6237 \times 10^{-3}\beta$$

$$\beta = 791.6^\circ C$$

4. An electric heater consists of  $5.0m$  of nichrome wire of diameter  $0.58mm$ . When connected to a  $240V$  supply, the heater dissipates  $2.5kW$  and the temperature of the heater is found to be  $1020^\circ C$ . If the resistivity of the nichrome at  $10^\circ C$  is  $1.02 \times 10^{-6} \Omega m$ . Calculate;

- (i) The resistance of nichrome at  $10^\circ C$   
 (ii) The mean temperature coefficient of resistance of nichrome between  $10^\circ C$  and  $1020^\circ C$

**Solution**

(i)  $R_{10} = \frac{\rho l}{A} = \frac{1.02 \times 10^{-6} \times 5}{\pi \left(\frac{0.58 \times 10^{-3}}{4}\right)^2} = 19.3 \Omega$

(ii) At  $1020^\circ C$ ,  $P_{1020} = \frac{V^2}{R_{1020}} = 2.5 kW$

$$R_{1020} = \frac{240^2}{2.5 \times 10^3} = 23.04 \Omega$$

$$23.04 = R_0(1 + 1020\alpha) \dots\dots\dots 1$$

At  $10^\circ C$ ,

$$19.3 = R_0(1 + 10\alpha) \dots\dots\dots 2$$

Eq 2 ÷ Eq 1

$$\frac{23.04}{19.3} = \frac{1 + 1020\alpha}{1 + 10\alpha}$$

$$\alpha = 1.92 \times 10^{-4} K^{-1}$$

**Exercise**

3. The resistance of a nichrome element of an electric fire is  $50 \Omega$  at  $20^\circ C$ . When operating on a  $240 V$  supply, the current flowing in it is  $4.0 A$ . Calculate the steady temperature reached by the electric fire if the temperature coefficient of resistance of nichrome is  $2.0 \times 10^{-4} K^{-1}$ . **An(1024.1°C)**
4. The resistivity of a certain wire is  $1.6 \times 10^{-7} \Omega m$  at  $30^\circ C$  and its temperature coefficient of resistance is  $6.0 \times 10^{-3} K^{-1}$ . Calculate the resistivity at  $80^\circ C$ . **An(2.01 × 10<sup>-7</sup> Ωm)**
5. A nichrome wire of length  $1.0m$  and diameter  $0.72mm$  at  $25^\circ C$ , is made into a coil. The coil is immersed in  $200cm^3$  of water at the same temperature and a current of  $5.0 A$  is passed through the coil for 8 minutes until when the water starts to boil at  $100^\circ C$ .

Find:

- (i) the resistance of the coil at  $25^\circ C$   
 (ii) the electrical energy expended assuming all of it goes into heating the water.  
 (iii) the mean temperature coefficient of resistance of nichrome between  $0^\circ C$  and  $100^\circ C$ .

5. Two wires A and B have lengths which are in the ratio 4 : 5, diameters which are in the ratio 2 : 1, and resistances in the ratio of 3 : 2. If the wires are arranged in parallel and current of 1.0 A flows through the combination, find the:
- ratio of resistance of wire A to that of wire B
  - current through wire A
6. A battery of e.m.f 12V and negligible internal resistance is connected to the ends of a metallic wire of length 50 cm and cross-sectional area 0.1 mm<sup>2</sup>. If the resistivity of a material of the wire is  $1.0 \times 10^{-6} \Omega \text{ m}$  at what rate is heat generated in the wire?
7. The table below shows the resistance of a nichrome wire at various temperatures.

|                  |     |       |       |       |       |
|------------------|-----|-------|-------|-------|-------|
| Temperature (°C) | 75  | 120   | 150   | 250   | 300   |
| Resistance (Ω)   | 103 | 103.8 | 104.4 | 105.9 | 106.8 |

Plot a suitable graph and use it to determine the temperature coefficient of resistance of nichrome

### Electromotive force and internal resistance

The e.m.f of a cell is the energy supplied by the cell to transfer 1C of charge round a complete circuit in which the cell is connected.

It may also be defined as the p.d across the terminals of the cell when on an open circuit.

Internal resistance of a cell is the opposition in series with the external circuit which accounts for energy losses inside the cell when the cell is supplying current.


Internal resistance is represented by r.

$$E = I(R + r)$$

### Examples

1. A battery of emf 1.5V and internal resistance 0.5Ω is connected in series with 2.5Ω resistor. Find;
- current through the circuit
  - p.d of the 2.5Ω resistor

### Solution

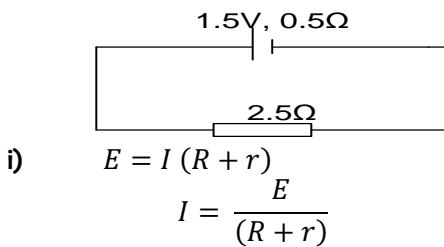

$$I = \frac{1.5}{(2.5 + 0.5)}$$

$$I = \frac{1.5}{3}$$


$$I = 0.5 \text{ A}$$

ii)  $V = IR$   
 $V = 0.5 \times 2.5$   
 $V = 1.25 \text{ V}$

2. A cell can supply a current of 1.2A through two 2Ω resistors connected in parallel. When they are connected in series the value of current is 0.4A. Calculate the internal resistance and emf of the cell.

### Solution

#### case 1

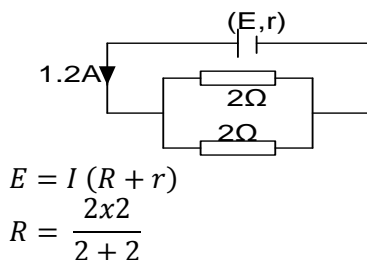


$$R = 1\Omega$$

$$E = 1.2(1 + r)$$

$$E = 1.2 + 1.2r \dots \dots [1]$$

#### Case 2

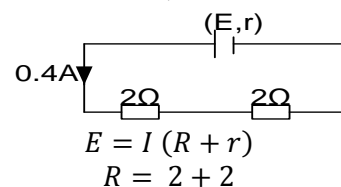

$$R = 4\Omega$$

$$E = 0.4(4 + r)$$

$$E = 1.6 + 0.4r \dots\dots [2]$$

Equating 1 and 2

$$1.2 + 1.2r = 1.6 + 0.4r$$

$$1.2r - 0.4r = 1.6 - 0.4$$

$$0.8r = 0.4$$

$$r = \frac{0.4}{0.8}$$

$$r = 0.5\Omega$$

**Also**  $E = 1.2 + 1.2r$


$$E = 1.2 + 1.2 \times 0.5$$

$$E = 1.2 + 0.6$$

$$E = 1.8V$$

3. An ammeter connected in series with a cell and a  $2\Omega$  resistor reads  $0.5A$ . When the  $2\Omega$  resistor is replaced by a  $5\Omega$  resistor, the ammeter reading drops to  $0.25A$ . Calculate the internal resistance and the *emf* of the cell.


Solution

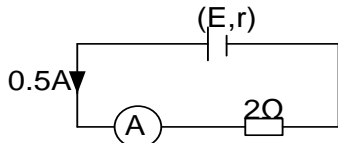

$$E = I(R + r)$$

$$E = 0.5(2 + r)$$

$$E = 1 + 0.5r \dots\dots [1]$$

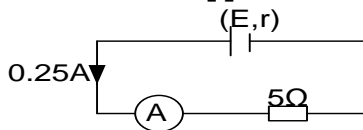

$$E = I(R + r)$$

$$E = 0.25(5 + r)$$

$$E = 1.25 + 0.25r \dots\dots [2]$$

Equating 1 and 2

$$1 + 0.5r = 1.25 + 0.25r$$

$$0.5r - 0.25r = 1.25 - 1$$

$$0.25r = 0.25$$

$$r = \frac{0.25}{0.25}$$

$$r = 1\Omega$$

**Also**  $E = 1 + 0.5r$


$$E = 1 + 0.5 \times 1$$

$$E = 1 + 0.5$$

$$E = 1.5V$$

**Exercise**

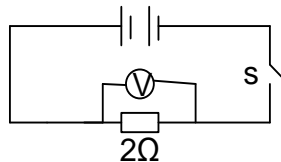
1. A battery of e.m.f and internal resistance,  $r$  is connected across a variable resistor, when the resistor is set at  $21\Omega$ , the current through it is  $0.48A$ . when it is set at  $36\Omega$ , the current is  $0.30A$ . find  $E$  and  $r$ . [ $4\Omega, 12V$ ]
2. A cell is joined in series with a resistance of  $2\Omega$  and a current of  $0.25A$  flows through it. When a second resistance of  $2\Omega$  is connected in parallel with the first, the current through the cell is  $0.3A$ . Calculate the internal resistance and *emf* of the cell. [ $4\Omega, 1.5V$ ]
3. Two cells each of e.m.f  $1.5V$  and internal resistance  $0.5\Omega$  are connected in series with a resistor of  $2\Omega$  as in the figure below.



The reading of the voltmeter  $V$  when  $S$  is closed is?

[2V]

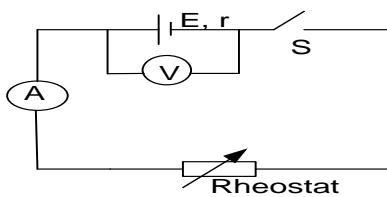**Measurement of E.m.f and internal resistance of a cell**



- A-ammeter, V- voltmeter, R-resistor, S- switch
- ❖ Arrange the apparatus as shown above.
- ❖ Switch is closed and rheostat adjusted to a suitable value of  $I$
- ❖ Ammeter reading  $I$  and voltmeter reading  $V$  are note and recorded

- ❖ The rheostat is varied for other values of  $I$  and corresponding values of  $V$  are noted and recorded.
- ❖ A graph of  $V$  against  $I$  is plotted.

- ❖ The intercept on the  $V$  axis is noted which is the e.m.f of the cell.
- ❖ The slope  $s$  is obtained and the internal resistance of the cell  $r = -s$


### CELL ARRANGEMENTS

#### 1. Series arrangement



$$\text{Total emf } E = E_1 + E_2 + E_3$$

#### 2. Parallel arrangement

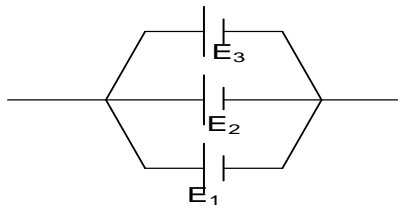


When cells of equal emf are connected in parallel

$$\text{Total emf } E = E_1 = E_2 = E_3$$
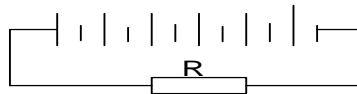
#### Example


- Find the total *emf* in each of the following circuits if each cell is of *emf* 1.5V
  -



#### Solution

$$\begin{aligned} \text{Total emf } E &= 1.5 + 1.5 + 1.5 + 1.5 + 1.5 + 1.5 \\ &= 9.0V \end{aligned}$$


(ii)

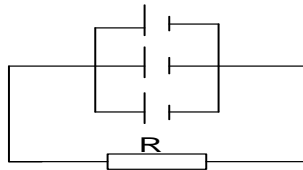

#### Solution

$$\text{Total emf } E = 1.5V$$

(iii)

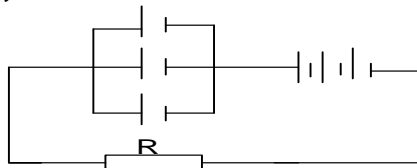

#### Solution

$$\begin{aligned} \text{Total emf } E &= 1.5 + 1.5 + 1.5 + 1.5 \\ &= 6.0V \end{aligned}$$

**Note:** If the cells are connected in parallel and have internal resistance, their resistance is calculated as resistors in parallel.


#### Advantages of series arrangement of cells over the parallel arrangement

In series arrangement the effective e.m.f is greater than the individual e.m.f of the cells and hence a greater current is drawn from the series combination than in the parallel combination.

However the series arrangement has a disadvantage of all the cells being drained at once thus the cells have a shorter life span.

#### Examples

1. Find the ammeter reading

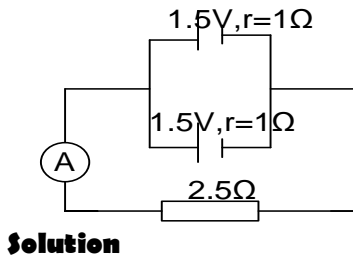

$$E = I(R + r)$$

$$r = \frac{1 \times 1}{1 + 1}$$

$$r = 0.5\Omega$$


$$1.5 = I(2.5 + 0.5)$$

$$I = \frac{1.5}{3}$$

$$I = 0.5A$$

2. Two cells of *emf* 2.0V and internal resistance 0.2Ω each are connected together in parallel to form a battery. This battery is connected to a lamp of resistance 0.9Ω. Calculate the current through the lamp and voltage across the lamp.

**Solution**

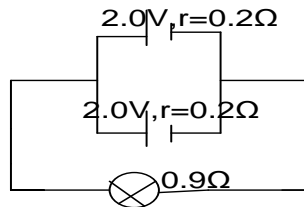

$$E = I(R + r)$$

$$r = \frac{0.2 \times 0.2}{0.2 + 0.2}$$

$$r = 0.1\Omega$$

current through the lamp

$$2 = I(0.9 + 0.1)$$

$$I = \frac{2}{1}$$

$$I = 2A$$

voltage across the lamp


$$V = IR$$

$$V = 2 \times 0.9$$

$$V = 1.8V$$

3. Four cells each of *emf* 1.5V and internal resistance 0.5Ω are connected in series. What current will flow through an external resistor of 22Ω

**Solution**

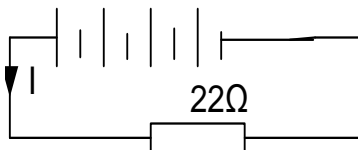

$$\text{Total emf } E = 1.5 \times 4$$

$$E = 6V$$

Total internal resistance  $r = 0.5 \times 4$

$$r = 2\Omega$$

$$E = I(R + r)$$

$$6 = I(22 + 2)$$


$$I = \frac{6}{24}$$

$$I = 0.25A$$

4. A battery containing 8 cells each of *emf* 1.5V and internal resistance 0.5Ω is connected to two other resistors of 4Ω and 16Ω. Calculate the minimum and maximum current that can flow through the battery.

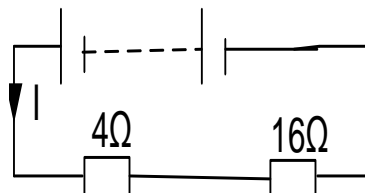**Solution**

For minimum current the resistors must be connected in series



$$\text{Total emf } E = 1.5 \times 8$$

$$E = 12V$$

$$\text{Total internal resistance } r = 0.5 \times 8$$

$$r = 4\Omega$$

$$\text{Total external resistance } R = 4 + 16$$


$$E = I(R + r)$$

$$12 = I(16 + 4 + 4)$$

$$I = \frac{12}{24}$$

$$I = 0.5A$$

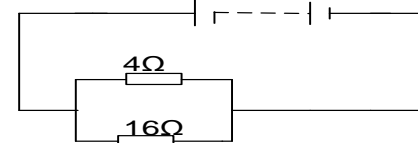For maximum current the resistors must be connected in parallel



$$\text{Total emf } E = 1.5 \times 8$$

$$E = 12V$$

Total internal resistance  $r = 0.5 \times 8$   
 $r = 4\Omega$   
 Total external resistance  $R = \frac{4 \times 6}{4+6}$   
 $R = 3.2\Omega$

$E = I(R + r)$   
 $12 = I(3.2 + 4)$   
 $I = \frac{12}{7.2}$   
 $I = 1.67A$

**WORK DONE BY AN ELECTRIC CURRENT(ELECTRICAL ENERGY)**

If the P.d,  $V$  is applied to the ends of a conductor and quantity of electricity,  $Q$  flows then

$work\ done = QV$  but  $Q = It$

$W = ItV$

$W = IVt$

but  $V = IR$

$W = I(IR)t$

$W = I^2 R t$

but  $I = \frac{V}{R}$

$W = \left(\frac{V}{R}\right)^2 R t$

$W = \frac{V^2 t}{R}$

The work done is transferred into internal molecular energy accompanied by a rise in temperature subsequently, this energy may be given out in form of heat

**ELECTRICAL POWER**

This is the rate of doing work by an electric current.

$power = \frac{work\ done}{time\ taken}$

$P = \frac{IVt}{t}$

$P = IV$

Also

$power = \frac{work\ done}{time\ taken}$

$P = \frac{I^2 R t}{t}$

Also

$P = I^2 R$


$power = \frac{work\ done}{time\ taken}$

$P = \frac{V^2 t}{R t}$

$P = \frac{V^2}{R}$

**Examples**

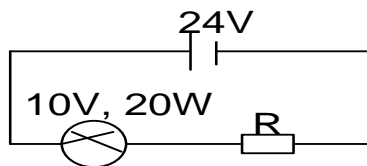1. A battery of  $emf\ 24V$  is connected in series with aresistance  $R$  and a lamp rated  $10V, 20W$  as shown below.



if the bulb is operating normally . Find,

- i) the p.d across the resistor
- ii) the value of  $R$
- iii) power dissipated in the resistor

**Solution**

i)  $p.d$  across the resistor  
 $= (24 - 10)V$   
 $= 14V$

ii) Current through the bulb  
 $I = \frac{P}{V}$   
 $I = \frac{20}{10}$


$I = 2A$   
 Bulb and resistor have the same current

$R = \frac{V}{I}$   
 $R = \frac{14}{2}$   
 $R = 7\Omega$

iii) power dissipated in the resistor

$P = I^2 R$   
 $P = 2^2 \times 7$   
 $P = 28W$

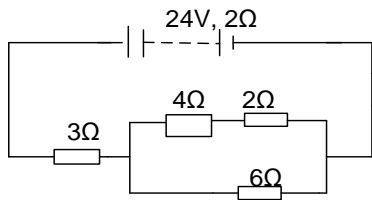
2. An accumulator of  $emf\ 24V$  and internal resistance  $2\Omega$  is connected in a circuit as shown below.



- calculate the current through the 6Ω resistor
- calculate the power expended in the 6Ω resistor
- find the total power expended

**Solution**

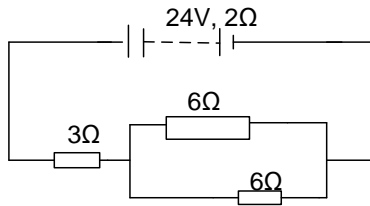a) for 4Ω and 2Ω resistors  
total resistance  $R = (4 + 2)$   
 $R = 6\Omega$



$$\text{Total resistance} = \left[ 3 + \left( \frac{6 \times 6}{6 + 6} \right) \right]$$

$$= 6\Omega$$

$$E = I(R + r)$$

$$24 = I(6 + 2)$$

$$I = \frac{24}{8}$$

$$I = 3A$$

p.d through parallel combination

$$V = IR$$

$$V = 3 \times \left( \frac{6 \times 6}{6 + 6} \right)$$

$$V = 9V$$

Current through the 6Ω resistor

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{9}{6}$$

$$I = 1.5A$$

b) power in 6Ω resistor

$$P = IV$$

$$P = 1.5 \times 9$$

$$P = 13.5W$$

c) total power =  $I E$


$$= 3 \times 24$$

$$= 72W$$

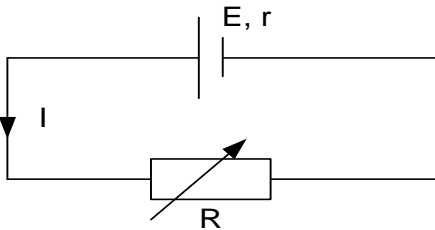**Power out put and efficiency**

Efficiency of the battery is the ratio of the useful power expended in the total external load to the power generated or supplied by the battery.

Usually efficiency is expressed in percentage and is denoted by  $\eta$



Power delivered to resistor,  $P_{out} = IV$

Power supplied by cell,  $P_{IN} = IE$

$$\text{Efficiency, } \eta = \frac{\text{Power output}}{\text{Power input}} \times 100\%$$

$$\eta = \frac{IV}{IE} \times 100\%$$

$$\eta = \frac{V}{E} \times 100\%$$

but  $E = I(R + r)$  and  $V = IR$

$$\eta = \left( \frac{R}{R + r} \right) \times 100\%$$

**Example**

A battery of e.m.f 18.0V and internal resistance 3.0Ω is connected to a resistor of resistance 8Ω. Calculate the

- power generated
- efficiency
- 

**Solution**

$$P_{gen} = IE = \left( \frac{E}{R + r} \right) E$$

$$P_{gen} = \left( \frac{18 \times 18}{8 + 3} \right) = 29.45W$$

$$\eta = \frac{\text{Power output}}{\text{Power input}} \times 100\%$$

$$\eta = \frac{IV}{IE} \times 100\%$$

but  $E = I(R + r)$  and  $V = IR$

$$\eta = \left( \frac{R}{R + r} \right) \times 100\%$$

$$\eta = \left(\frac{8}{8+3}\right) \times 100\%$$

$$\eta = 72.7\%$$

### Maximum power output

Suppose the load resistance  $R$  is variable then the useful power expended in  $R$  will also vary and will be maximum when  $R = r$ .

$$\text{Power output} = IV = \left(\frac{E}{R+r}\right) \times \left(\frac{ER}{R+r}\right)$$

$$\text{Power output, } P_0 = \frac{E^2}{(R+r)^2} R$$


At maximum power,  $P_m$ ,  $\frac{dP_0}{dR} = 0$

$$\frac{dP_0}{dR} = E^2 \frac{[(R+r)^2 - 2R(R+r)]}{(R+r)^4} = 0$$


As  $R$  tends to zero,  $P$  tends to zero

As  $R$  tends to  $\infty$ ,  $P$  tends to zero.

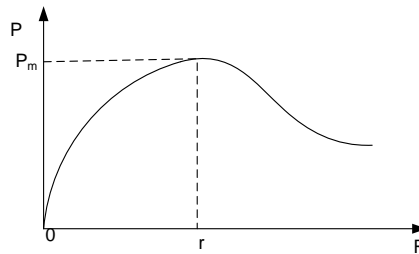A graph of power out put  $P$  against load resistance  $R$  is shown below.




### Variation of $\eta$ and $P$ with $R$

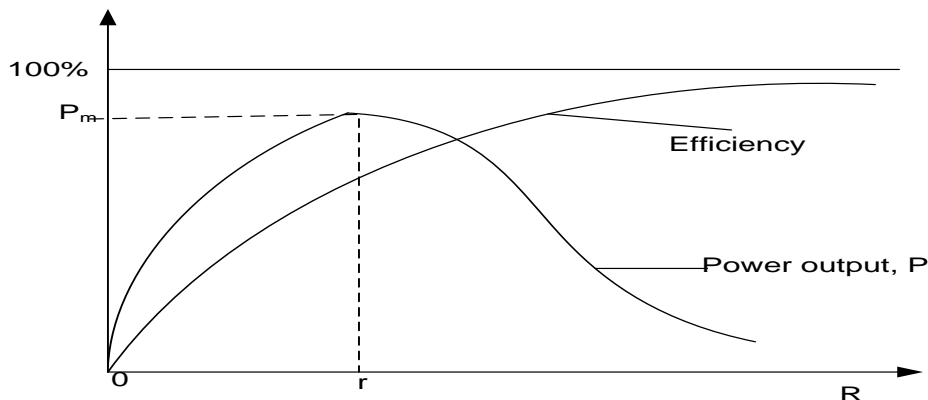

For values of  $R$  less than  $r$ , power output increases and attains a maximum value when  $R = r$ . For
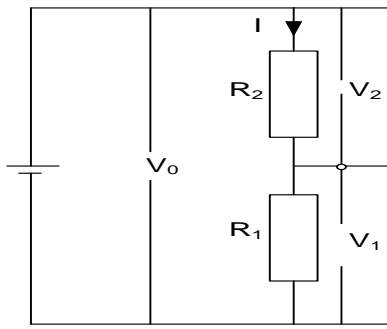
### The Potential Divider

The potential divider is used to obtain a fraction of a given p.d. The fraction can be fixed or variable.



Total resistance in the circuit,  $R = R_1 + R_2$ .

$$V_0 = I R$$


$$V_0 = I (R_1 + R_2)$$

$$I = \frac{V_0}{R_1 + R_2}$$

$$V_1 = I R_1$$

$$V_1 = \left( \frac{V_0}{R_1 + R_2} \right) R_1$$

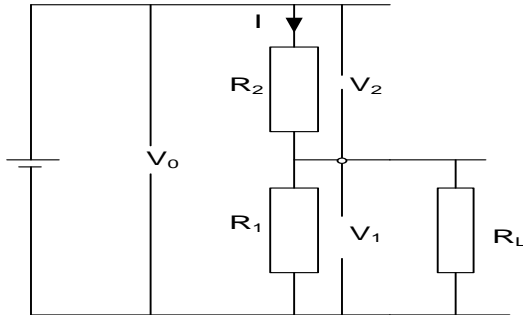Suppose a load of resistance  $R_L$  is connected in parallel with  $R_1$ .



$$R_p = \frac{R_1 R_L}{R_1 + R_L}$$

Effective resistance in the circuit,  $R = R_p + R_2$

Total current in the circuit,  $I = \frac{V_0}{R_p + R_2}$


Hence  $V_1 = I R$

$$V_1 = \left( \frac{V_0}{R_p + R_2} \right) R_p$$

Let the effective resistance of  $R_1$  and  $R_L$  be  $R_p$ .

### Example

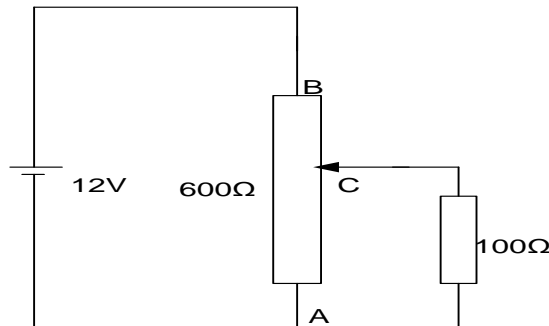1. A 12V battery is connected across a potential divider of resistance  $600\Omega$  as shown below. If the load of  $100\Omega$  is connected across the terminals A and C when the slider is half way up the divider, find:



- (i) p.d across the load
- (ii) p.d across a and c when the load is removed.

### Solution

- (i) Effective resistance

$$R = \frac{300 \times 100}{300 + 100} + 300 = 375\Omega$$

current supplied by the battery,  $I = \frac{V}{R}$

$$I = \frac{12}{375} = 0.032A$$

hence current through parallel combination of resistors =  $0.032A$

### Exercise

p.d across parallel combination of resistors,

$$V = IR = 0.032 \times \left( \frac{300 \times 100}{300 + 100} \right) = 2.4V$$


Hence the p.d across the load is  $2.4V$ .

- (ii) when the load is removed

$$I = \frac{12}{600} = 0.02A$$

Hence p.d across AC =  $0.02 \times 300 = 6V$

1.

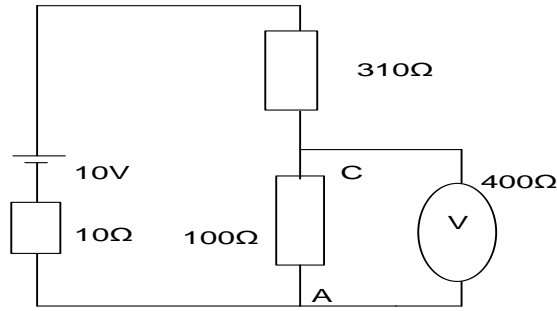


- (i) Find the reading of the voltmeter
  - (ii) Calculate the power dissipated in the  $10\Omega$  resistor
2. A resistor of  $500\Omega$  and one of  $200\Omega$  are placed in series with a  $6V$  supply. What will be the reading on a voltmeter of internal resistance  $2000\Omega$  when placed across
- (i) the  $500\Omega$  resistor
  - (ii)  $200\Omega$  resistor.

### WHEATSTONE BRIDGE

It is a bridge circuit consisting of four resistances  $R_1, R_2, R_3, R_4$  and a sensitive centre - zero galvanometer, G.

#### Balance condition for a wheatstone

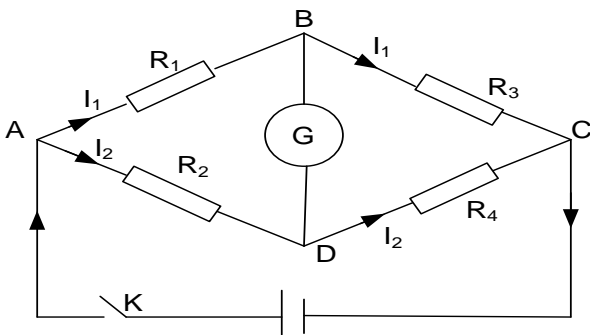

Switch K is closed and the resistance  $R_1, R_2, R_3$  and  $R_4$  adjusted until the galvanometer shows no deflection.  
At balance condition B and D are at the same potential.

P.d across AB, = p.d across AD,

$$I_1 R_1 = I_2 R_2 \dots \dots \dots (1)$$

Current flowing through  $R_3$  is therefore  $I_1$  and that through  $R_4$  is  $I_2$

P.d across BC, = p.d across DC,

$$I_1 R_3 = I_2 R_4 \dots \dots \dots (2)$$

Eqn(1)  $\div$  (2)

$$\frac{I_1 R_1}{I_1 R_3} = \frac{I_2 R_2}{I_2 R_4}$$

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

Equation in the box is called the balance condition of a Wheatstone bridge.


**NOTE :**

A wheatstone bridge is not suitable for measuring very low and very high resistances

**Explanation**

- ❖ When the resistances are very low, resistances of connecting wires become comparable to the test resistances. Errors in the measured values therefore become significant
- ❖ When the resistances are very high, the current flowing becomes very small. The galvanometer becomes less sensitive hence difficulty in determining the balance value

**Examples**

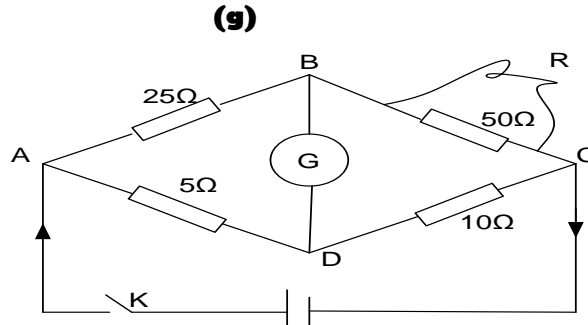

When the switch is closed the galvanometer shows no deflection when the 50Ω resistor is shunted with a resistance R, find the value of R

**Solution**

Let  $R_p$  be the total resistance of  $R \Omega$  and  $50\Omega$  that are in parallel.

$$\therefore R_p = \frac{50R}{50 + R} \Omega$$

Then at balance;

$$\frac{R_1}{R_3} = \frac{R_2}{R_4} \Rightarrow \frac{25}{R_p} = \frac{5}{10} \quad \therefore R_p = 12.5\Omega$$

$$\therefore 12.5 = \frac{50R}{50 + R}$$

$$\therefore R = 16.67\Omega$$

- (h) In a Wheatstone bridge, the ratio arms  $R_1$  and  $R_2$  are approximately equal. When  $R_3 = 500\Omega$ , the bridge is balanced. On interchanging  $R_1$  and  $R_2$ , the value of  $R_3$  for balancing is  $505\Omega$ . Find the value of  $R_4$  and the ratio  $R_1 : R_2$ . **An(502.5Ω, 1:1.005)**

**The Metre Bridge or Slide Wire**


The simple metre bridge is the practical form of a Wheatstone bridge.

It consists of a uniform resistance wire 1 m long lying alongside or on a metre rule scale.

Thick copper or brass strips of low resistance connect various parts of the metre bridge.

Since the wire is uniform its resistance per cm is constant. The resistance of wire between any two points on the wire is proportional to the length separating them.

$$R_{AC} = kl_1$$

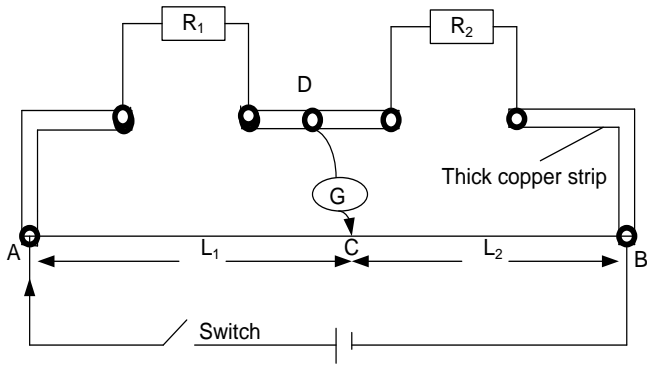

**Balance condition**

On closing switch K, the jockey is tapped along AB until a point is found when the

galvanometer shows no deflection. At balance point, D and C are at the same potential.

p.d across  $R_1 =$  p.d across  $l_1$

p.d across  $R_2 =$  p.d across  $l_2$

but current through  $R_1 =$  current through

$R_1 = I_1$  and current through AB =  $I_2$

$$I_1 R_1 = I_2 r l_1 \dots\dots\dots 1$$

$$I_1 R_2 = I_2 r l_2 \dots\dots\dots 2$$

Where  $r$  is resistance per cm of wire AB.

Divide equation 1 by 2

$$\frac{I_1 R_1}{I_1 R_2} = \frac{I_2 r l_1}{I_2 r l_2} \dots\dots\dots 3$$

$$\boxed{\frac{R_1}{R_2} = \frac{l_1}{l_2}}$$

**End – errors**

$R_2$  should be chosen such that the balance point, C is fairly near the centre of the wire (between 30 and 70 cm). This minimizes errors in the result and gives a more accurate value because the end –errors from both ends will be evenly distributed. A better result can be obtained by interchanging  $R_1$  and  $R_2$  and obtaining a second pair of values of  $l$  and  $l$ . An average value of  $R_1$  can then be taken.

If either  $l$  or  $l$  is very small, the resistance of the end connections is not negligible and must be added to  $R_{AC}$  or  $R_{CB}$ .

Let the end connection errors be equivalent to lengths  $e_1$  and  $e_2$  from A and B respectively.


Equation 3 then becomes;  $\boxed{\frac{R_1}{R_2} = \frac{l_1 + e_1}{l_2 + e_2}}$

**Note**

The metre bridge is therefore unsuitable for very low resistances because the contact resistances become comparable to the test

resistances. It is equally not suitable for very high resistances because the galvanometer becomes insensitive

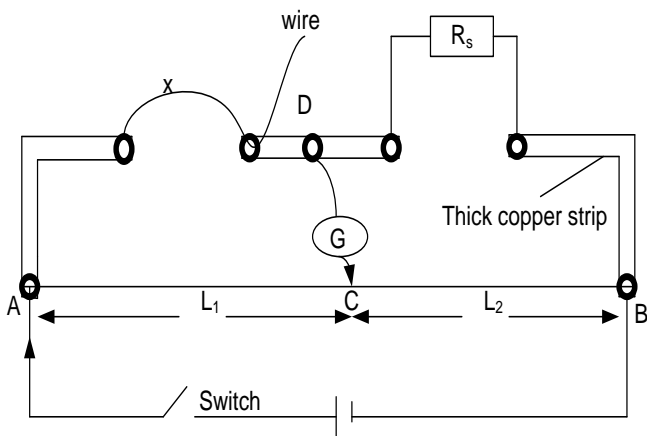**To determine the resistivity of a material in form of a wire**




- ❖ With a micrometer screw gauge measure the diameter  $d$ , of the wire and the cross-sectional area  $A$ , of the wire determined from  $A = \frac{\pi d^2}{4}$ .
- ❖ Connect a length  $x$  of the wire across the left hand gap and a standard resistance  $R_s$  in the right hand gap as shown above.
- ❖ Close switch K and tap the jockey along AB until you locate a point for which the galvanometer shows no deflection.
- ❖ Measure and record the balance lengths  $l_1$  and  $l_2$
- ❖ Determine the resistance R of the wire from

$$R_x = R_s \frac{l_1}{l_2}$$

- ❖ Repeat the procedure for different values of  $x$  and tabulate the results in a suitable table.

**Example:**

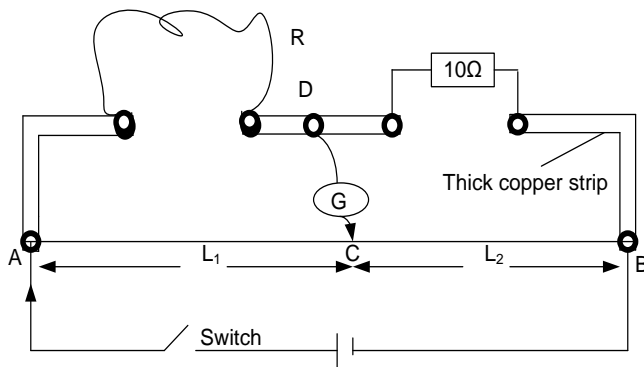1. A 110cm length of wire of diameter 0.85mm is placed in the left hand gap of a metre bridge and standard  $10\Omega$  coil being placed in the right hand gap.



- ❖ Plot a graph of  $R_x$  against  $x$  and determine the slope  $s$  of the graph.
- ❖ Determine the resistivity of the wire from  $\rho = SA$

Balance length obtained was 46.7cm from end of the bridge. Calculate the resistivity of the wire.

**Solution**


**At balance;**  $\frac{R}{46.7} = \frac{10}{53.6}$   
 $\therefore R = 8.713\Omega$

$$\therefore \rho = \frac{RA}{L} = \frac{R\pi d^2}{L \times 4}$$

$$\rho = \frac{8.713 \times 3.14 \times (0.85 \times 10^{-3})^2}{1.1 \times 4}$$

$$\rho = 4.5 \times 10^{-6} \Omega m$$

2.

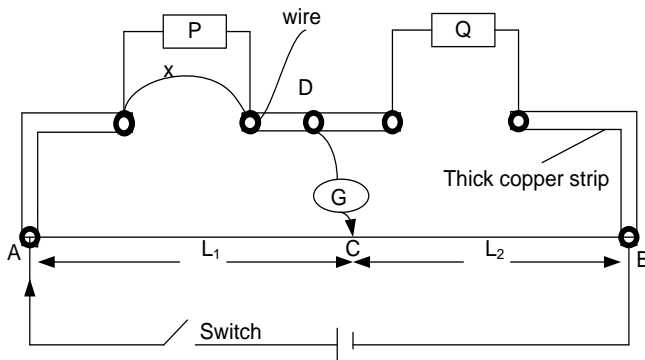

In the diagram below, resistors P and Q are  $5\Omega$  and  $2\Omega$  respectively. A wire X of length 60.0 cm and diameter 0.02 mm is connected across P so that the balance point is 66.7 cm from A. Calculate the resistivity of the wire.

**Solution:**

Let the effective resistance of P and X be R

When G shows no deflection, there is balance, hence

$$\frac{R}{Q} = \frac{l_1}{l_2}$$

$$\frac{R}{33.3} = \frac{66.7}{33.3}$$

$$\frac{R}{2} = \frac{66.7}{33.3}$$

$$R = 4 \Omega$$

But  $R = \frac{PX}{P+X}$

$$\therefore 4 = \frac{5X}{5+X}$$

$$X = 20 \Omega$$

Length,  $l$  of X = 60 cm = 0.60 m and diameter,  $d = 0.02$  mm

Cross sectional area of X,  $A = \frac{\pi d^2}{4}$

$$A = \frac{\pi}{4} \times (0.02 \times 10^{-3})^2 = 3.14 \times 10^{-10} \text{ m}^2$$

From  $R = \frac{\rho l}{A}$ , it follows that  $\rho = \frac{RA}{l}$

$$\rho = \frac{20 \times 3.14 \times 10^{-10}}{0.6}$$

$$\rho = 1.05 \times 10^{-8} \Omega \text{ m}$$

3. A material of a wire of length 120cm and cross-sectional area  $0.04 \text{ cm}^2$  has a resistance as  $0.5 \Omega$  at  $0^\circ\text{C}$ . Find the resistivity of metal at  $300^\circ\text{C}$ , given temperature coefficient of resistance as  $7.5 \times 10^{-3} \text{ K}^{-1}$ .

**Solution**

$$R_\theta = R_0(1 + a\theta)$$

$$R_{300} = 0.5(1 + 7.5 \times 10^{-3} \times 300)$$

$$= 1.625 \Omega$$

$$\therefore \rho = \frac{RA}{L} = \frac{1.625 \times 0.04 \times 10^{-4}}{1.2}$$

$$\rho = 5.42 \times 10^{-6} \Omega \text{ m}$$

4. Find length of a wire of diameter 1.5mm and resistivity  $2 \times 10^{-6}$  at  $30^\circ\text{C}$  needed to make a coil of resistance  $4 \Omega$  at  $125^\circ\text{C}$ , if temperature coefficient of resistance is  $2.5 \times 10^{-3} \text{ K}^{-1}$ .

**Solution:**

$$R_\theta = R_0(1 + a\theta)$$

Resistance at  $30^\circ\text{C}$ :

$$R_{30} = R_0(1 + 2.5 \times 10^{-3} \times 30).$$

$$R_{30} = 1.075R_0 \dots \dots \dots (i)$$

Resistance at  $125^\circ\text{C}$ :

$$R_{125} = R_0(1 + 2.5 \times 10^{-3} \times 125)$$

$$R_{125} = 1.3125R_0 \dots \dots \dots (ii)$$

But  $R_{125} = 4 \Omega$

$$4 = 1.3125R_0$$

$$R_0 = 3.048 \Omega$$

$$R_{30} = 1.075R_0$$

$$R_{30} = 1.075 \times 3.048 = 3.28 \Omega$$

$$R = \frac{\rho L}{A}$$


We are required to find length at  $30^\circ\text{C}$

$$L = \frac{RA}{\rho} = \frac{R_{30}A}{\rho_{30}} \text{ and } A = \frac{\pi d^2}{4}$$

$$L = \frac{3.28 \times \pi (1.5 \times 10^{-3})^2}{2 \times 10^{-6} \times 4}$$

$$L = 2.9 \text{ m}$$

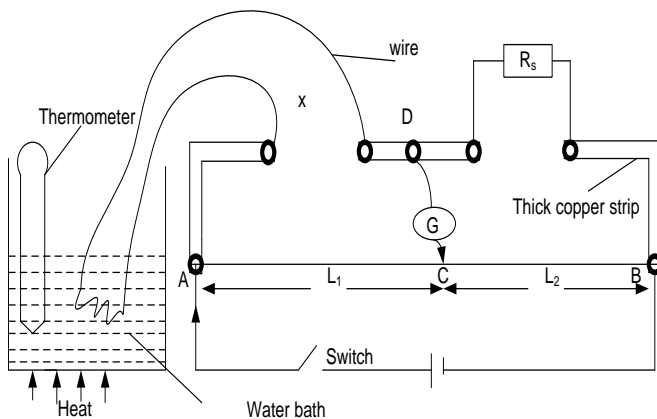**To Determine the Temperature Coefficient of Resistance of a Material**



- ❖ A specimen fine wire is made into a coil and immersed in a water bath placed.
- ❖ The ends of the coil are connected in the left hand gap of the meter bridge and a standard resistance  $R_s$  in the right hand gap.
- ❖ The water bath is heated to a suitable temperature  $\theta$  and stirred to ensure uniform temperature.
- ❖ Switch K is closed and the jockey tapped at different points on a uniform wire AB until a point is found where the galvanometer shows no deflection.
- ❖ The balance lengths  $l_1$  and  $l_2$  are measured and recorded.

- ❖ The resistance  $R_\theta$  of the coil at temperature  $\theta$  is determined from

$$R_\theta = R_s \frac{l_1}{l_2}$$

- ❖ The experiment is repeated for different values of temperature,  $\theta$  and the results tabulated.

**Example:**

1. A resistance coil is connected across the left hand gap of a metre bridge. When a  $5.0 \Omega$  standard resistor is connected across the right hand gap and the coil is immersed in an ice – water mixture, the balance point is at a point  $45.0$  cm from the left hand end. When the coil is immersed in a steam bath at  $100^\circ\text{C}$ , the balance point shifts to a point  $52.8$  cm from the left hand end of the bridge. Find the temperature coefficient of the material of the coil.

**Solution:**

At  $0^\circ\text{C}$ ; Using the balance condition

$$\frac{R_o}{R_s} = \frac{l_1}{l_2}$$

$$R_o = \frac{45}{55} \times 5 = 4.09\Omega$$

At  $100^\circ\text{C}$ : resistance at  $100^\circ\text{C}$  be  $R_{100}$

$$\frac{R_{100}}{R_s} = \frac{l_1}{l_2}$$

- ❖ A graph of  $R_\theta$  against  $\theta$  is plotted.
- ❖ The intercept  $R_o$  on the  $R_\theta$  - axis is read and the slope,  $S$  of the graph is determined.
- ❖ The temperature coefficient of resistance of the material is calculated from  $\alpha = \frac{S}{R_o}$ .

$$R_{100} = \frac{52.8}{47.8} \times 5 = 5.59\Omega$$

$$\alpha = \frac{R_{100} - R_o}{\Delta\theta R_o}$$

$$\alpha = \frac{5.59 - 4.09}{4.09 \times (100 - 0)}$$

$$\alpha = 3.6 \times 10^{-3} \text{K}^{-1}$$

2. A resistance coil consists of a nichrome wire of diameter  $4 \times 10^{-4} \text{m}$  and length  $\frac{\pi}{2}$ . The coil is connected across the left hand gap of a metre bridge. When a  $10 \Omega$  standard resistor is connected across the right hand gap and the coil is immersed in an ice – water mixture, the balance point is at a point  $60.0$  cm from the left hand end.

- (i) Find the resistivity of nichrome wire and its resistance at  $0^\circ\text{C}$
- (ii) What would the balance length be when the coil is immersed in a steam bath at  $100^\circ\text{C}$  ( temperature coefficient of the nichrome wire between  $0^\circ\text{C}$  and  $100^\circ\text{C}$  is  $1.7 \times 10^{-4} \text{K}^{-1}$ )

**Solution:**

- (i) At  $0^\circ\text{C}$ ;

Using the balance condition we have;

$$\frac{R_o}{R_s} = \frac{l_1}{l_2}$$

$$R_o = \frac{60}{40} \times 10 = 15\Omega$$

$$\rho = \frac{RA}{L} \text{ and } A = \frac{\pi d^2}{4}$$

$$\rho_o = \frac{15 \times \pi (4 \times 10^{-4})^2}{4 \times \frac{\pi}{2}}$$

$$\rho_o = 1.2 \times 10^{-6} \Omega \text{m}$$

- (ii)  $R_{100} = R_o(1 + 100\alpha)$

$$R_{100} = 15(1 + 1.7 \times 10^{-4} \times 100)$$

$$R_{100} = 15.26\Omega$$

At  $100^\circ\text{C}$

$$\frac{R_{100}}{R_s} = \frac{l_1}{l_2}$$

$$\frac{15.26}{10} = \frac{l}{100 - l}$$

$$l = 60.4 \text{cm}$$

3. A nickle wire and a  $10 \Omega$  standard resistor are connected across the gaps of a meter bridge. When the nickel wire was at  $0^\circ\text{C}$ , balance point was found  $40.0$  cm from the end of the bridge wire adjacent to the nickel wire. When the nickel wire was at  $100^\circ\text{C}$ , the balance point shifts to a point  $50.0$  cm. Find the temperature of the nickel wire when the balance point was at  $42.0$ cm and the resistivity of nickel at this temperature. ( length of the wire is  $150$ cm and cross-sectional area is  $2.5 \times 10^{-4} \text{cm}^2$ )

**Solution:**

At 0°C ; Using the balance condition

$$\frac{R_o}{R_s} = \frac{l_1}{l_2}$$

$$R_o = \frac{40}{60} \times 10 = 6.67\Omega$$

At 100°C: resistance at 100°C be  $R_{100}$

$l_1 = 50 \text{ cm}, l_2 = 100 - 50 = 50 \text{ cm}$

$$\frac{R_{100}}{R_s} = \frac{l_1}{l_2}$$

$$R_{100} = \frac{50}{50} \times 10 = 10\Omega$$

$$\alpha = \frac{R_{100} - R_o}{\Delta\theta R_o}$$

$$\alpha = \frac{10 - 6.67}{6.67 \times (100 - 0)}$$

$$\alpha = 5.0 \times 10^{-3} \text{K}^{-1}$$

when the balance length is 42cm let the resistance be  $R_\theta$

$$R_\theta = \frac{42}{58} \times 10 = 7.24\Omega$$

$$R_\theta = R_o(1 + \theta\alpha)$$

$$7.24 = 6.67(1 + 5.0 \times 10^{-3}\theta)$$

$$\theta = 17.24^\circ\text{C}$$

$$\rho = \frac{RA}{L}$$

$$\rho_\theta = \frac{7.24 \times 2.5 \times 10^{-4} \times 10^{-4}}{1.5}$$

$$\rho_\theta = 1.21 \times 10^{-7} \Omega \text{ m}$$

4. When a coil x is connected across the Left hand gap of a metre bridge and heated to a temperature of 30°C, the balance point is found to be 51.5cm from the left hand side of the slide wire. when the temperature is raised to 100°C, the balance point is 54.6cm from the left hand side. Find the temperature coefficient of resistance of x.

**Solution**

$$\frac{R_1}{R_2} = \frac{l_1}{l_2}$$

$$R_{30} = \frac{51.5}{100 - 51.5} R_x = 1.06R_x$$

$$R_{100} = \frac{54.6}{100 - 54.6} R_x = 1.203R_x$$

$$R_{30} = R_o(1 + 30\alpha) \dots \dots \dots (i)$$

$$R_{100} = R_o(1 + 100\alpha) \dots \dots \dots (ii)$$


$$\frac{R_{30}}{R_{100}} = \frac{R_o(1 + 30\alpha)}{R_o(1 + 100\alpha)} = \frac{1.06R_x}{1.203R_x}$$

$$\alpha = 2.01 \times 10^{-3} \text{K}^{-1}$$

**Exercise**

- Two resistance coils P and Q are placed in the gaps of a metre bridge. A balance point is found when the movable contact touches the bridge wire at a distance of 35.5cm from the end joined to end P. When the coil Q is shunted with a resistance of 10Ω, the balance point is moved through a distance of 15.5cm. Find the values of the resistances P and Q.
- In a metre bridge when a resistance in left gap is 2Ω and unknown resistance in right gap, the balance point is obtained from the zero end at 40cm on the bridge wire. On shunting the unknown resistance with 2Ω, find the shift of the balance point on the bridge wire. **An (22.5cm)**
- With a certain resistance in the left gap of a slide wire, the balancing point is obtained when a resistance of 10Ω is taken out from the resistance box. On increasing the resistance from the resistance box by 12.5Ω, the balancing point shifts by 20cm. Find the value of unknown resistance. **An(15Ω)**
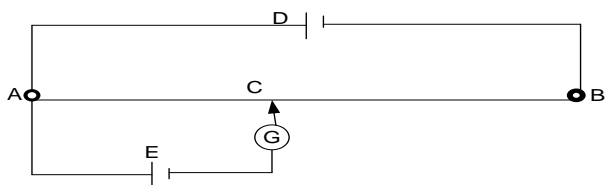
## PRINCIPLE OF POTENTIOMETER SLIDE- WIRE




- ❖ A driver cell **D**, maintains a constant current through the slide wire.

- ❖ The wire is uniform hence has a constant resistance per cm and therefore the p.d per cm is also constant.
- ❖ Knowing the p.d per cm of the slide wire any p.d can be determined by balancing it against a known length of the wire
- ❖ If p.d per cm is  $k$  and balance length is  $l$  then the required p.d is  $V = kl$

**NB:** The slider or jockey must not be scrapped on the potentiometer wire otherwise the wire will become non-uniform when scrapped.
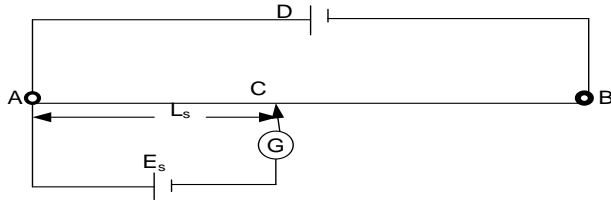
### **Standardization (calibration) of a potentiometer wire**

This refers to determining the p.d per cm of a potentiometer wire using a standard cell so that it can be used to measure p.ds.




- ❖ Connect a standard cell of e.m.f  $E_s$  as shown above.

- ❖ The sliding contact is moved along the uniform wire AB until a point is found where the galvanometer G shows no deflection.
- ❖ The balance length  $l_s$  is measured.
- ❖ At balance point,  $E_s = \text{p.d across AC}$ .  
 $\therefore E_s = kl_s$   
 $\Rightarrow k = \frac{E_s}{l_s}$  where  $k = \text{calibration constant}$

### Applications of the potentiometer
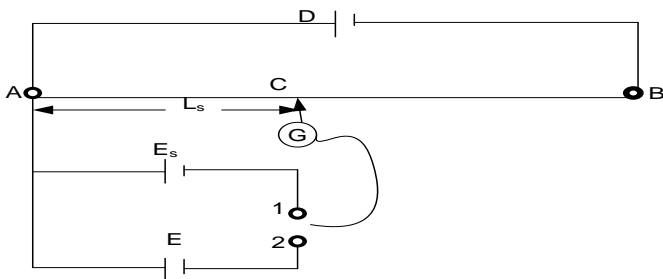
#### To Measure e.m.f of a cell by comparison



- ❖ Connect a standard cell of e.m.f  $E_s$  and the cell of unknown e.m.f  $E$  as shown above.
- ❖ With galvanometer connected to position 1, the jockey is tapped at different points along


- wire AB until a point is found where the galvanometer G shows no deflection.
- ❖ Measure the balance length  $l_s$ .
- ❖ With galvanometer connected to position 1, the jockey is tapped at different points along wire AB until a point is found where the galvanometer G shows no deflection.
- ❖ Measure the balance length  $l$ .
- ❖ The e.m.f of the test cell is got from

$$E = \left(\frac{l}{l_s}\right) E_s$$

#### Example:

A standard cell of e.m.f  $1.5\text{ V}$  is balanced on a potentiometer wire by a length of  $60.0\text{ cm}$ . Another cell of unknown e.m.f,  $E$  is balanced on the same potentiometer wire by a length of  $75.0\text{ cm}$ . Calculate the value of  $E$ .

#### Solution:

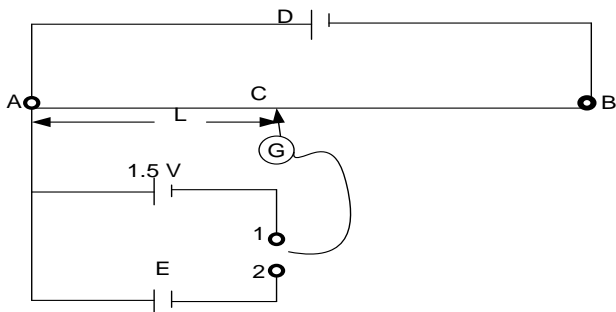


When G is at 1, the standard cell is balanced. At balance, p.d across AC = e.m.f of the standard cell

$$E = \left(\frac{l}{l_s}\right) E_s$$

$$E = \left(\frac{75}{60}\right) \times 1.5$$

$$E = 1.88\text{ V}$$
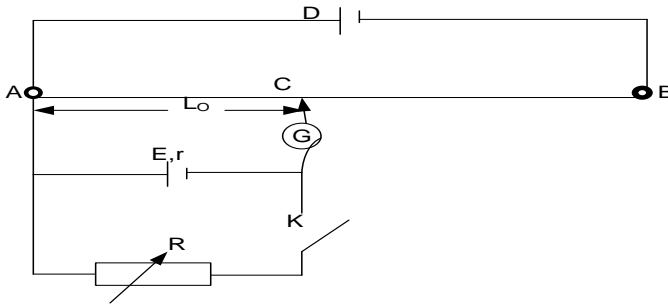
#### To measure the internal resistance, $r$ of a cell.



- Connect the cell and a resistance box  $R$ , as shown above.

### Theory of experiment

At balance when  $K$  is open, the cell is on an open circuit and p.d across  $AC$  is equal to e.m.f of cell.

$$E = k l_0 \dots\dots\dots 1$$

When  $K$  is closed the cell supplies current to  $R$  and is now on a closed circuit.

At balance p.d across  $R =$  p.d across  $AC$

$$V = k l \dots\dots\dots 2$$

Divide equation 1 by 2

- With switch  $K$  open, tap the jockey at different positions along the slide wire  $AB$  until you locate a point at which the galvanometer shows no deflection.
- Measure the balance length  $l_0$
- Set the resistance box to a suitable value  $R$  and then close switch  $K$ .
- Tap the jockey at different positions along  $AB$  until a point  $C$  at which the galvanometer shows no deflection is located.
- Measure and record the balance length  $AC = l$ .
- Internal resistance of cell,  $r = R \left( \frac{l_0}{l} - 1 \right)$

$$\frac{E}{V} = \frac{l_0}{l} \dots\dots\dots 3$$

$$E = I(R + r) \text{ and } V = IR$$

Substitute for  $E$  and  $V$  in equation 3

$$\frac{I(R + r)}{IR} = \frac{l_0}{l}$$

$$r = R \left( \frac{l_0}{l} - 1 \right)$$

### Example:

1. A dry cell gives a balance length of 84.8 cm on a potentiometer wire. When a resistor of resistance  $15\Omega$  is connected across the terminals of the cell, a balance length of 75.0 cm is obtained. Find the internal resistance of the cell.

#### Solution

$$\frac{E}{V} = \frac{l_0}{l}$$

$$E = I(R + r) \text{ and } V = IR$$

$$\frac{I(R + r)}{IR} = \frac{l_0}{l}$$

$$r = R \left( \frac{l_0}{l} - 1 \right)$$

$$r = 15 \left( \frac{84.8}{75} - 1 \right)$$

$$r = 1.96\Omega$$

2. The e.m.f of a battery  $A$  is balanced by a length of 75.0cm on a potentiometer wire. The e.m.f of a standard cell of 1.02V is balanced by a length of 50.0cm. Find;
  - (i) E.m.f of battery  $A$
  - (ii) The new balance length if  $A$  has internal resistance of  $2\Omega$  and a resistor of  $8\Omega$  is connected across its terminals

#### Solution

$$E = \left( \frac{l}{l_s} \right) E_s$$

$$E = \left( \frac{75}{50} \right) \times 1.02$$


$$E = 1.53V$$

$$r = R \left( \frac{l_0}{l} - 1 \right)$$

$$2 = 8 \left( \frac{75}{l} - 1 \right)$$

$$l = 60cm$$

3.

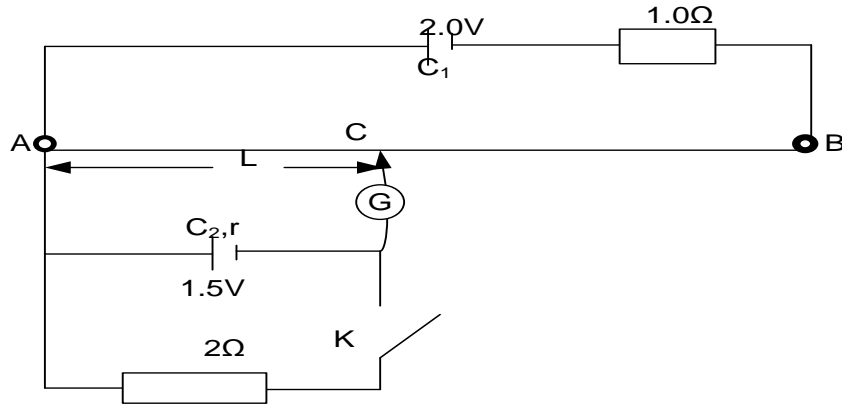


In the circuit above, AB is a uniform wire of length 1 m and resistance  $4.0 \Omega$ .  $C_1$  is an accumulator of e.m.f 2 V and negligible internal resistance.  $C_2$  is a cell of e.m.f 1.5 V.

(a) Find the balance length AC when the switch is open

(b) If the balance length is 75.0 cm when the switch is closed, find the internal resistance of  $C_2$ .

**Solution:**

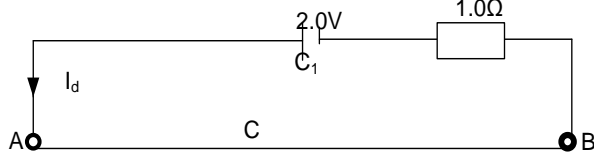(a) Consider the driver cell circuit only.



$$2 = I_d(R_{AB} + 1)$$

$$2 = I_d(4 + 1)$$

$$I_d = \frac{2}{5} = 0.4 \text{ A}$$


P.d across the whole wire,  $V_{AB} = I_d R_{AB}$  where  $R_{AB}$  is the resistance of wire AB.

$$V_{AB} = 0.4 \times 4 = 1.6 \text{ V}$$

P.d per cm,  $k$  of AB is given by:

$$k = \frac{V_{AB}}{AB} = \frac{1.6}{100} = 0.016 \text{ V cm}^{-1}$$

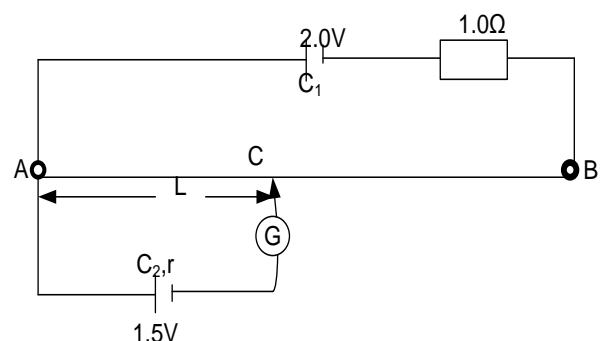
With S open cell  $C_2$  is now on an open circuit and at balance; p.d across AC = e.m.f of  $C_2$ .




$$V_{AD} = kl = 1.5$$

$$l = \frac{1.5}{k} = \frac{1.5}{0.016} = 93.75 \text{ cm}$$

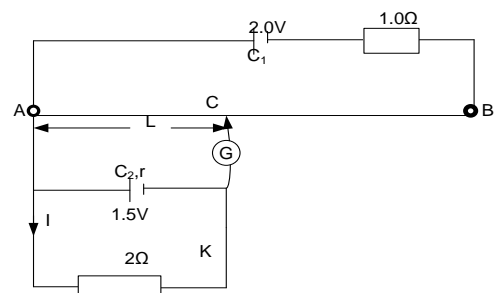(b) With S closed, current is drawn from  $C_2$  and the cell is now on a closed circuit and supplies current  $I$  to the  $2.0 \Omega$  resistor.



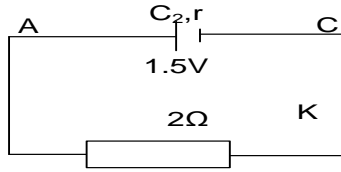

At balance p.d across AC = p.d across the  $2.0 \Omega$  resistor,  $V$

$V = k.l$  where  $l = 75.0 \text{ cm}$

$$V = 0.016 \times 75 = 1.2 \text{ V}$$

But  $V = IR$ , hence  $I = \frac{V}{R} = \frac{1.2}{2} = 0.6 \text{ A}$

Since at balance the current through G is zero, we can now only consider the lower circuit shown above.

From  $E = I(R + r)$  we have;

$$1.5 = 0.6(2 + r)$$

$$1.5 = 1.2 + 0.6r$$


$$r = \frac{0.3}{0.6} = 0.5 \Omega$$

Or

$$r = R \left( \frac{l_0}{l} - 1 \right)$$

$$r = 2 \left( \frac{93.7}{75} - 1 \right) = 0.5 \Omega$$

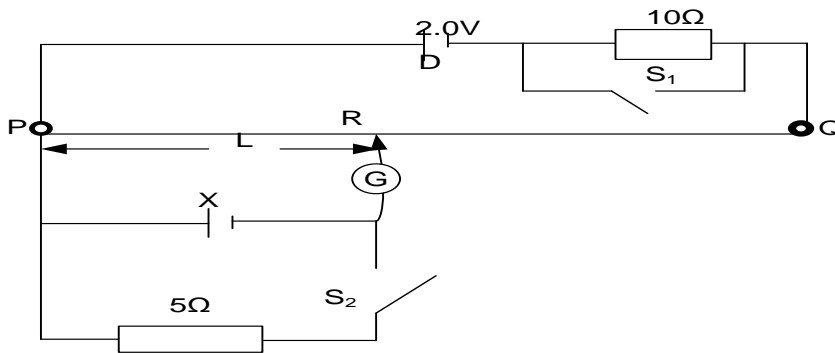4. The figure below shows a cell D of negligible internal resistance with e.m.f  $2V$ . PQ is a uniform slide wire of length  $1.00 \text{ m}$  and resistance  $50 \Omega$ .



With both switches  $S_1$  and  $S_2$  open, the balance length PR is  $0.90 \text{ m}$ . When  $S_2$  is closed and  $S_1$  left open, the balance length changes to  $0.75 \text{ m}$ . Determine the

- e.m.f of cell X.
- internal resistance,  $r$ , of X
- balance length when both  $S_1$  and  $S_2$  are closed

**solution**

- (i) with both switches open:  $2 = I_d(R_{AB} + 10)$

$$2 = I_d(50 + 10)$$

$$I_d = \frac{1}{30} \text{ A}$$

P.d across the wire AB:  $V_{AB} = \frac{1}{30} \times 50 = \frac{5}{3} \text{ V}$

P.d per cm,  $k$  of AB is given by:

$$k = \frac{5}{300} \text{ V cm}^{-1}$$

e.m.f of cell  $x = kl$

$$E = \frac{5}{300} \times 90 = 1.5 \text{ V}$$

- (ii) With  $S_2$  closed:  
p.d across x;

$$V = \frac{5}{300} \times 75 = 1.25 \text{ V}$$

current supplied by x:

$$I = \frac{V}{R} = \frac{1.25}{5} = 0.25 \text{ A}$$

But  $E = I(r + R)$

$$1.5 = 0.25(r + 5)$$

$$r = 1 \Omega$$

Or

$$\frac{E}{V} = \frac{l_0}{l}$$

$E = I(R + r)$  and  $V = IR$

$$\frac{I(R + r)}{IR} = \frac{l_0}{l}$$

$$r = 5 \left( \frac{90}{75} - 1 \right) = 1.0 \Omega$$

(iii) When both switches are closed  
 $10\Omega$  is out of the circuit, current passes through the switch

$$\begin{aligned} 2 &= I_d(R_{AB}) \\ 2 &= I_d(50) \\ I_d &= \frac{1}{25} A \end{aligned}$$

P.d across the wire AB:  $V_{AB} = \frac{1}{25} \times 50 = 2 V$

P.d per cm,  $k$  of AB is given by:


$$k = \frac{2}{100} V \text{ cm}^{-1}$$

e.m.f of cell  $x = kl$

$$\begin{aligned} 1.25 &= \frac{2}{100} xl \\ l &= 62.5 \text{ cm} \end{aligned}$$
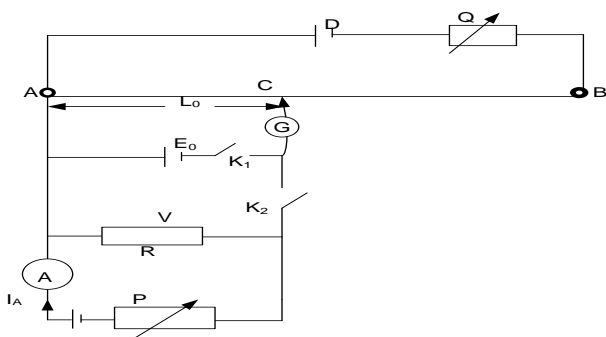
### **Calibration of an ammeter and Current Measurement**

Current can be measured on a potentiometer by measuring the p.d  $V$  it sets up across a standard resistance  $R$ , and then using  $I = \frac{V}{R}$ .




- Connect a standard cell of e.m.f  $E_0$  and a standard low resistance  $R$  as shown above.
- With switches  $K_1$  closed and keep  $K_2$  open, tap the jockey at different positions along AB until the galvanometer shows no deflection.

- Measure and record the balance length  $l_0$
- P is adjusted so that the ammeter records the smallest current  $I_r$ . With switch  $K_1$  open and  $K_2$  closed, the balance length  $l$  is obtained and recorded.
- Determine the actual current  $I_A$ ,  $\left( I_A = \frac{E_0}{l_0} \times \frac{l}{R} \right)$  and error  $e$ , in the ammeter reading,  $e = I_A - I_r$  and
- The experiment is repeated for different adjustments of P and hence for different readings of the ammeter  $I_r$ .
- Tabulate the results including values of  $I_r$  and  $e$ .
- Plot a calibration graph of  $e$  against  $I_r$ .

**NB:** The percentage error in the ammeter reading =  $\frac{e}{I_a} \times 100\%$ .

By calculating  $l_0$  the potentiometer is being used to measure current.  
 The nature of the graph shows that the errors in  $l_r$  occur randomly.


### **Example:**

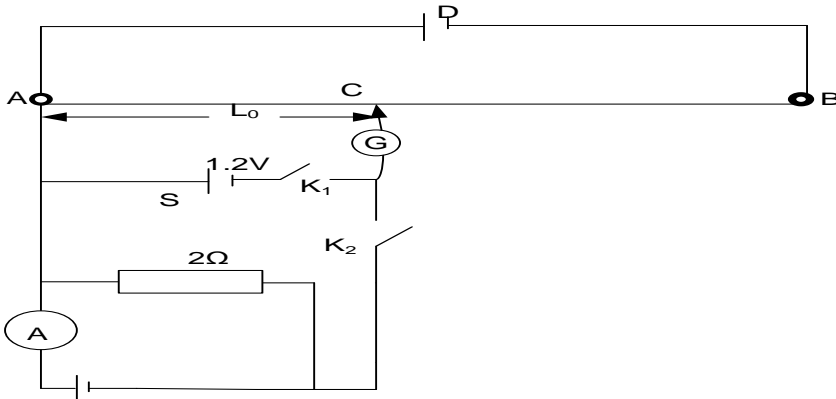

In the circuit above,  $S$  is a standard cell of e.m.f  $1.2\text{ V}$ . When switch  $K_1$  is closed and  $K_2$  is open, a balance length  $AC = 30.2\text{ cm}$  is obtained. When  $K_1$  is opened and  $K_2$  is closed, the balance length is  $26.8\text{ cm}$  and the ammeter,  $A$  reads  $0.4\text{ A}$ . Calculate the percentage error in the ammeter reading.

**Solution**

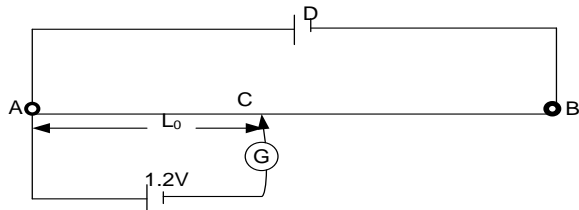**$K_1$  is closed and  $K_2$  is open;**




At balance, p.d across  $AC = 1.2$

$$30.2 \times k = 1.2$$

$$k = \frac{1.2}{30.2} = 0.0397\text{ V cm}^{-1}$$

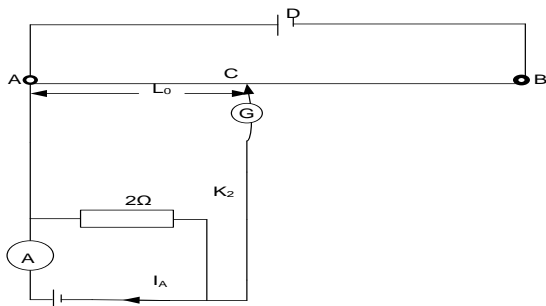**$K_1$  is opened and  $K_2$  is closed;**



**Calibration of Voltmeter**

At balance, p.d across  $AC =$  p.d across  $2\ \Omega$

$$V = AC \times k$$

$$V = 26.8 \times 0.0397 = 1.064\text{ V}$$

But  $V = I_a R$


$$I_a = \frac{V}{R} = \frac{1.064}{2} = 0.532\text{ A}$$

Error in the ammeter reading,  $e = I_a - I_r$

$$e = 0.532 - 0.4 = 0.132\text{ A}$$

$$\text{percentage error} = \frac{e}{I_a} \times 100\%$$
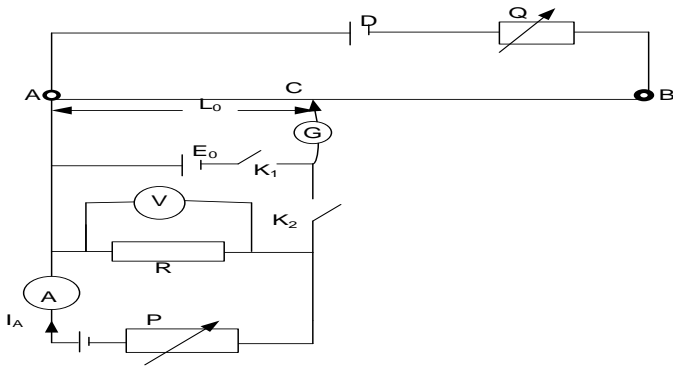
$$= \frac{0.132}{0.532} \times 100 = 24.8\%$$




- ❖ A standard cell of e.m.f  $E_0$  and a rheostat P are connected as shown above.
- ❖ Switch  $K_1$  is closed while  $K_2$  is left open. A balance point is located where the galvanometer indicates zero deflection. The balance length  $l$  is measured and recorded..

- ❖ The p.d per cm,  $k$  of the slide wire is calculated from  

$$k = \frac{E_0}{l_0} \dots\dots\dots 1$$
- ❖ P is adjusted so that the voltmeter records the smallest p.d it possible to read.  $K_1$  is then closed and a point is located where the galvanometer register zero current.
- ❖ The balance length  $l$  is obtained and recorded.
- ❖ The experiment is repeated for different adjustments of P and hence for different readings,  $V_r$  of the voltmeter. Balance length  $l$  is determined.
- ❖ The results are tabulated including values of  $V_a = kl$  and the error  $e = (V_a - V_r)$ .
- ❖ A graph of  $e$  against  $V_r$  is plotted and constitutes the calibration curve for the voltmeter.

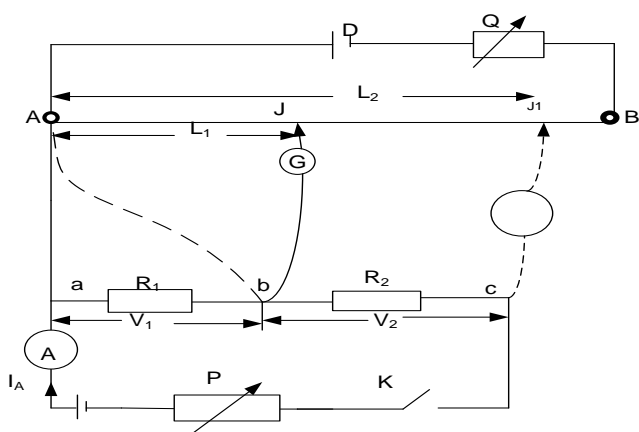**Comparison of two Resistances (measurement of resistance)**



- ❖ Connect the two resistances  $R_1$  and  $R_2$  in series with an ammeter A and rheostat P as shown above.
- ❖ Close switch K. With the galvanometer at **a** and **b**, the balance length  $AJ = l_1$  is measured and recorded. Hence  $IR_1 = kl_1 \dots\dots\dots (i)$
- ❖ Connections at **a** and **b** are removed and replaced by those at **b** and **a** (dotted lines).
- ❖ The balance length  $AJ' = l_2$  is measured and recorded. Hence  $IR_2 = kl_2 \dots\dots\dots (ii)$


$$\frac{R_1}{R_2} = \frac{l_1}{l_2}$$

**Practical points to note**

1. If the balance point cannot be obtained with both resistances, then either  $I$  is too large or the p.d  $V_{AB}$  across AB is very small. Balance can be achieved by adjusting rheostats P and Q.
2. If balance can be obtained with  $R_1$  and not with  $R_2$ , then  $R_2$  is much greater than  $R_1$ . The method is thus suitable for resistances that do not differ much in magnitude.
3. If the balance lengths are very small, an end – error (correction) due to the resistance of the contact at the zero end must be added to the balance lengths.

**Example**

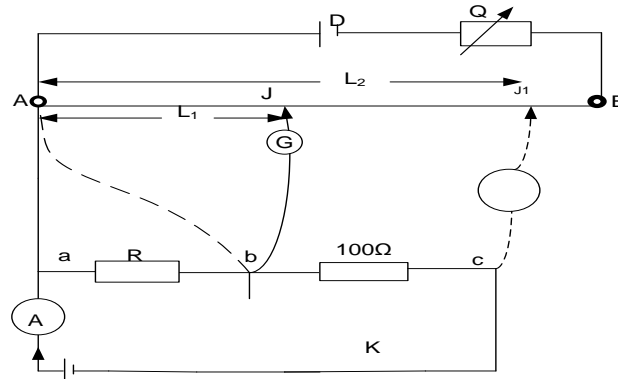1. The circuit below is used to compare the resistance  $R$  of an unknown resistor with a standard  $100\ \Omega$  resistor.



The distances  $l$  from one end of the slide wire of the potentiometer to the balance point are  $40.0\text{ cm}$  and  $58.8\text{ cm}$ , respectively when  $G$  is connected to  $b$  and then to  $c$  respectively. If the slide wire is  $1.00\text{ m}$  long, find the value of  $R$ .

**Solution**

Let the current in the lower circuit be  $I$

With  $G$  connected at  $b$ ,

the p.d across  $100\ \Omega = \text{p.d across } l_1$

$$100I = kl_1$$

where  $k$  is the p.d per cm and  $l_1 = 40.0\text{ cm}$

$$100I = 40k \text{ ----- 1}$$

With  $G$  at  $c$  p.d  $100 + R = \text{p.d across the new balance length,}$

$$(100 + R)I = kl_2$$

$$(100 + R)I = 58.8k \text{ ----- 2}$$


Divide equation 2 by equation 1

$$\frac{100 + R}{100} = \frac{58.8}{40.0}$$

$$100 + R = 147$$

$$R = 47\ \Omega$$

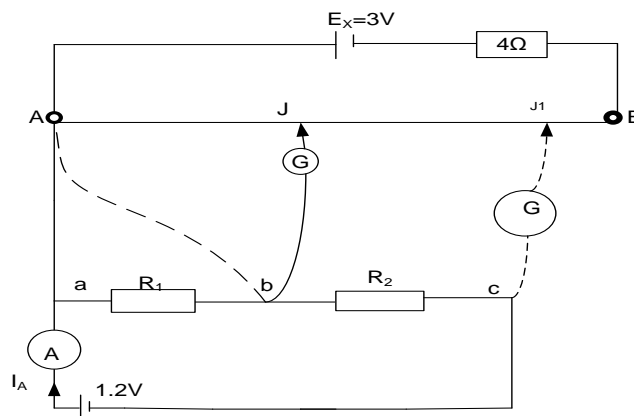2. An accumulator of e.m.f  $3\text{V}$  with negligible internal resistance is connected in series to a  $4\ \Omega$  resistor and a potentiometer wire  $AB$  of length  $1.0\text{m}$  as shown below.



The accumulator supplies a steady current of  $0.25\text{A}$  through the wire  $AB$ . With the galvanometer connected at  $b$ , the balance length  $AJ = 46\text{cm}$  and when the galvanometer is at  $c$ , the balance length  $AJ^1 = 75\text{cm}$ . Find;

- (i) The value of  $R_1$  and  $R_2$
- (ii) The reading of the ammeter  $A$

**Solution**

(i) The current along  $AB$   $I = 0.25\text{A}$

p.d across  $4\ \Omega = 0.25 \times 4 = 1.0\text{V}$

P.d across AB  $V_{AB} = 3 - 1 = 2V$   
P.d per cm along AB,  $k = \frac{2}{100} = 0.02 Vcm^{-1}$   
With G connected at b,  
the p.d across  $R_1 =$  p.d across /  
 $R_1 I = k l_1$   
where k is the p.d per cm and  $l_1 = 46.0$  cm  
 $R_1 \times 0.25 = 0.02 \times 46$   
 $R_1 = 3.68 \Omega$

With G at c, p.d  $R_1$  and  $R_2 =$  p.d across the new balance length,

$$(R_1 + R_2)I = k l_2$$

$$(3.68 + R_2) \times 0.25 = 0.02 \times 75$$

$$R_2 = 2.32 \Omega$$

(ii)

$$(R_1 + R_2)I_A = 1.2$$

$$\frac{1.2}{3.68 + 2.32} = I_A$$

$$I_A = 0.2A$$


### MEASUREMENT OF THERMOELECTRIC E.M.F

The e.m.fs of thermo junctions (thermocouples) are very small; of the order of a millivolt.

If such an e.m.f is measured on a simple potentiometer the balance – point is found to be very near end A and results in the end –error being serious, thus affecting the value obtained.
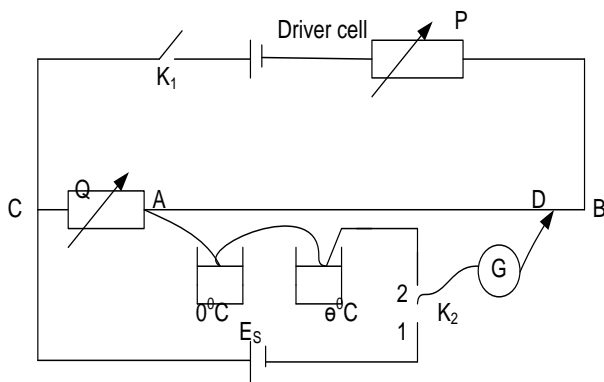
#### How to modify the simple potentiometer to measure small e.m.f.s or p.d.s

To obtain measurable balance lengths a suitable high resistance R is connected in series with the slide wire so that the driver cell sets up a small p.d across AB. This helps in producing a small p.d per cm.



- ❖ The standard cell of emf  $E_s$  is connected across Q and the slide wire.
- ❖  $K_1$  is closed and  $K_2$  is connected to position 1. Tap the jockey at different positions along wire AB until the galvanometer shows no deflection.
- ❖ The balance length  $l_s$  is measured and recorded.
- ❖ While  $K_1$  is closed,  $K_2$  is connected to position 2 and the point on AB when the galvanometer registers zero current is found. The balance length  $l$  is measured.
- ❖  $E$  is found using the formula  $E = \frac{E_s r l}{Q + r l_s}$  where  $r$  is the resistance per cm of the slide wire.

#### Theory of experiment

Current through the wire AB  $i_p = \frac{V_0}{P + Q + r l}$

where L is the length of the wire.

Hence p.d per cm,  $k = i_p r = \frac{V_0 r}{P + Q + r l}$

When  $K_2$  is in position 1,  $E_s = i_p Q + k l_s$

$$E_s = \frac{V_0}{P + Q + r l} (Q + r l_s) \dots \dots \dots (i)$$

When  $K_2$  is in position 2,  $E = k l$

Where E is the emf of the thermocouple.

$$E = \frac{V_0 r l}{P + Q + r l} \dots \dots \dots (ii)$$


equation (ii) divide by (i)

$$\frac{E}{E_s} = \frac{r l}{Q + r l_s}$$

$$\text{Hence } E = \frac{E_s r l}{Q + r l_s}$$

**Examples:**

1.

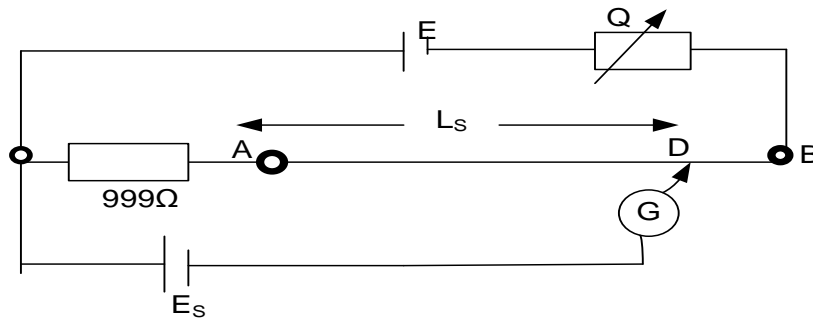

In the figure above, E is a driver cell of e.m.f 2 V and negligible internal resistance.  $E_s$  is a standard cell of e.m.f 1.00 V and AB is a uniform wire of resistance  $10 \Omega$  and length 100 cm. the galvanometer G shows no deflection when  $l_s = 10.0 \text{ cm}$ . Find

- (i) The current in the driver circuit
- (ii) The resistance of the rheostat
- (iii) The e.m.f of a thermocouple which is balanced by a length of 60 cm of the slide wire AB.

**Solution:**

- (i) Let the resistance per cm of AB be  $\beta$

$$\beta = \frac{R_{AB}}{100} = \frac{10}{100} = 0.1 \Omega \text{ cm}^{-1}$$

$$R_{AD} = \beta l_s$$

$$R_{AD} = 0.1 \times 10 = 1 \Omega$$


But,  $E_s = V_{999} + V_{AD}$

$$E_s = I_d(R + R_{AD})$$


$$I_d = \frac{E_s}{R + R_{AD}}$$

$$I_d = \frac{1}{999 + 1} = \frac{1}{1000} = 0.001 \text{ A}$$

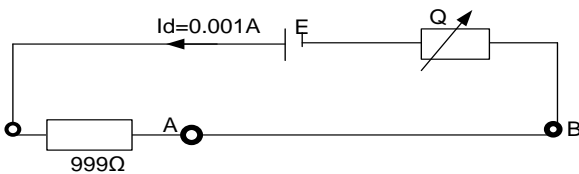- (ii)  $E = I_d(999 + 10 + R)$   
 $2 = 0.001(1009 + R)$   
 $= 1.009 + 0.001R$   
 $R = 991 \Omega$



- (iii)

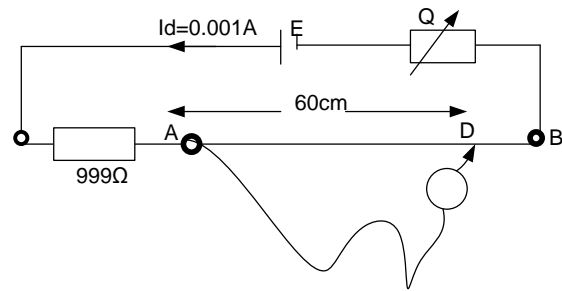

$$V_{AB} = I_d R_{AB}$$


$$V_{AB} = 0.001 \times 10 = 0.01 \text{ V}$$

$$\text{p. d per cm, } k = \frac{V_{AB}}{100} = \frac{0.01}{100}$$

$$k = 0.0001 \text{ V cm}^{-1}$$

$$E = kl = 0.0001 \times 60 = 0.006 \text{ V}$$

2.

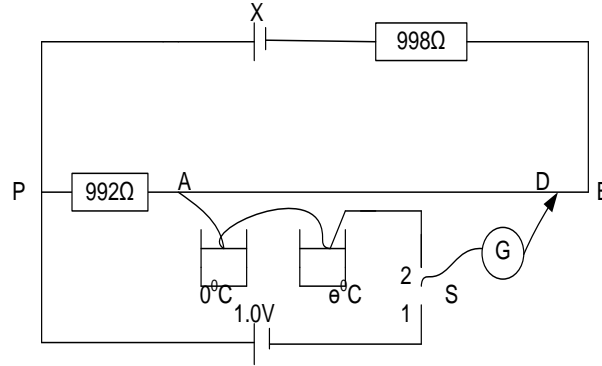

In the figure above X is an accumulator of negligible internal resistance. AB is a uniform wire of length 1.0m and diameter  $3.57 \times 10^{-4} \text{m}$  and resistivity  $1.0 \times 10^{-6} \Omega \text{m}$ . G is a galvanometer connected to a sliding contact D. When s is in position 1, G shows no deflection when AD is 80cm. When s is in position 2, G shows no deflection when AD is 40cm. find;

- (i) The resistance of AB
- (ii) E.m.f of the thermocouple
- (iii) The e.m.f of the accumulator x

**Solution**

$$(i) \quad R = \rho \frac{l}{A}$$

$$R_{AB} = 1.0 \times 10^{-6} \times \frac{1}{\pi \left( \frac{3.57 \times 10^{-4}}{2} \right)^2}$$

$$R_{AB} = 10 \Omega$$

- (ii) When s is in position 1, the 1.0V cell is being balanced  
For the driver cell; Let the resistance per cm of AB be  $\beta$

$$\beta = \frac{R_{AB}}{100} = \frac{10}{100} = 0.1 \Omega \text{ cm}^{-1}$$

$$R_{AD} = \beta l_s$$

$$R_{AD} = 0.1 \times 80 = 8 \Omega$$

$$\text{At balance: } 1.0 = V_{PA} + V_{AD}$$

$$1.0 = I_d(R + R_{AD})$$

$$I_d = \frac{1}{992+8} = \frac{1}{1000} = 0.001 \text{ A}$$

$$V_{AB} = I_d R_{AB}$$

$$V_{AB} = 0.001 \times 10$$

$$V_{AB} = 0.01 \text{ V}$$

$$\text{p.d per cm along AB; } k = \frac{0.01}{100} = 1 \times 10^{-4} \text{ V cm}^{-1}$$

When s is in position 2, the thermocouple is being balanced

$$E_T = kl$$

$$E_T = 1 \times 10^{-4} \times 40$$

$$E_T = 4 \text{ mV}$$

$$(iii) \quad E_x = I_d(998 + 992 + 10)$$

$$E_x = 0.001(998 + 992 + 10)$$

$$E_x = 2.0 \text{ V}$$

**Advantages of a potentiometer**

1. It does not draw any current from the p.d being measured and therefore gives accurate results. Resistance of the connecting wires and the galvanometer does not affect the results.
2. It can measure a wide range of p.ds since the length of the slide wire can be adjusted.
3. It gives accurate results since they depend only on measurements of lengths, standard resistances and standard e.m.fs.

**Disadvantages:**


1. It does not give direct results and is therefore time consuming;
2. It requires technical skills to operate;
3. It is cumbersome.

**Exercise**

1. A dry cell gives a balance length of 85.0cm on a potentiometer wire. When a resistor of resistance  $16\Omega$  is connected across the terminals of the cell, a balance length of 76.0cm is obtained. Find the internal resistance of the cell. **An(1.89 $\Omega$ )**
2. A dry cell gives a balance length of 0.75m on a potentiometer wire. When the cell is shunted by a resistance of  $14\Omega$ , the balance length of 0.70m is required. Find the internal resistance of the cell. **An(1.0 $\Omega$ )**
3. A  $1\Omega$  resistor is in series with an ammeter  $m$  in a circuit. The p.d across the resistor is balanced by a length of 60cm on a potentiometer wire. A standard cell of emf 1.02V is balanced by a length of 50cm. If  $m$  reads 1.1A, what is the error in the reading? **An(0.124A)**
4. A potentiometer wire of length 1m and resistance  $1\Omega$  is used to measure an emf of the order mV. A battery of emf 2V and negligible internal resistance is used as a driver cell. Calculate the resistance to be in series with potentiometer so as to obtain a potential drop of 5mV across the wire. **An(399 $\Omega$ )**
5. In a potentiometer, a cell of emf  $x$  gave a balance length of  $a$  cm and another cell of emf  $y$  gave a balance length of  $b$  cm. When the cells are connected in series, a balance length of  $c$  cm was obtained.

It was also discovered that  $a + b \neq c$ . Show that the true ratio  $\frac{x}{y} = \frac{c-b}{c-a}$ .


6.

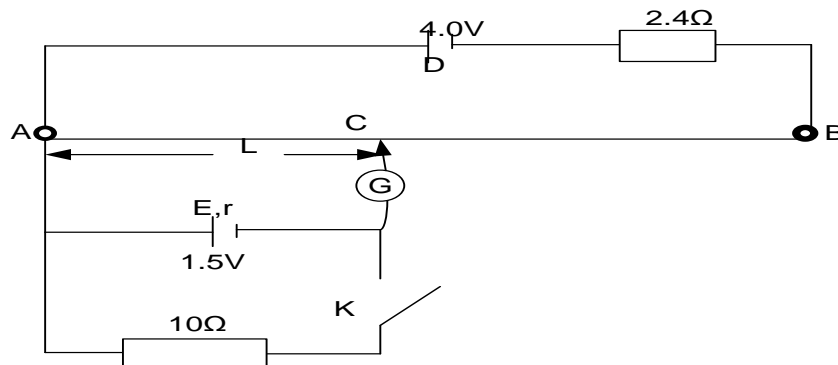

In the circuit above, AB is a uniform wire of length 1 m and resistance  $2.0\Omega$ . D is a cell of e.m.f 4.0 V and negligible internal resistance. E is a cell of e.m.f 1.5 V.

- (i) Find the balance length AC when the switch is open. **An(82.5cm)**
- (ii) If the balance length is 71.5 cm when the switch is closed, find the internal resistance of E. **An(1.54 $\Omega$ )**


7.

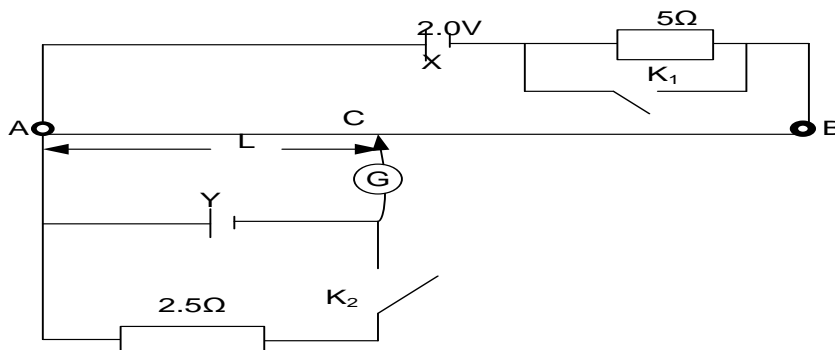

In the circuit above,  $\mathcal{E}$  has negligible internal resistance and length AB is 100cm and resistance of AB is  $20\Omega$ . When  $K_1$  and  $K_2$  is open, the balance length  $AC = 80\text{cm}$ . When  $K_2$  is closed and  $K_1$  open, the balance length  $AC = 65\text{cm}$ . Find

- (i) the emf of cell y
- (ii) internal resistance of cell y.
- (iii) the balance length when  $K_1$  and  $K_2$  are closed.


8.

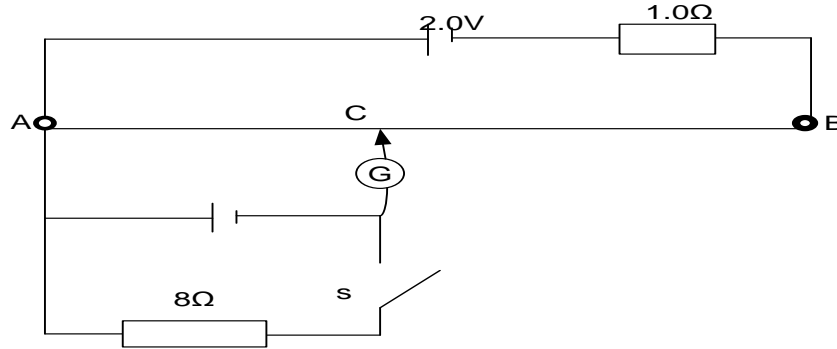

In the figure above the slide wire AB is 1 m long and has a resistance of  $4\Omega$ . When switch S is:

- (i) open, the balance length AC is 88.8 cm. Find the value of the e.m.f of the cell
- (ii) closed, the balance length is found to be 82.5 cm. Calculate the internal resistance of this cell

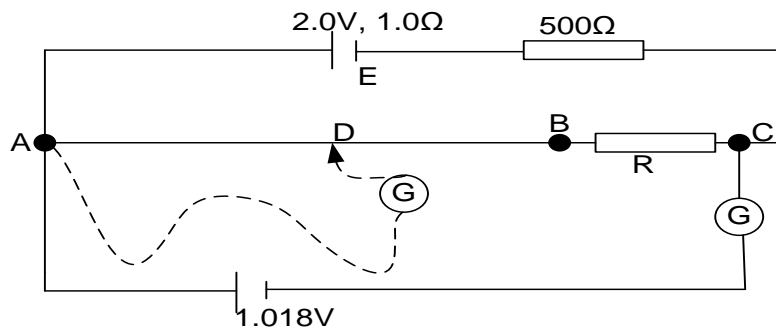9. In the figure below, AB is a uniform resistance wire of length 1.00 m and resistance  $10.0\Omega$ . E is an accumulator of e.m.f 2.0 V and internal resistance  $1.0\Omega$




When a standard cell of e.m.f 1.018 V is connected in series with a galvanometer, G across AC, the galvanometer shows no deflection. When the standard cell is removed and a thermocouple connected via the galvanometer, G, as shown by the dotted line, G shows no deflection when  $AD = 41.0\text{ cm}$ .

Calculate the:

- (i) value of R,
- (ii) e.m.f of the thermocouple. **An(509.3Ω, 8.04mV)**
- (iv)

10.

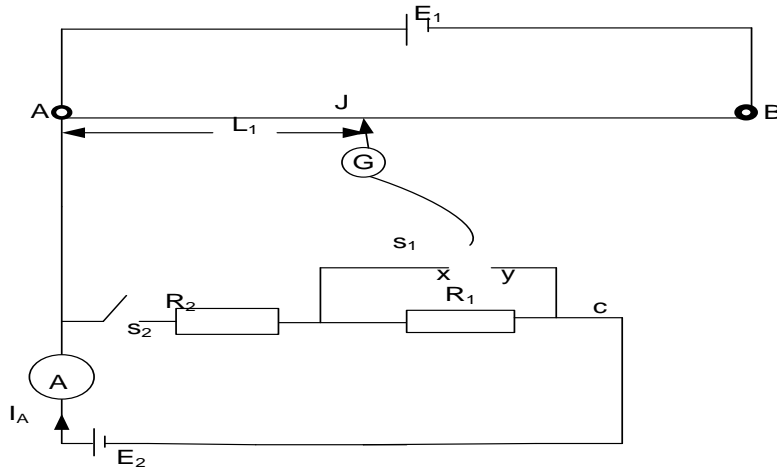


The circuit above shows a uniform slide wire AB of length 100 cm. The e.m.f. of cell  $E_1$  is 2.0 V and its internal resistance is negligible.  $E_2$  is a cell of e.m.f 1.1 V and its internal resistance is  $1.0 \Omega$ ,  $R_1 = 1.0 \Omega$  and  $R_2 = 2.0 \Omega$ . The switch  $S_1$  enables the galvanometer G to be connected to X or Y. Calculate the balance length for each position of  $S_1$  when the switch  $S_2$  is


- (a) open and
- (b) Closed.

**Uneb 2016**

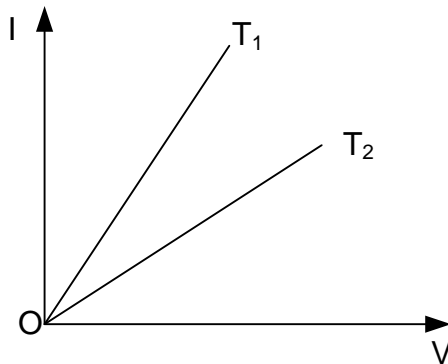- (a) (i) Define **electrical resistivity** (01mark)
- (ii) Explain how length and temperature of a conductor affect its resistance. (04marks)
- (iii) Figure below shows the current- voltage graphs for a metallic wire at two different temperatures  $T_1$  and  $T_2$



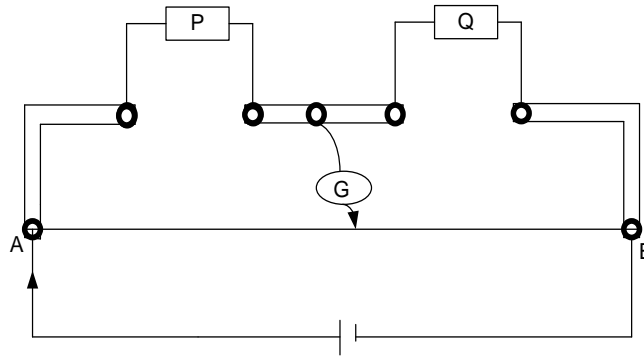- (b) State which of the two temperature is greater and explain your answer. (03marks)
- (i) Derive the balance condition when using a meter bridge to measure resistance. (04marks)
- (ii) State two precautions taken to achieve an accurate measurement. (02marks)
- (c) Figure below show two resistors P and Q of resistance  $5\Omega$  and  $2\Omega$  respectively connected in the two gaps of the meter bridge.





A resistance  $X$  of cross-sectional area  $1\text{mm}^2$  is connected across  $P$  so that the balance point is  $66.7\text{ cm}$  from  $A$ . If the resistivity of the wire  $X$  is  $1.0 \times 10^{-5} \Omega\text{m}$  and the resistance wire  $AB$  of the meter bridge is  $100\text{cm}$  long, calculate the length of  $X$ . (04marks)

- (d) Explain how electrons attain a steady drift velocity when current flows through a conductor. (02marks)

**Uneb 2015**

- (a) (i) Define **temperature coefficient** of resistance (01mark)  
(ii) Explain the origin of the heating effect of electric current in a metal conductor. (03marks)  
(iii) Describe with the aid of an  $I$ - $V$  sketch the variation of current with p.d across a semiconductor. (02marks)

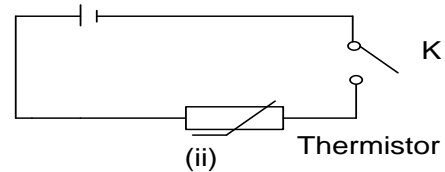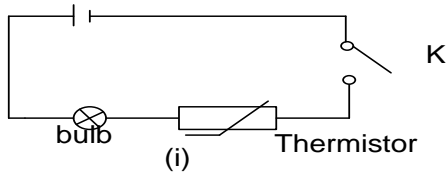
- (b) A cell, a bulb, a switch and a thermistor with negative temperature coefficient of resistance are connected as shown below



- (i) Explain what would happen when in figure (i) switch  $K$  is closed (04marks)  
(ii) If the bulb in figure (i) is removed and circuit connected as shown in figure (ii), explain what happens when switch  $K$  is closed. (03marks)

- (c) State the **law of conservation of current at a junction**. (01mark)

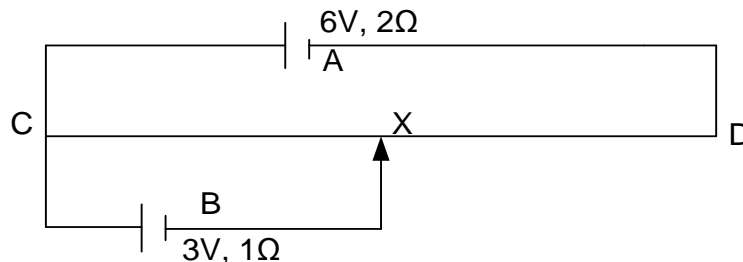- (d) Two cells  $A$ , of e.m.f  $6\text{V}$  and internal resistance  $2\Omega$  and  $B$  of e.m.f  $3\text{V}$  and internal resistance  $1\Omega$  respectively are connected across a uniform resistance wire  $CD$  of resistance  $8\Omega$  as shown below



If  $X$  is exactly in the middle of the wire  $CD$ , calculate the;

- (i) Power dissipated in  $CX$  (04marks)  
(ii) P.d across the terminals of cell  $A$  (02marks)